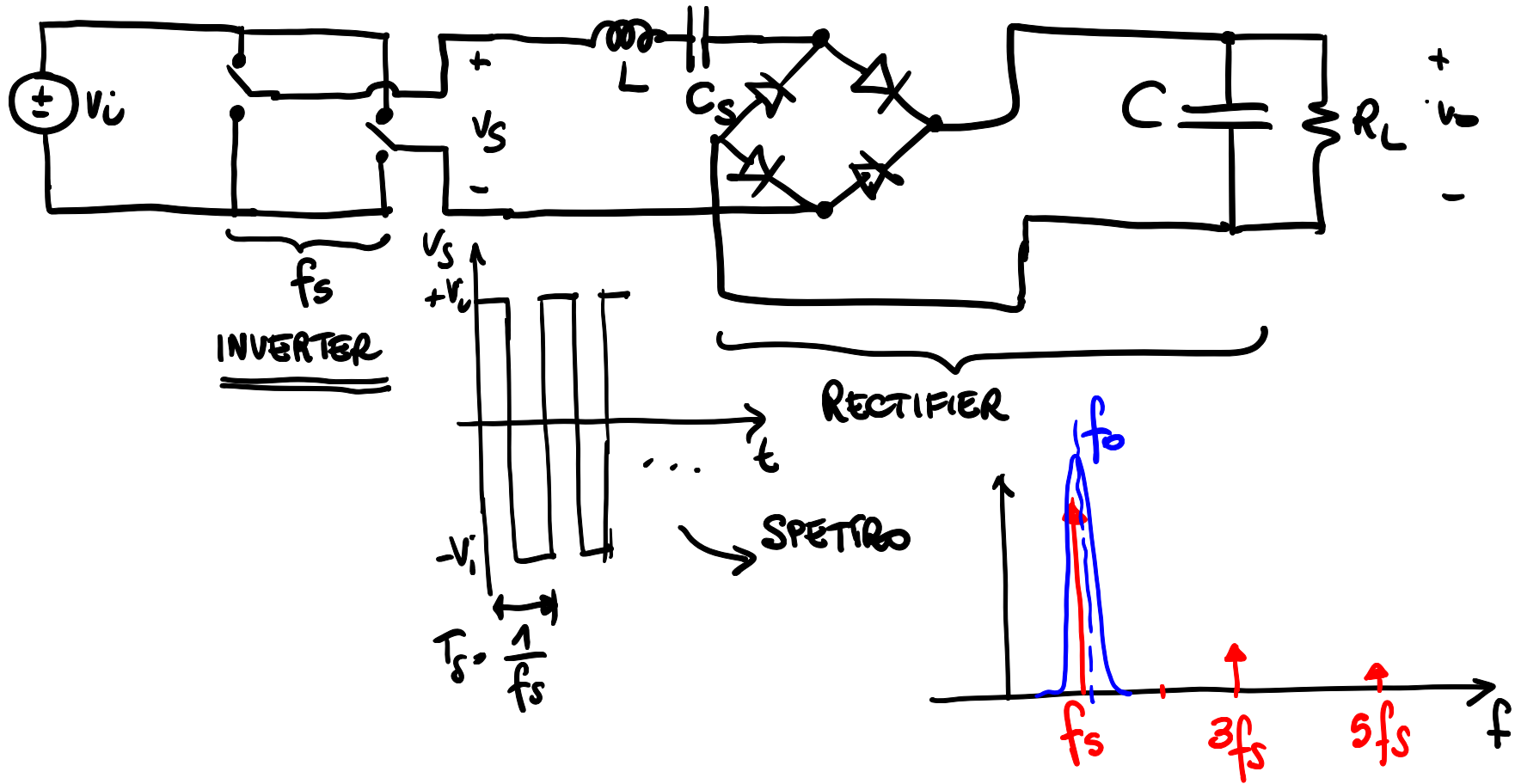




Convertitori RISONANTI (DC-DC)

Filtro LC Risonante



Analisi con approssimazione sinusoidale (1^a armonica)

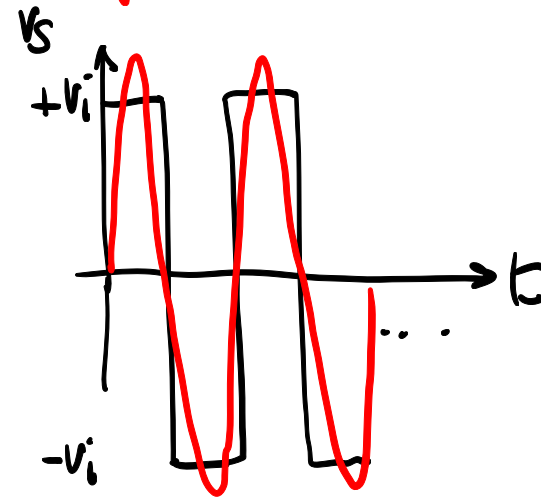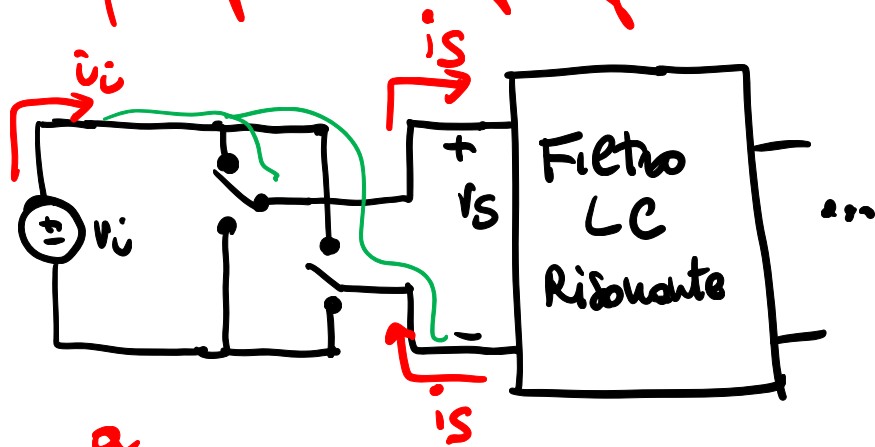si può fare se $f_s \gg f_0$ e Q del filtro LC alto




1^a armonica

$$v_{s_1}(t) = \frac{4}{\pi} v_i \sin(\omega_s t)$$

$$i_{s_1}(t) = I_{s_1} \sin(\omega_s t - \phi_s)$$

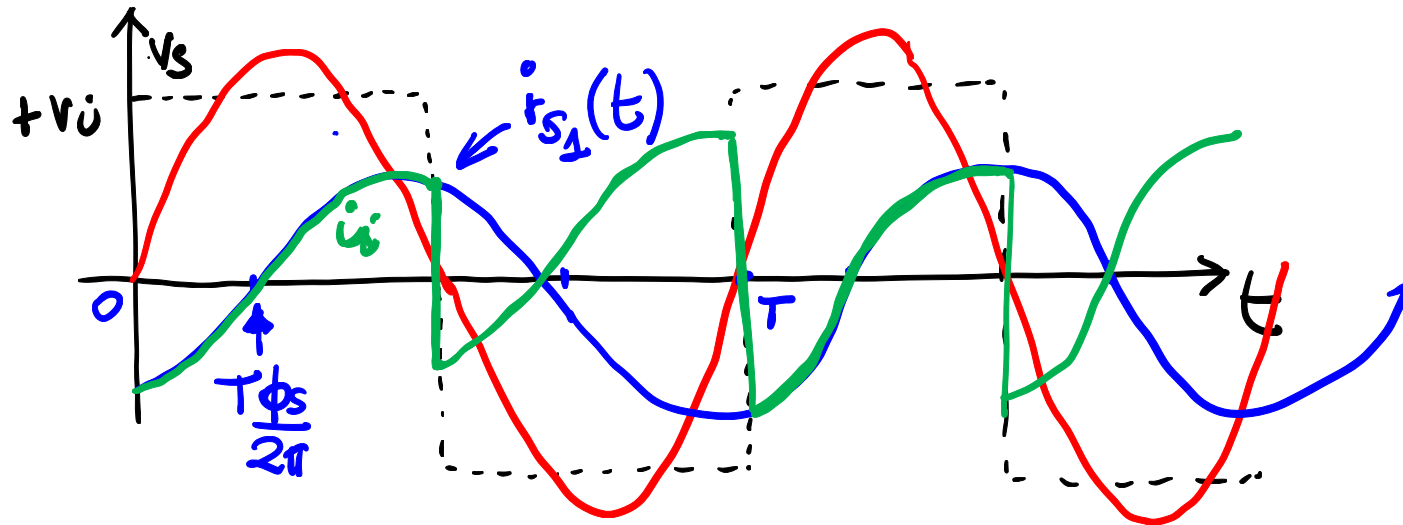[se $v_s = v_i$ allora $i_s = i_i$]
 [se $v_s = -v_i$ allora $i_s = -i_i$]





$$\langle i_i \rangle = \frac{1}{T/2} \int_0^{T/2} i_{s1}(t) dt = \frac{1}{T/2} \int_0^{T/2} I_{s1} \sin(\omega_s t - \phi_s) dt =$$

$$= \frac{1}{T/2} \frac{I_{s1} \cos(\omega_s t - \phi_s)}{\omega_s} \Big|_0^{T/2} = \frac{-2}{T\omega_s} I_{s1} \left[\cos\left(\frac{\omega_s T}{2} - \phi_s\right) - \cos(-\phi_s) \right]$$



$$\langle i_i \rangle = +\frac{2}{\pi} I_{s1} \cos \phi_s$$

$$\frac{\omega_s T}{2} = \frac{2\pi f_s}{2} \frac{1}{f_s} = \pi$$

CIRCUITO EQUIVALENTE :

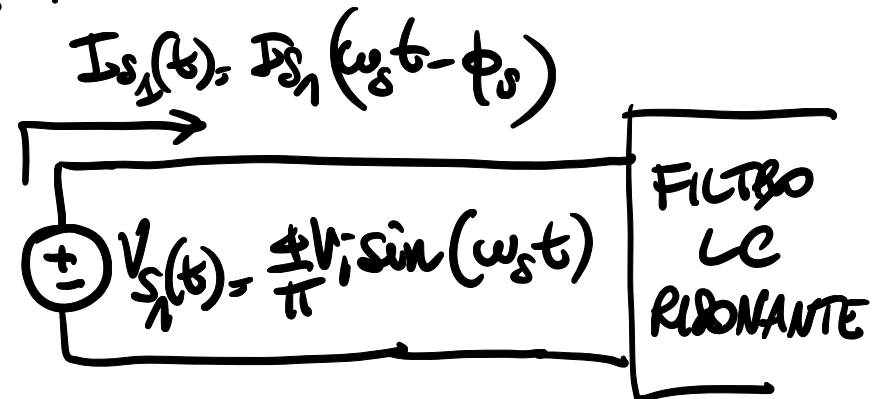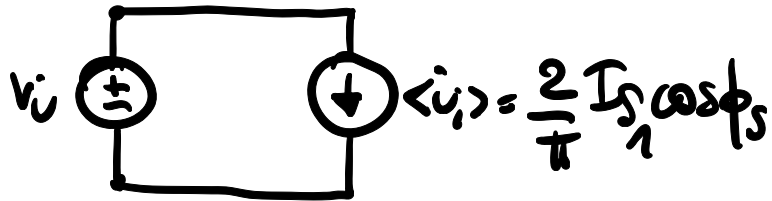

Raddrizzatore

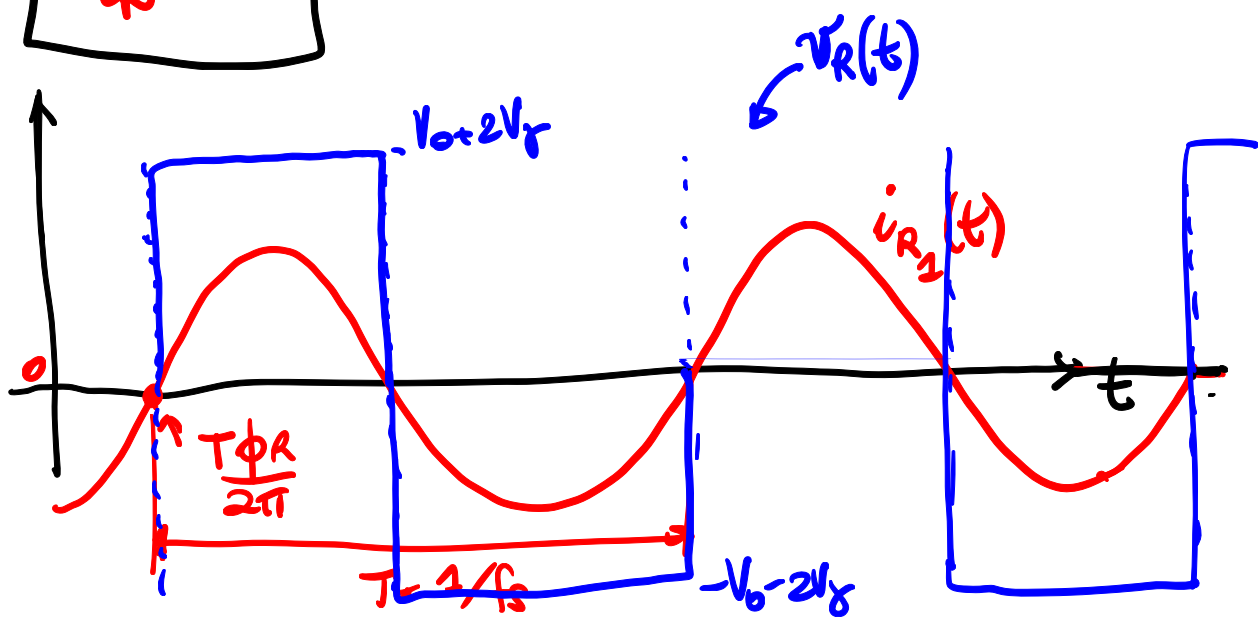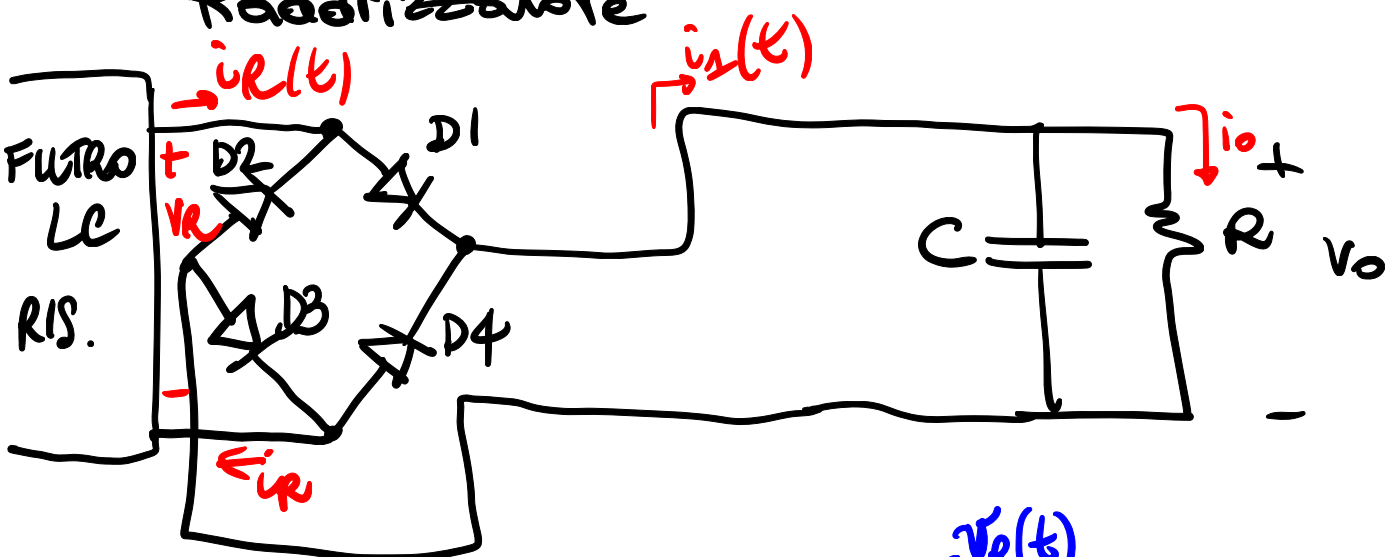

se $i_R > 0$

$D1, D3$ ON
 $D2, D4$ OFF $\Rightarrow v_o = v_R - 2V_\gamma$
 $v_R = v_o + 2V_\gamma$



se $i_R < 0$

$D1, D3$ OFF
 $D2, D4$ ON $\Rightarrow v_o = -v_R - 2V_\gamma$
 $v_R = -v_o - 2V_\gamma$

$$i_{R1}(t) = \underline{I_{R1}} \sin(\omega_s t - \phi_R)$$

$$v_{R1}(t) = \frac{4}{\pi} \underbrace{(v_o + 2V_\gamma)}_{V_{R1}} \sin(\omega_s(t) - \phi_R)$$

CIRCUITO equivalente (1^a armonica)

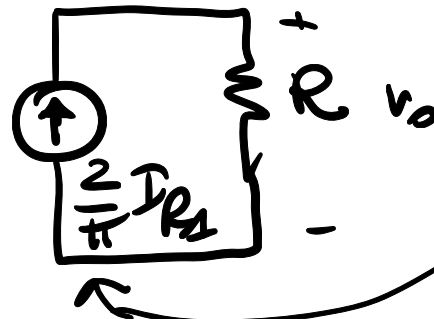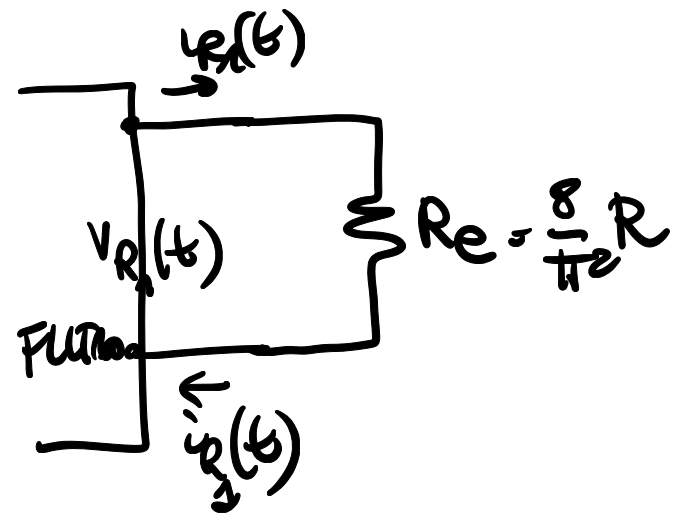

$$i_1(t) = |i_R(t)|$$

$$\langle i_0 \rangle = \langle i_1(t) \rangle = \langle |i_R(t)| \rangle$$

$$\langle i_0 \rangle = \frac{2}{\pi} I_{R1}$$

$$v_0 = \langle i_0 \rangle R = \frac{2}{\pi} I_{R1} R$$


$$v_{R1} = \frac{4}{\pi} (v_0 + 2v_\delta) = \frac{4}{\pi} \left(\frac{2}{\pi} I_{R1} R + 2v_\delta \right)$$

si trascura $2v_\delta$

$$v_{R1} = \frac{8}{\pi^2} R I_{R1}$$

$$\boxed{\frac{v_{R1}}{I_{R1}} = \frac{8R}{\pi^2} = R_e} \leftarrow \text{Resistenza equivalente per la 1^a armonica}$$


CIRCUITO EQUIVALENTE PER LA 1^a armonica

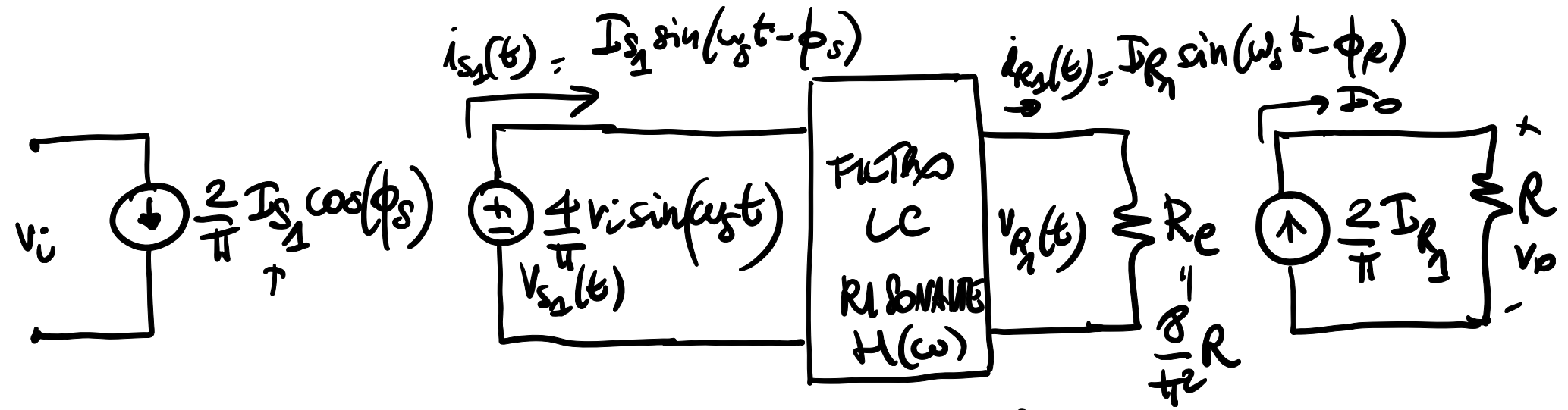

$$H(\omega) = \frac{V_{R1}(\omega)}{V_{S2}(\omega)} \text{ con carico } \underline{R_e}$$

$$\begin{aligned}
 VCR &= \frac{V_o}{v_i} = \frac{V_o}{I_o} \cdot \frac{I_o}{I_{R1}} \cdot \frac{I_{R1}}{V_{R1}} \cdot \frac{V_{R1}}{V_{S2}} \cdot \frac{V_{S2}}{v_i} = \\
 &= R \cdot \frac{2}{\pi} \cdot \frac{1}{R_e} |H(\omega_s)| \cdot \frac{4}{\pi} \cdot \underbrace{\frac{8R}{\pi^2 R_e}}_1 |H(\omega_s)| = |H(\omega_s)|
 \end{aligned}$$

FILTRO LC RISONANTE SERIE

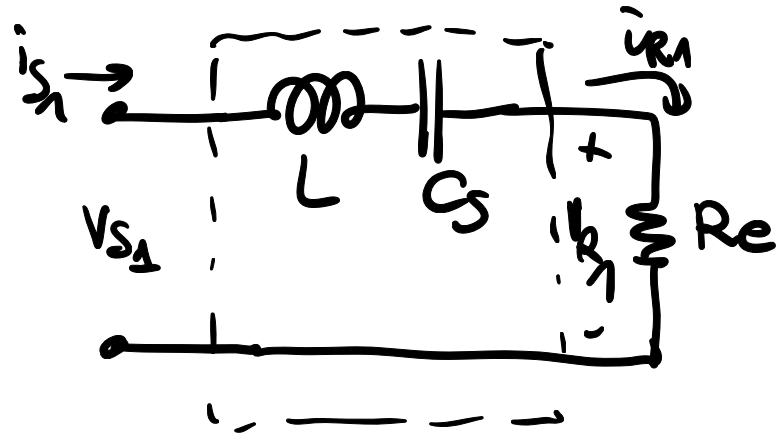

$$H(s) = \frac{R_e}{R_e + Ls + \frac{1}{C_S s}}$$

$$H(s) = \frac{R_e C_S s}{LC_S s^2 + R_e C_S s + 1}$$

$$H(s) = \frac{\frac{s}{Q\omega_0}}{\frac{\omega^2}{\omega_0^2} + \frac{s}{Q\omega_0} + 1}$$


$$\omega_0 = \frac{1}{\sqrt{LC_S}}$$

$$\frac{1}{Q\omega_0} = R_e C_S \rightarrow Q = \frac{1}{\omega_0 R_e C_S} = \frac{1}{R_e} \sqrt{\frac{L}{C_S}} \gg 1$$


$$|H(j\omega_s)| = \frac{\left| \frac{j\omega_s}{Q\omega_0} \right|}{\left| \frac{-\omega_s^2}{\omega_0^2} + \frac{j\omega_s}{Q\omega_0} + 1 \right|} = \frac{\frac{\omega_s}{Q\omega_0}}{\sqrt{\left(1 - \frac{\omega_s^2}{\omega_0^2}\right)^2 + \frac{\omega_s^2}{Q^2\omega_0^2}}}$$

Let $F = \frac{\omega_s}{\omega_0}$

$$|H(j\omega_s)| = \frac{F/Q}{\sqrt{(1-F^2)^2 + \frac{F^2}{Q^2}}} = \frac{1}{\sqrt{1 + \frac{(1-F^2)^2 Q^2}{F^2}}}$$

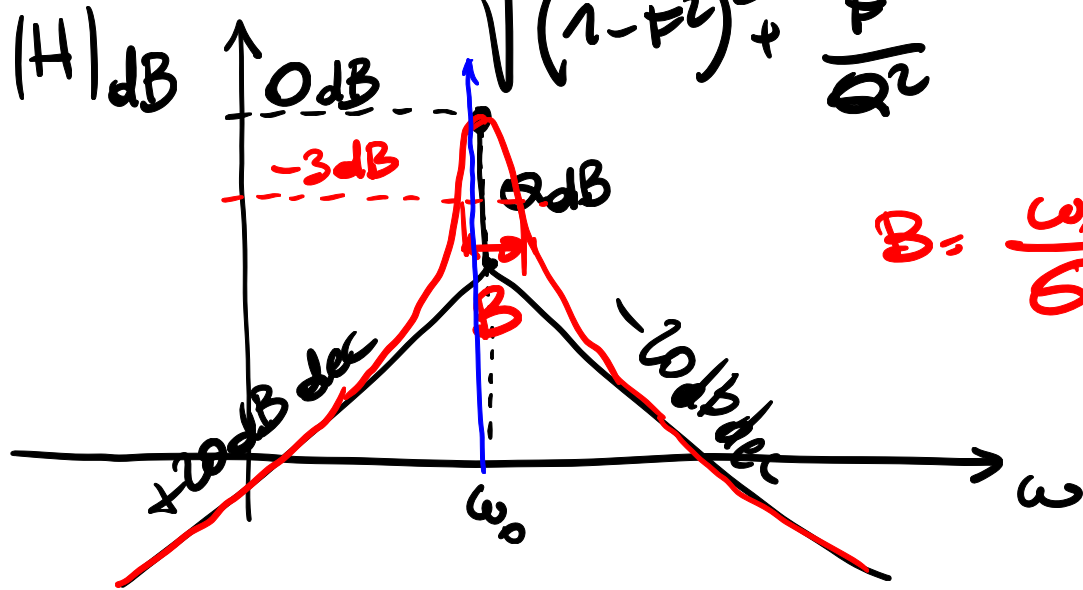

FILTRO LC RISONANTE PARALLELO (STEP UP)

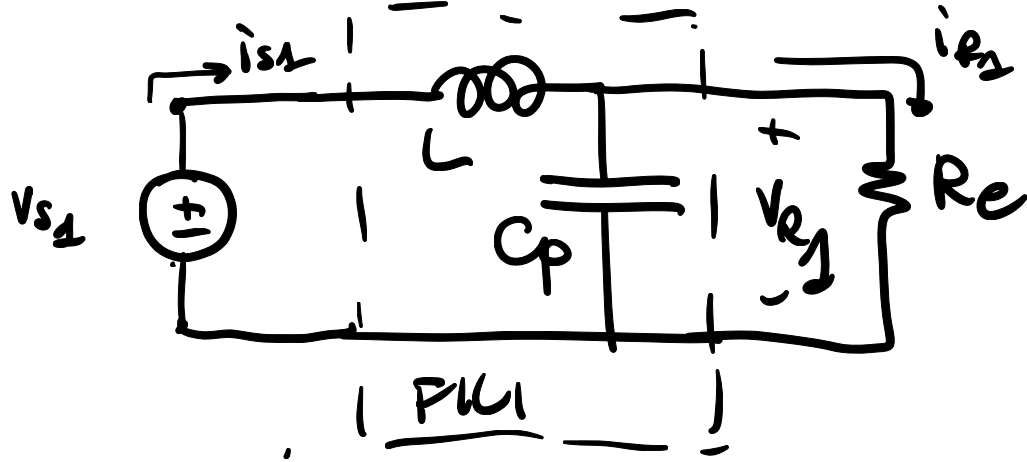

$$H(s) = \frac{V_{R_e}(s)}{V_{s_1}(s)} = \frac{R_e \parallel \frac{1}{C_p s}}{R_e \parallel \frac{1}{C_p s} + Ls}$$

$$H(s) = \frac{\frac{R_e}{1 + R_e C_p s}}{\frac{R_e}{1 + R_e C_p s} + Ls} = \frac{R_e}{L C_p R_e s^2 + Ls + R_e}$$

$$H(s) = \frac{1}{\frac{s^2}{\omega_0^2} + \frac{s}{Q\omega_0} + 1}$$

$$\omega_0 = \frac{1}{\sqrt{L C_p}}$$

$$Q = \frac{R_e}{L\omega_0} = R_e \sqrt{\frac{C_p}{L}}$$

$$H(s) = \frac{1}{L C_p s^2 + \frac{L}{R_e} s + 1}$$

$M(j\omega) / \text{dB}$

