

DC-DC Converters

DC-DC Converters

Typical uses:

- DC Power supplies
- DC Motor drive

Types of converters

- **Step-down (buck)**
- **Step-up (boost)**
- Buck-boost
- Cuk
- Full-Bridge

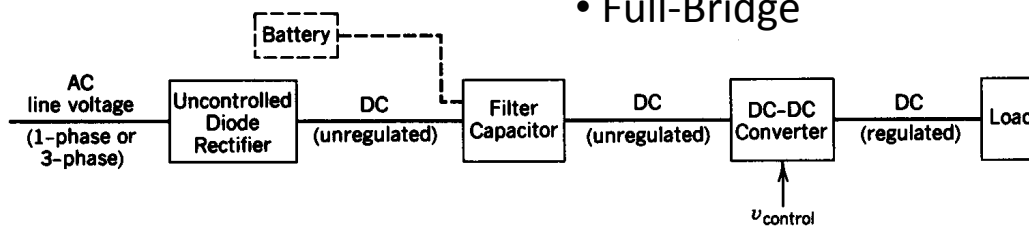


Figure 7-1 A dc-dc converter system.

Ideal concept of step-down converter with PWM* switching

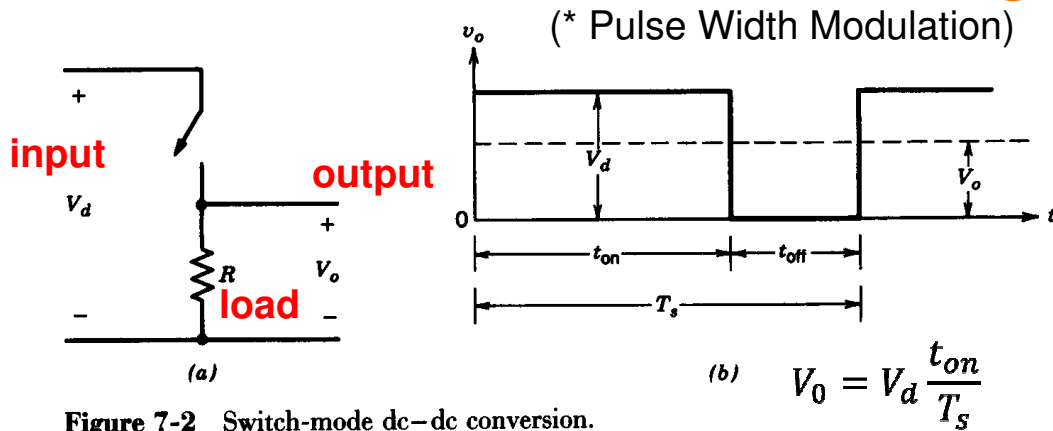


Figure 7-2 Switch-mode dc-dc conversion.

Assumptions: Switches, L, C are lossless, DC input has zero internal impedance, load is an equivalent R

This cannot work: 1. Load is inductive and can destroy switch by dissipating all stored energy, 2. output voltage must be continuous


Step-down (buck) converter

DC power supplies, DC motor drives -- $V_o < V_d$


Low-pass filter keeps output voltage constant

Note: 2nd order non dissipative filter
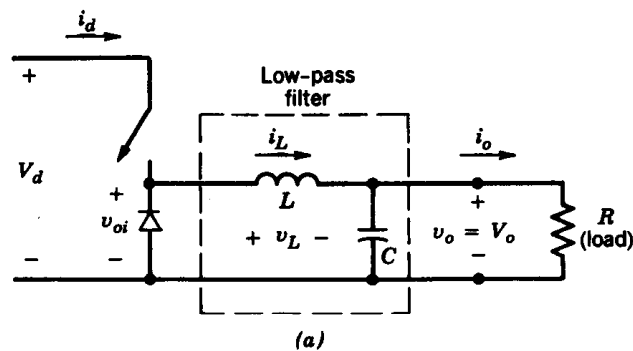
$$f_c = \frac{1}{2\pi} \frac{1}{\sqrt{LC}} \ll f_s$$



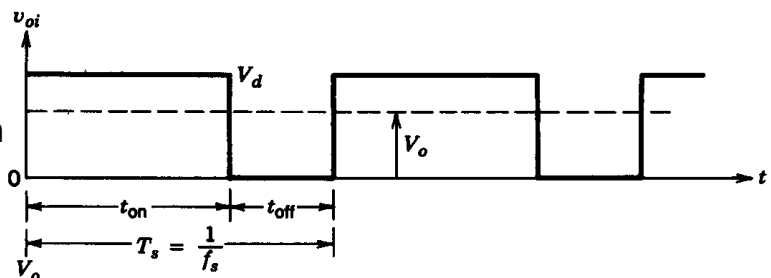Diode avoids voltage spike on switch (when switch is off, diode provides current to L)



Continuous-conduction mode

Current in L is always > 0




- t_{on} : $\frac{dI}{dt} = \frac{V_d - V_o}{L}$
- t_{off} : $\frac{dI}{dt} = -\frac{V_o}{L}$

At steady state: $I(t + T_s) = I(t)$.

Therefore

$$\frac{V_d - V_o}{L} t_{on} - \frac{V_o}{L} t_{off} = 0$$
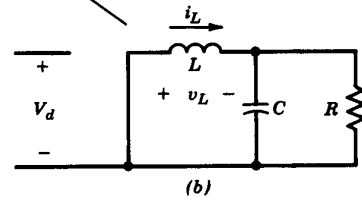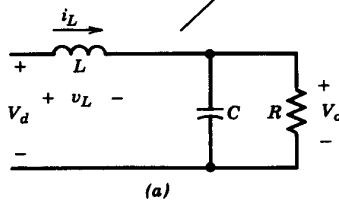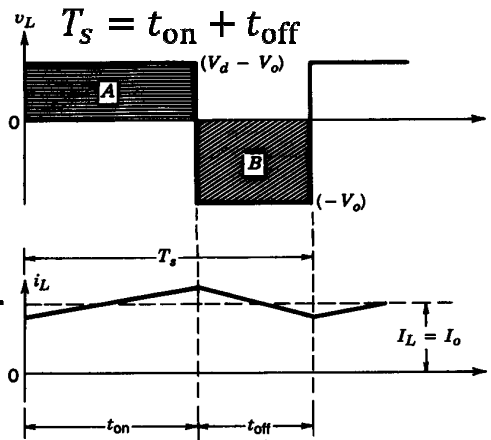
$$\frac{V_o}{V_d} = \frac{t_{on}}{T_s} = D$$



Limit of continuous conduction

If the ripple amplitude $I_{LB} \equiv \frac{I_{peak}}{2} = I_o$, the converter is at the limit of continuous conduction (i.e. $\min\{I_L\} = 0$)

$$I_{LB} \equiv \frac{I_{peak}}{2} = \frac{t_{on}(V_d - V_o)}{2L} = \frac{DT_s V_d (1 - D)}{2L} = I_{LBmax} 4D(1 - D)$$


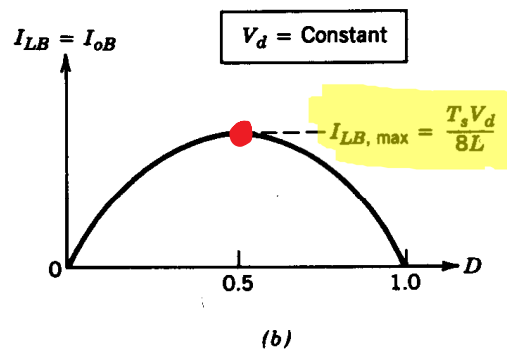
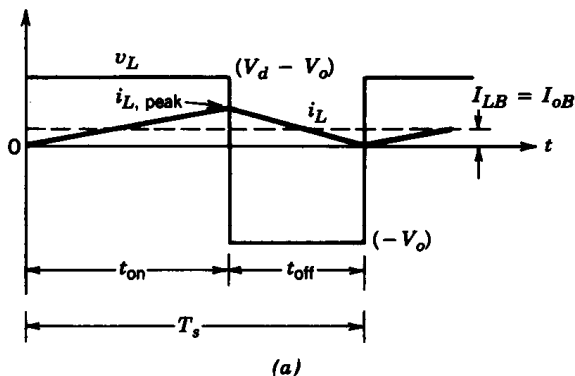


Figure 7-6 Current at the boundary of continuous–discontinuous conduction: (a) current waveform; (b) I_{LB} versus D keeping V_d constant.

Discontinuous-conduction mode with constant V_d

Motor drives
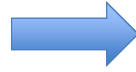
$$I_{\text{peak}} = \frac{(V_d - V_o)DT_s}{L} = \frac{V_o\Delta_1 T_s}{L}$$



$$\frac{V_o}{V_d} = \frac{D}{D + \Delta_1}$$

$$I_{\text{peak}} = \frac{V_d T_s}{L} \frac{D\Delta_1}{D + \Delta_1}$$

$$I_{\text{peak}} = 4I_{\text{LBmax}} \frac{D\Delta_1}{D + \Delta_1}$$

$$I_o T_s = \frac{I_{\text{peak}}(D + \Delta_1)T_s}{2}$$

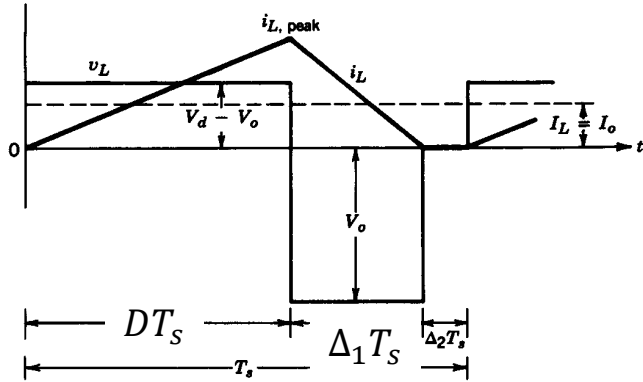


Figure 7-7 Discontinuous conduction in step-down converter.

$$I_o = 4I_{\text{LBmax}} D\Delta_1$$

$$\frac{V_o}{V_d} = \frac{D^2}{D^2 + I_o / (4I_{\text{LBmax}})}$$

Limits of continuous-discontinuous conduction (constant V_d)

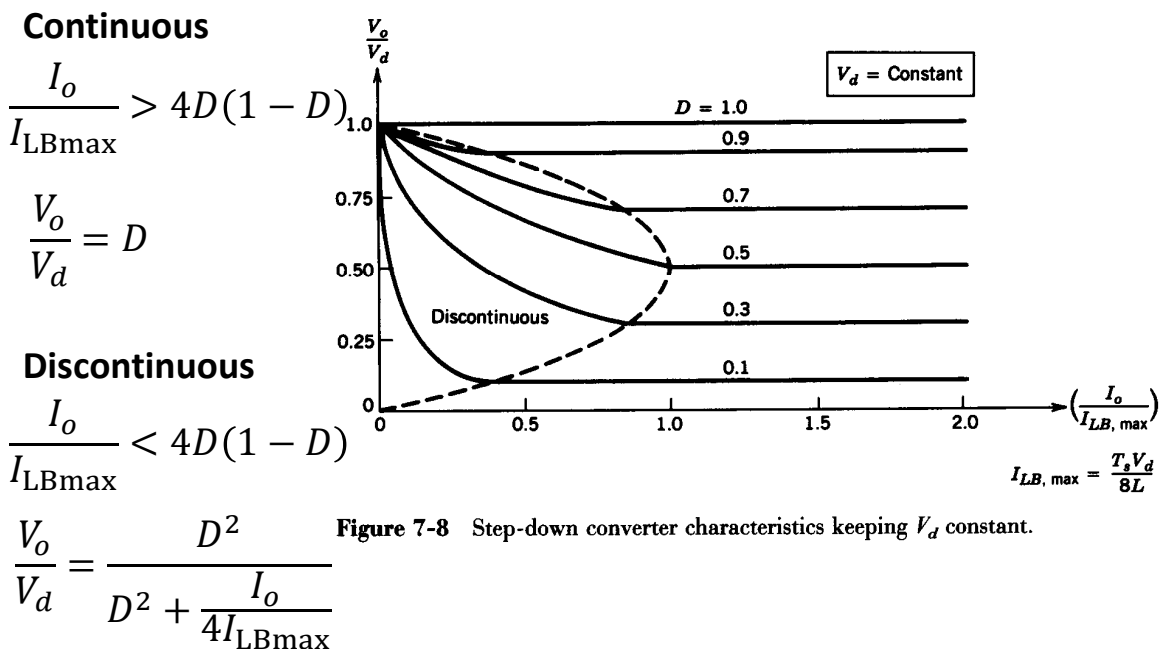


Figure 7-8 Step-down converter characteristics keeping V_d constant.

Discontinuous-conduction with constant V_o

DC voltage supply

At the limit of continuous conduction

$$I_{LB} = \frac{V_o T_s (1 - D)}{2L} = I_{LBmax} (1 - D)$$

We can write D explicitly from:

$$I_{peak} = \frac{V_o \Delta_1 T_s}{L} = 2 I_{LBmax} \Delta_1$$

$$I_o = \frac{I_{peak} (D + \Delta_1)}{2} = I_{LBmax} \Delta_1 (D + \Delta_1) \quad \frac{V_d}{V_o} = \frac{D + \Delta_1}{D}$$

$$\frac{I_o}{I_{LBmax}} = D^2 \frac{V_d}{V_o} \left(1 - \frac{V_d}{V_o}\right) \quad \Rightarrow \quad D = \left[\frac{V_o}{V_d} \frac{I_o}{I_{LBmax}} \left(1 - \frac{V_d}{V_o}\right)^{-1} \right]^{\frac{1}{2}}$$

Discontinuous-conduction with constant V_o

DC voltage supply

Continuous: $I_o > I_{LB}$

$$D > 1 - \frac{I_o}{I_{LBmax}}$$

$$D = \frac{V_o}{V_d}$$

Discontinuous: $I_o < I_{LB}$

$$D < 1 - \frac{I_o}{I_{LBmax}}$$

$$D = \left[\frac{V_o}{V_d} \frac{I_o}{I_{LBmax}} \left(1 - \frac{V_d}{V_o}\right)^{-1} \right]^{\frac{1}{2}}$$


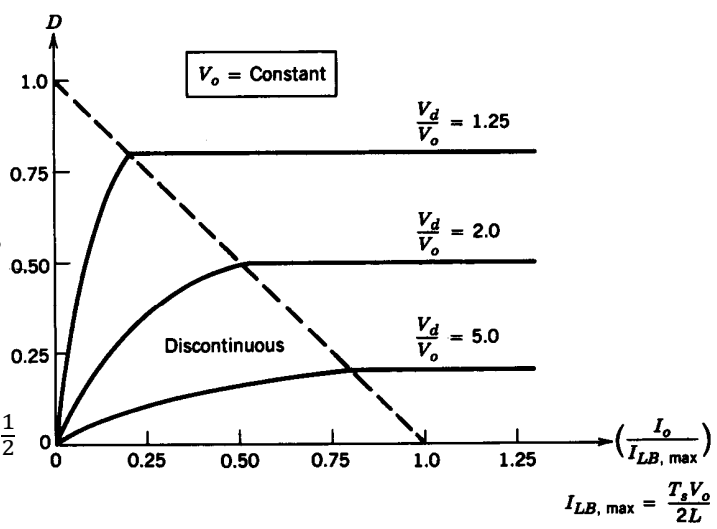


Figure 7-9 Step-down converter characteristics keeping V_o constant.

Output voltage ripple

First order calculation:

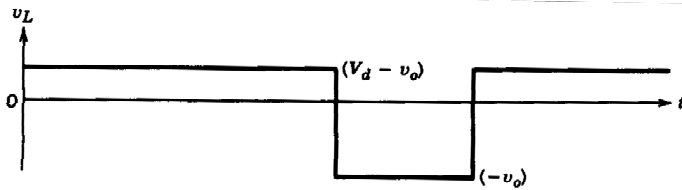The average i_L flows in the load, and the ripple component in C.



Additional charge:


$$\Delta Q = \frac{1}{2} \frac{\Delta I_L}{2} \frac{T_s}{2}$$

Current ripple:

$$\Delta I_L = (V_o/L)(1 - D)T_s$$

Voltage ripple:
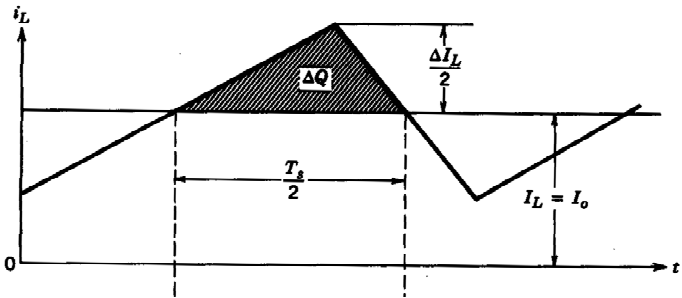
$$\Delta V_o = \frac{\Delta Q}{C} = \frac{V_o}{8LC} T_s^2 (1 - D)$$



$$\frac{\Delta V_o}{V_o} = \frac{\pi^2}{2} (1 - D) \frac{f_c^2}{f_s^2}$$


Step-up (boost) converter

- DC power supplies
- Regenerative braking of DC motors

Output voltage always larger than the input

Switch on → diode off, output isolated, L accumulates energy from input

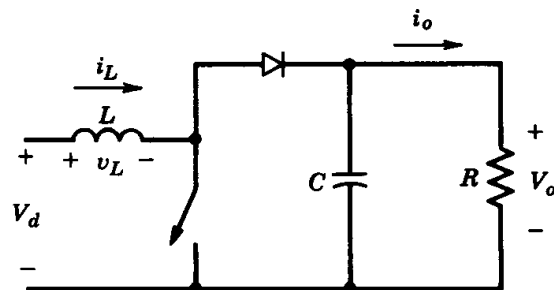Switch off → diode on, load receives energy from input and from L



Continuous-conduction mode

Periodic conditions:

$$\frac{t_{on}V_d}{L} + \frac{t_{off}(V_d - V_o)}{L} = 0$$

if $t_{on} = DT_s$ and


$$t_{off} = (1 - D)T_s$$

$$T_s V_d + T_s(1 - D)V_o = 0$$


$$\frac{V_o}{V_d} = \frac{1}{1 - D}$$

No losses:

$$V_o I_o = V_d I_d$$

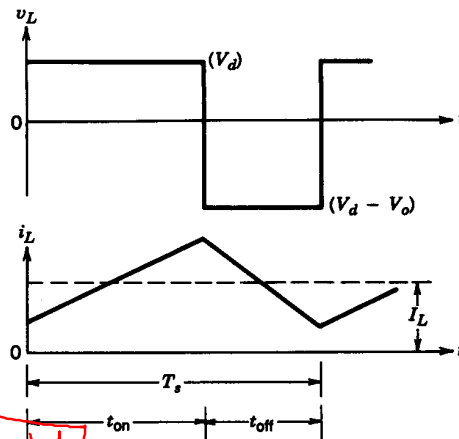

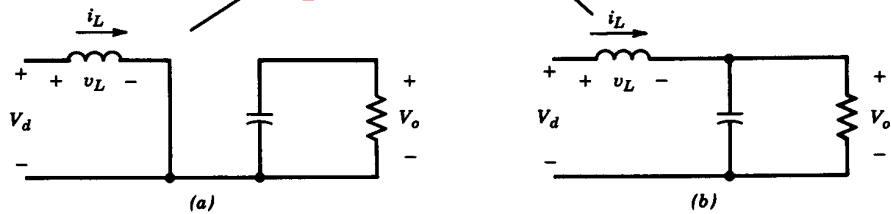$\frac{V_d}{V_o} = 1 - D \Rightarrow D = 1 - \frac{V_d}{V_o}$



Continuous-discontinuous boundary


Average current in L

= ripple :

$$I_{LB} = \frac{V_d t_{on}}{2L} = \frac{V_o(1 - D)T_s D}{2L}$$

Average output current at the limit:
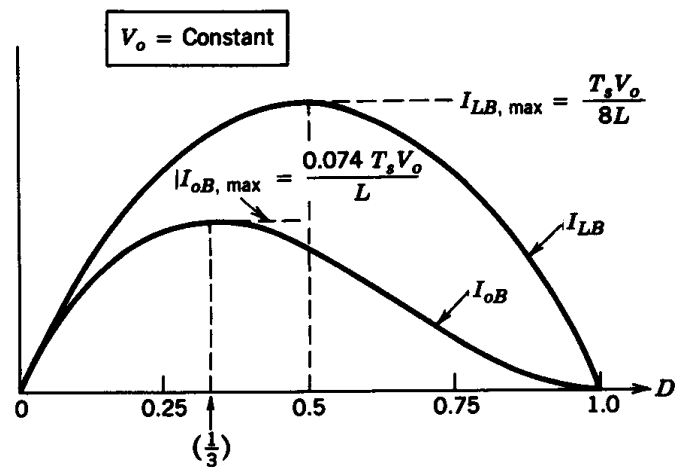
$$I_{oB} = I_{LB}(1 - D) = \frac{V_o T_s (1 - D)^2 D}{2L}$$



$$I_{LB} \text{ is max if } D=0.5 \rightarrow I_{LBmax} = \frac{V_o T_s}{8L}$$

$$I_{oB} \text{ is max if } D=1/3 \rightarrow I_{oBmax} = \frac{2V_o T_s}{27L} \rightarrow I_{oB} = \frac{27}{4} (1 - D)^2 D I_{oBmax}$$

Discontinuous conduction mode (constant V_o)

⊗ Periodic conditions:

$$\frac{DT_s V_d}{L} + \frac{\Delta_1 T_s (V_d - V_o)}{L} = 0$$

$$\frac{V_o}{V_d} = 1 + \frac{D}{\Delta_1} = \frac{I_d}{I_o}$$

⊗ Average current in L


$$I_d T_s = \frac{DT_s V_d}{L} \frac{(D + \Delta_1) T_s}{2}$$

Average output current

$$I_o = I_d \frac{\Delta_1}{D + \Delta_1} = \frac{T_s V_d}{2L} D \Delta_1$$

$$= \frac{27}{4} I_{oBmax} \frac{V_d}{V_o} D^2 \frac{V_d}{V_o - V_d}$$
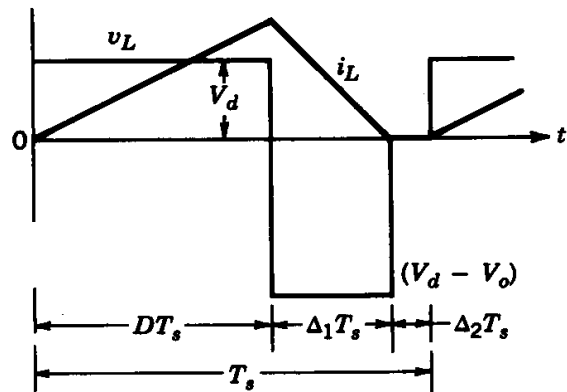
$$\rightarrow D = \left[\frac{4}{27} \frac{V_o}{V_d} \left(\frac{V_o}{V_d} - 1 \right) \frac{I_o}{I_{oBmax}} \right]^{\frac{1}{2}}$$



Continuous-discontinuous mode (constant V_o)

Continuous mode:

$$I_o > I_{oB}$$

$$= I_{oBmax} \frac{27(1-D)^2 D}{4}$$

$$D = 1 - \frac{V_d}{V_o}$$

Discontinuous mode:

$$I_o < I_{oB}$$

$$D = \left[\frac{4}{27} \frac{V_o}{V_d} \left(\frac{V_o}{V_d} - 1 \right) \frac{I_o}{I_{oBmax}} \right]^{\frac{1}{2}}$$

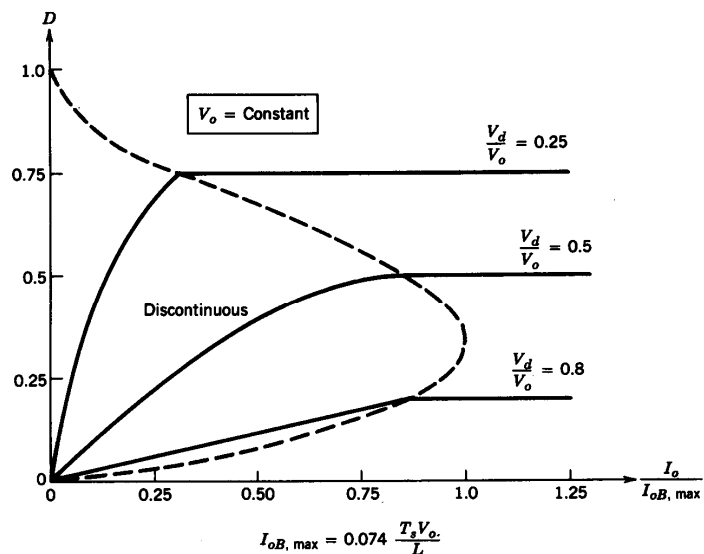


Figure 7-15 Step-up converter characteristics keeping V_o constant.

Losses and ripple

Losses: inductor, capacitor, switch, diode

Ripple: first order assumption: when the switch is on the C is discharged through the load

$$\Delta V_o = \frac{\Delta Q}{C} = \frac{I_o DT_s}{C} = \frac{V_o DT_s}{RC}$$


$$\frac{\Delta V_o}{V_o} = D \frac{T_s}{\tau}$$

Buck-boost converter

Negative DC power supply


Switch on: inductance accumulates energy, diode off, C supplies the load

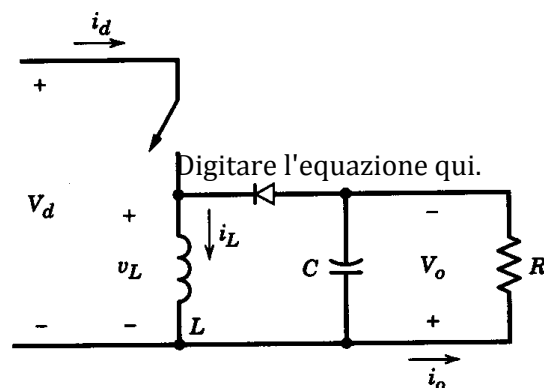Switch off: diode on, inductance transfers energy to the capacitance and to the load



Periodic conditions in continuous conduction mode:
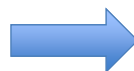
$$\frac{DT_s V_d}{L} - \frac{V_o(1-D)T_s}{L} = 0$$



$$\frac{V_o}{V_d} = \frac{D}{1-D} = \frac{I_d}{I_o}$$

$$I_L = I_o + I_d = \frac{I_o}{1-D}$$

Continuous-discontinuous boundary

Current in L at the boundary



$$I_{LB} = \frac{DT_s V_d}{2L}$$

$$I_{LB} = I_{LBmax}(1 - D)$$

Output current at the boundary:

$$I_{oB} = I_{LB}(1 - D) = \frac{T_s V_o}{2L} (1 - D)^2$$

$$I_{oB} = I_{oBmax}(1 - D)^2$$

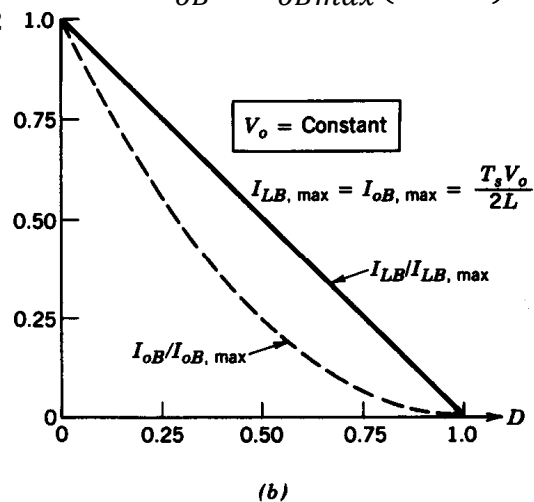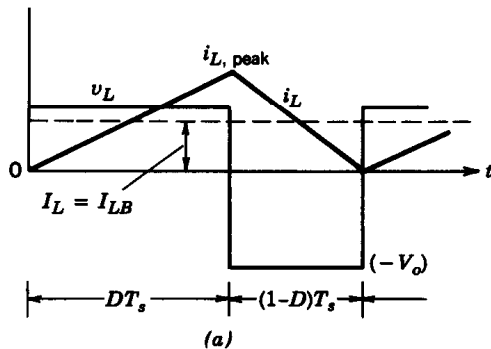

Discontinuous conduction

Periodic conditions:

$$\frac{DV_d T_s}{L} - \frac{V_o \Delta_1 T_s}{L} = 0$$

$$\frac{V_o}{V_d} = \frac{D}{\Delta_1} = \frac{I_d}{I_o}$$

Average current in L:

$$I_L T_s = \frac{V_d D T_s}{L} \frac{(D + \Delta_1) T_s}{2}$$

Therefore:

$$I_L = I_o \left(1 + \frac{D}{\Delta_1} \right) = \frac{V_d T_s}{2L} D (D + \Delta_1)$$

$$\frac{I_o}{I_{oBmax}} = D \Delta_1 \frac{V_d}{V_o} = D^2 \left(\frac{V_d}{V_o} \right)^2 \rightarrow D = \frac{V_o}{V_d} \sqrt{\frac{I_o}{I_{oBmax}}}$$

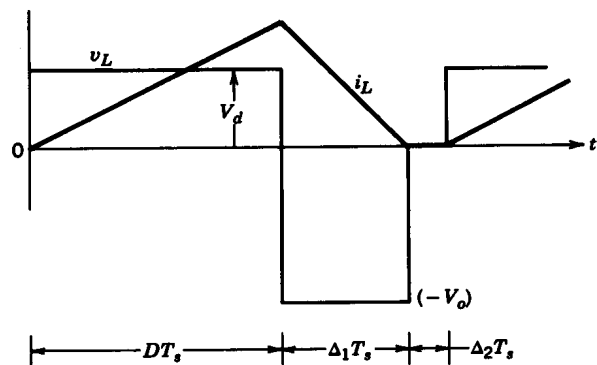


Figure 7-21 Buck-boost converter waveforms in a discontinuous-conduction mode.

Continuous-discontinuous mode

Continuous operation

$$I_o > I_{oB} = I_{oBmax}(1 - D)^2$$

$$D = \frac{V_o}{V_d - V_o}$$

Discontinuous operation

$$I_o < I_{oB}$$

$$D = \frac{V_o}{V_d} \sqrt{\frac{I_o}{I_{oBmax}}}$$

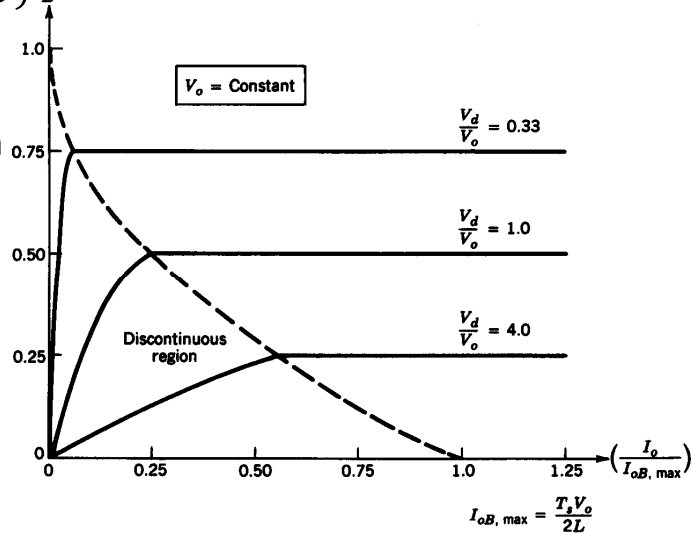


Figure 7-22 Buck-boost converter characteristics keeping V_o constant.

Output voltage ripple

When the switch is ON, C is discharged through the load

$$\Delta V_o = \frac{\Delta Q}{C} = \frac{DT_s V_o}{RC} \rightarrow \frac{\Delta V_o}{V_o} = D \frac{T_s}{\tau}$$

Cuk DC-DC converter

Negative DC power supply

DC analysis: $V_{C1} = V_d + V_o$ note: ($V_{C1} > V_d$)

Assumption: Large C_1 (Voltage almost constant)

Switch OFF: C_1 is charged through L_1 and the input, Diode ON, L_2 supplies energy to R (currents in L_1 and L_2 decrease)

Switch ON: L_1 receives energy, Diode OFF, C_1 supplies current to R , C_1 gives energy to L_2 (currents in L_1 and L_2 increase)

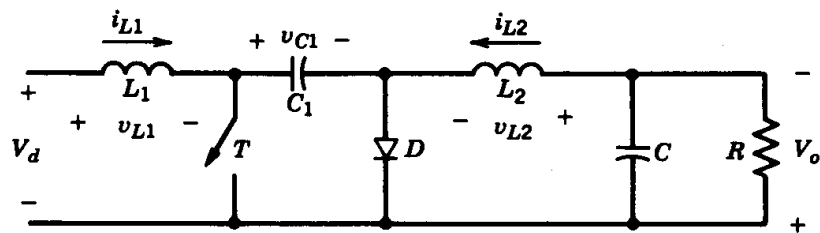


Figure 7-25 Cúk converter.

Cuk

Periodic conditions in L1

$$V_d DT_s + (1 - D)T_s(V_d - V_{C1}) = 0$$

$$V_{C1} = \frac{V_d}{1 - D}$$

Periodic conditions in L2

$$(V_{C1} - V_o)DT_s - V_o(1 - D)T_s = 0$$

$$V_{C1} = \frac{V_o}{D}$$

Therefore

$$\frac{V_o}{V_d} = \frac{D}{1 - D}$$

Pro: currents

in L_1 and L_2 ripple free

Con: C_1 must be large

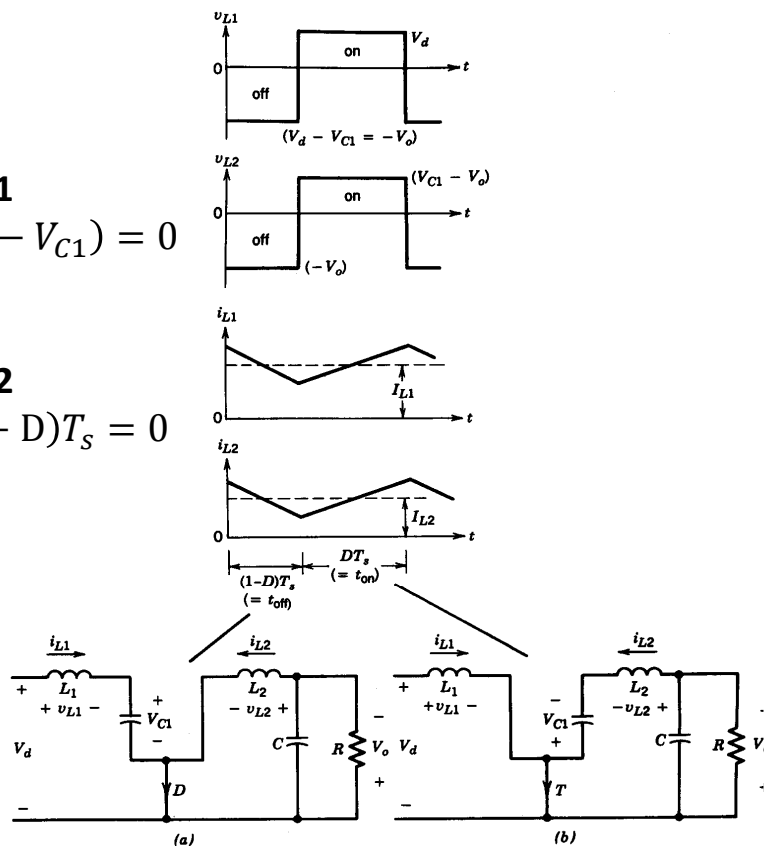


Figure 7-26 Cúk converter waveforms: (a) switch off; (b) switch on.

Full bridge DC-DC converter

When switch TA+ is on:

$i_o > 0$: i_o through TA+

$i_o < 0$: i_o through DA+

$$V_{AN} = V_d \text{duty cycle}(TA^+)$$

When switch TB+ is on:

$i_o < 0$: i_o through TB+

$i_o > 0$: i_o through DB+

$$V_{BN} = V_d \text{duty cycle}(TB^+)$$

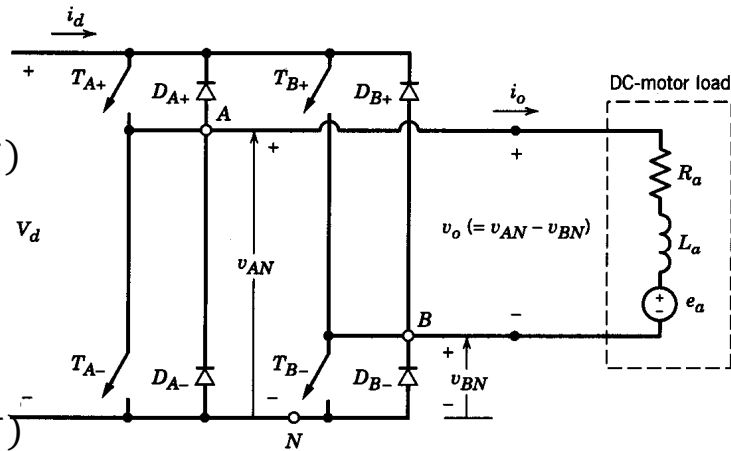



Figure 7-27 Full-bridge dc-dc converter.

$$V_o = V_{AN} - V_{BN}$$

Four quadrant operation

on V_o, I_o

PWM with bipolar voltage switching

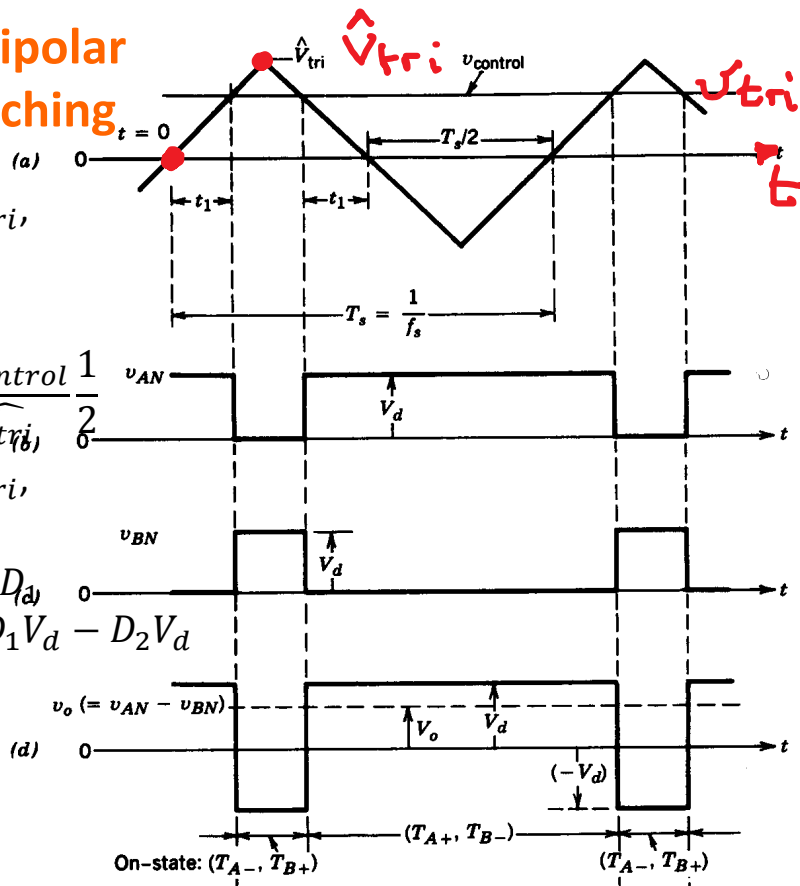

When $v_{control} > v_{tri}$,

TA+ and TB- are ON

Duty cycle

$$D_1 = \frac{1}{2} + \frac{v_{control}}{\widehat{V}_{tri}} \frac{1}{2}$$

When $v_{control} < v_{tri}$,

TA- and TB+ are ON

$$D_2 = 1 - D_1$$

$$V_o = V_{AN} - V_{BN} = D_1 V_d - D_2 V_d$$

$$= (2D_1 - 1)V_d$$

$$= \frac{V_d}{\widehat{V}_{tri}} v_{control}$$

PWM with unipolar voltage switching

When $v_{control} > v_{tri}$,
 TA+ and TB- are ON


Duty cycle

$$D_1 = \frac{1}{2} + \frac{v_{control}}{\widehat{V}_{tri}} \frac{1}{2}$$



When $-v_{control} < v_{tri}$,
 TA- and TB+ are ON



$$D_2 = 1 - D_1$$
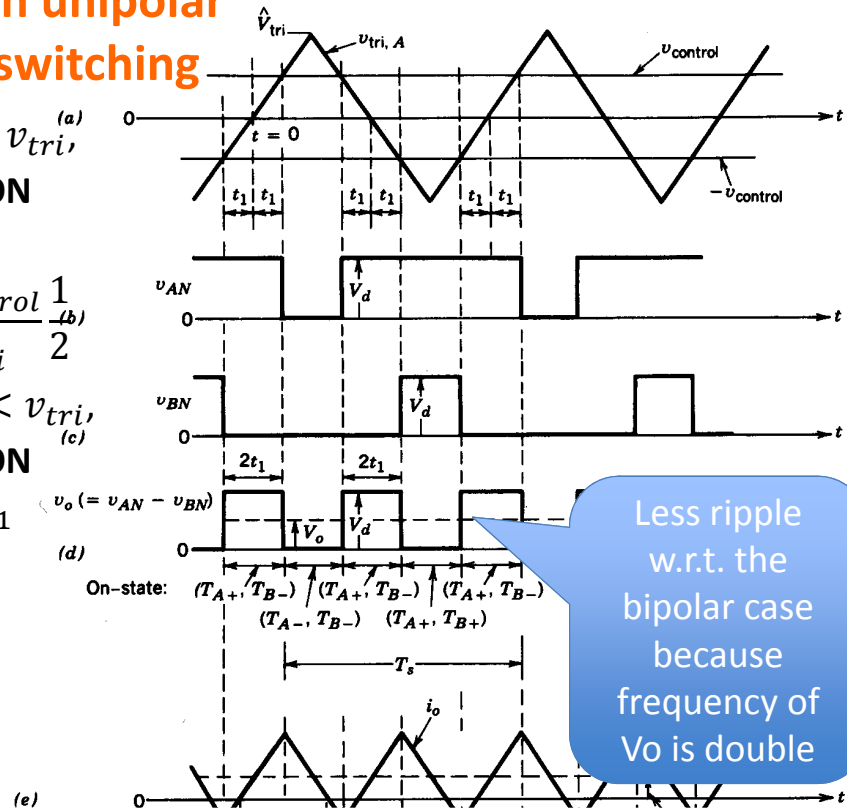
$$\begin{aligned} V_o &= V_{AN} - V_{BN} \\ &= D_1 V_d - D_2 V_d \\ &= (2D_1 - 1)V_d \\ &= \frac{V_d}{\widehat{V}_{tri}} v_{control} \end{aligned}$$



PWM signal generation

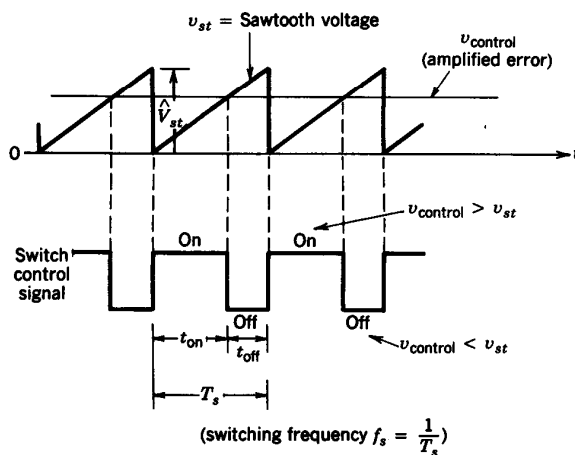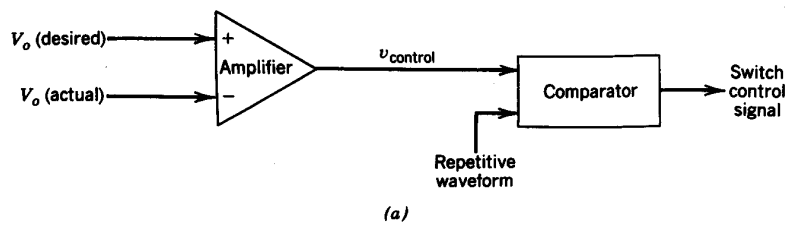

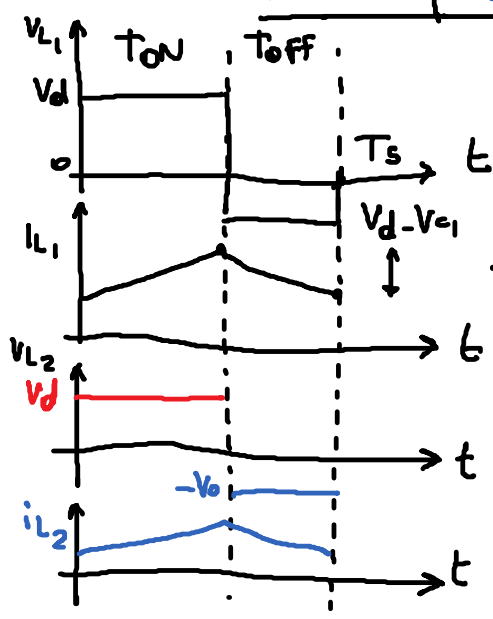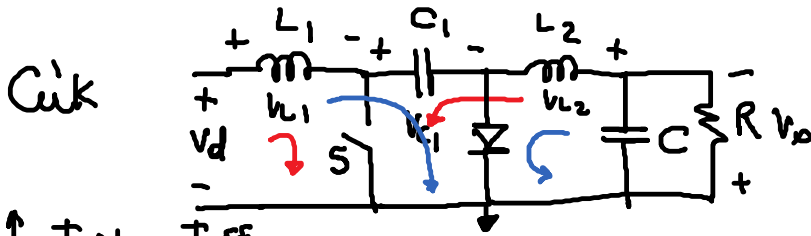

$$V_{C1} = V_d + V_o$$

$$t_{on} = D T_s$$



$$\Delta I_{L1} = t_{on} \frac{V_d}{L_1} = t_{off} \frac{V_{C1} - V_d}{L_1} = \frac{t_{off} V_o}{L_1}$$

$$D V_d = (1 - D) V_o$$

$$V_o = \frac{D}{1 - D} V_d$$

(buckboost) PRO: corrente continua dall'incontro
 CONTROL: C_1 grande

Full Bridge DCDC Converter (4Q)

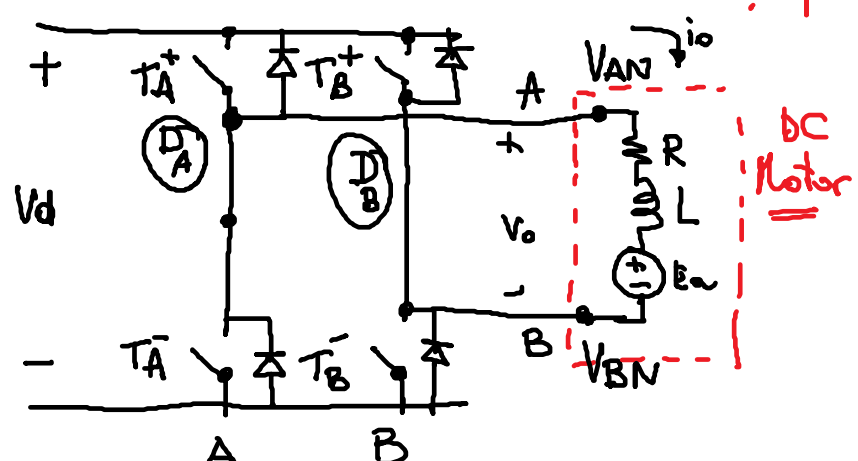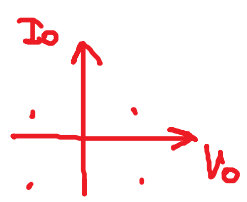


$$D_A: \text{duty cycle of } T_{A^+} \quad V_{AN} = D_1 V_d$$

$$D_B: \text{duty cycle of } T_{B^+} \quad V_{BN} = D_2 V_d$$

$$V_o = V_{AN} - V_{BN} = (D_1 - D_2) V_d$$

Control: PWM → bipolar voltage
 → unipolar voltage

PWM with bipolar voltage

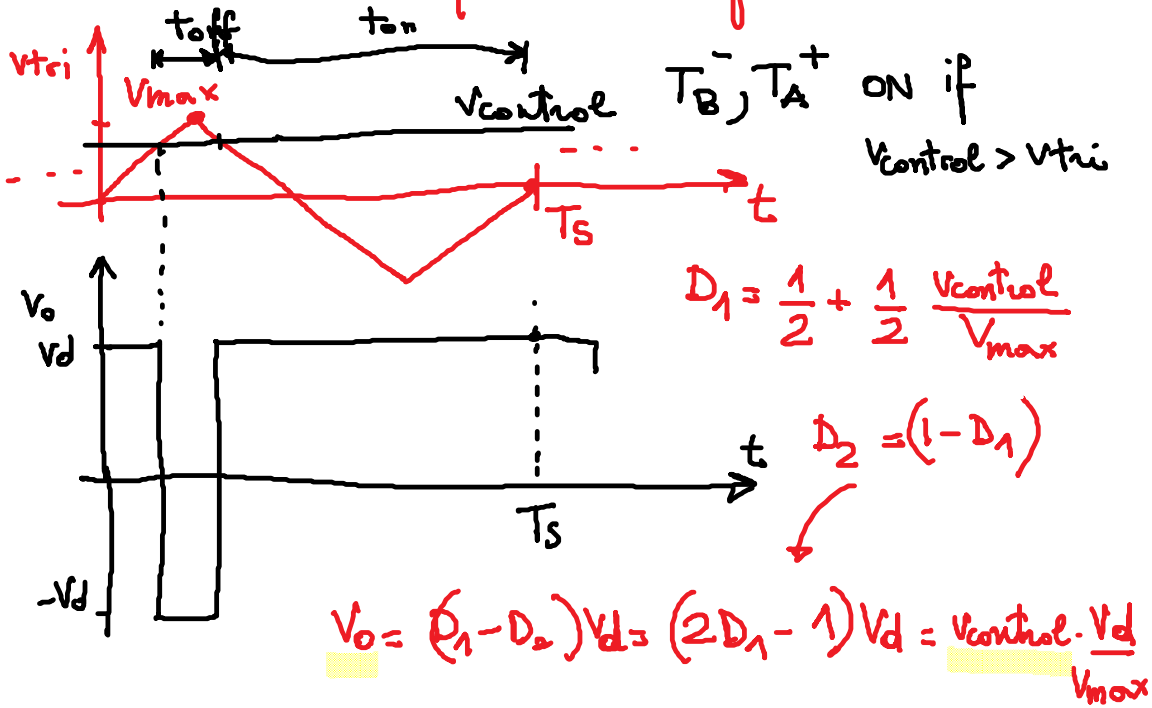

PWM with unipolar voltage

