
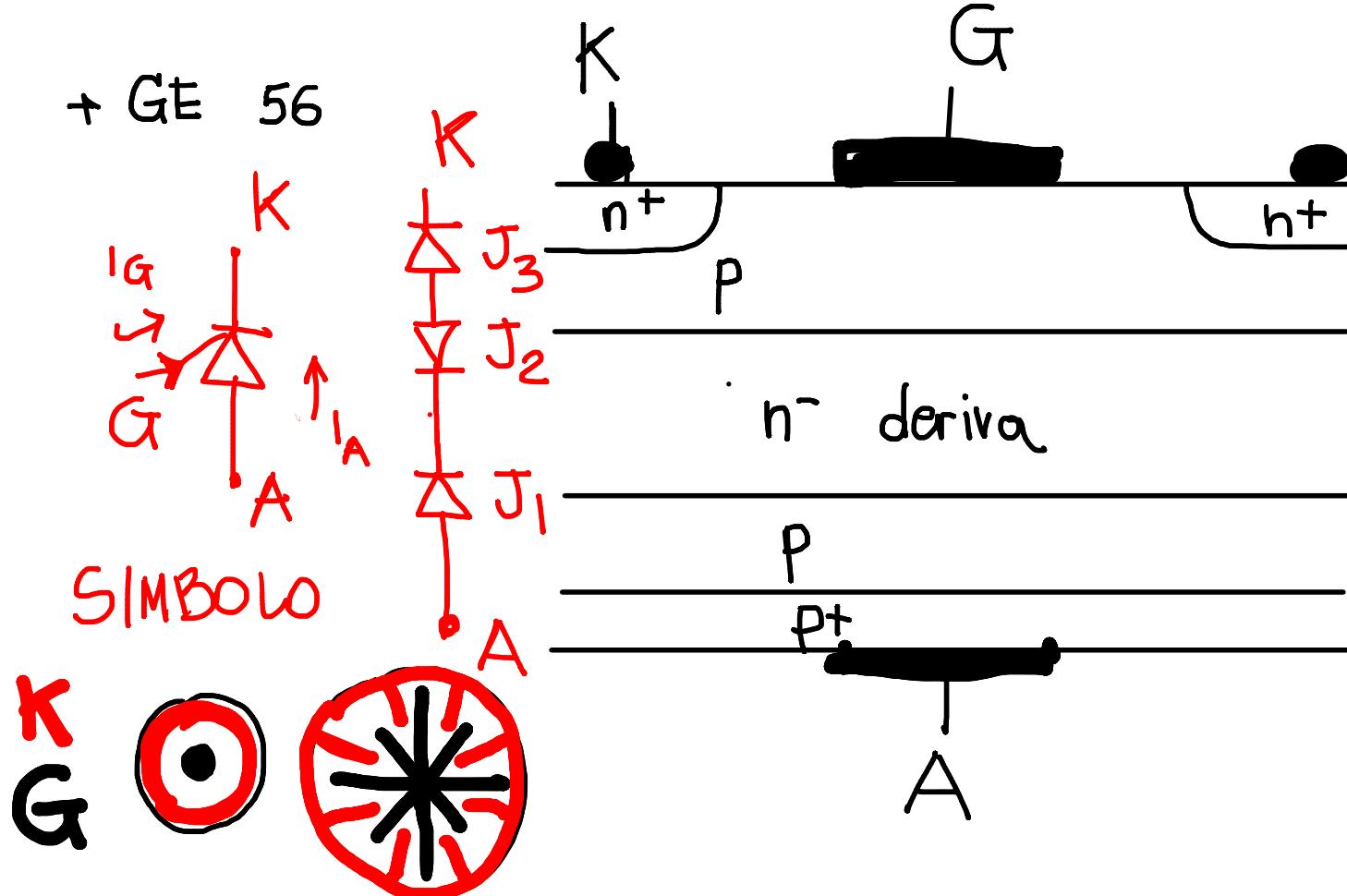


# TIRISTORI

SCR - Silicon Controlled Rectifier

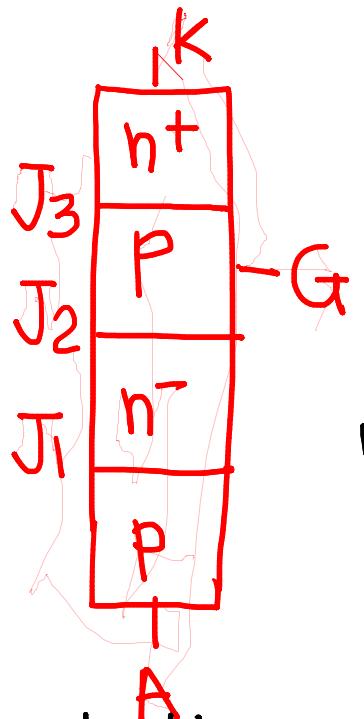




2 stati

OFF (blocco)

ON i 2 BJT in sat.

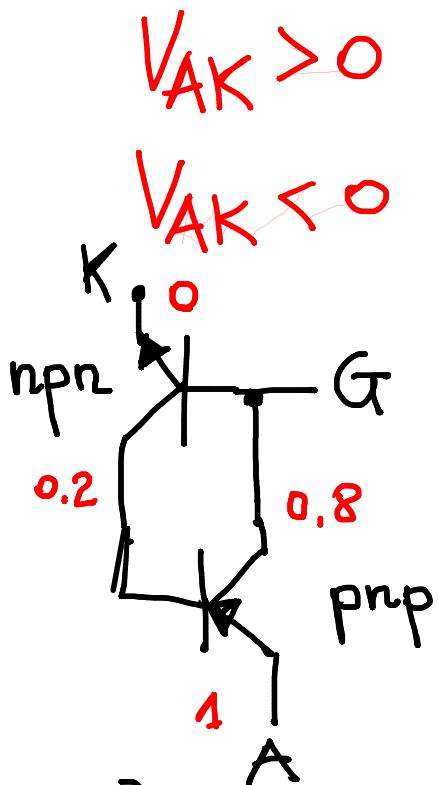


$$V_{AK} > 0$$

$$V_{AK} < 0$$

$J_2$  Sopporta la V  
 $J_1$  " "

$$\alpha_{npn} \approx 1 (0,9)$$

$$\alpha_{pnp} < 0,1$$

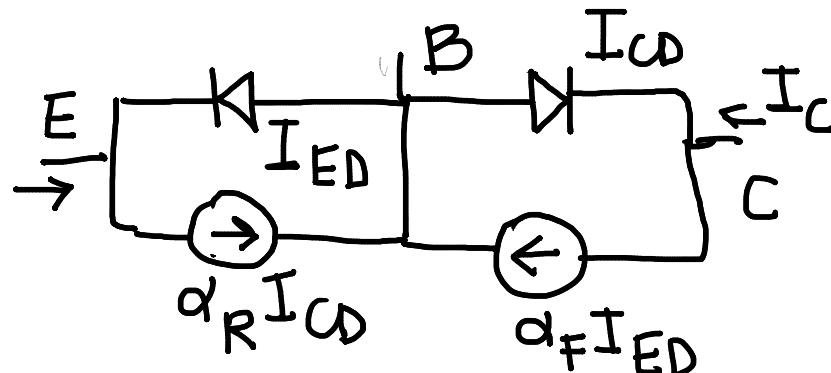

Modello  
di Ebers-Möll


z.a.d

$$I_{CD} = -I_{CS}$$

$$I_E = -I_{ED} - \alpha_R I_{CS}$$

$$I_C = \alpha_F I_{ED} + I_{CS} = -\alpha_F I_E + I_{CO}$$

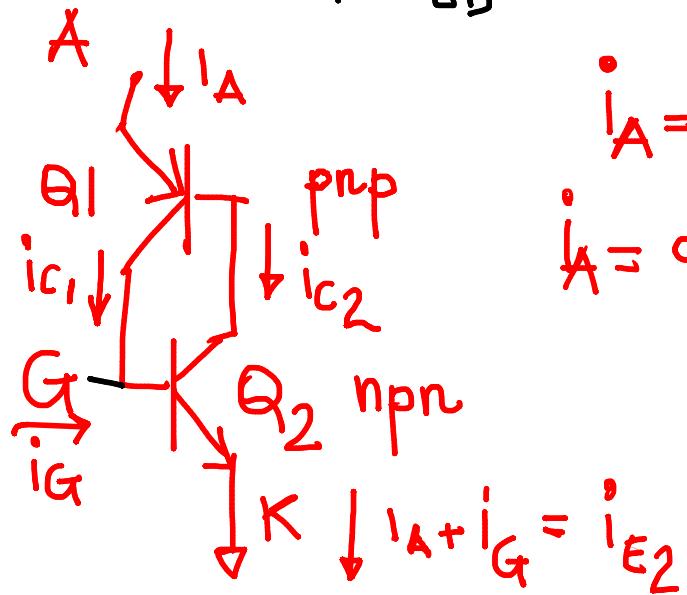
$$\boxed{I_{CO} = (1 - \alpha_F \alpha_R) I_{CS}}$$



$$i_A = i_{C1} + i_{C2} = i_{E1}$$

$$i_A = \alpha_{PnP} i_{E1} - I_{CO1} + \alpha_{NPN} (i_A + i_G) + I_{CO2}$$
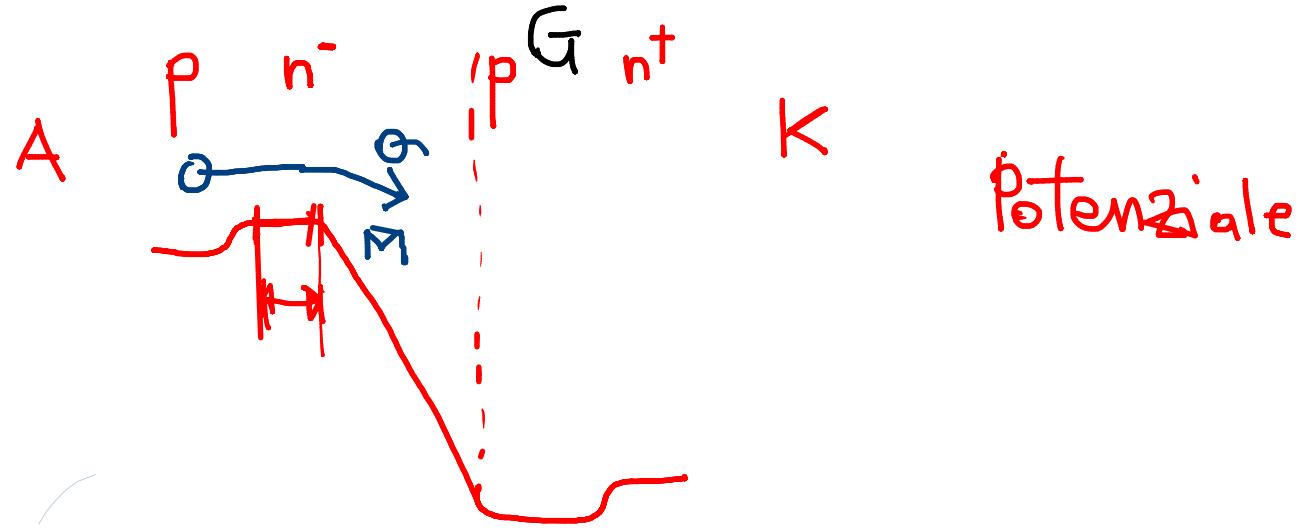
$$i_A = \frac{i_A + \alpha_{NPN} i_G - I_{CO1} + I_{CO2}}{(1 - \alpha_{PnP} - \alpha_{NPN})}$$



Se Aumenta  $V_{AK}$

- 1) si può avere un inizio di moltiplicazione che aumenta  $\alpha_{pnp}$   $\rightarrow$



2) aumenta lo svuotamento della regione di derivazione

$i_G \uparrow i_{C_2} \uparrow M \uparrow \alpha_{pnp} \uparrow \rightarrow$  si sposta la base del pnp  $\uparrow \alpha_{pnp}$


$$i_A = \frac{+\alpha_{npp} i_G - I_{C01} + I_{C02}}{(1 - \alpha_{ppp} - \alpha_{npp})}$$


$\alpha_{ppp} + \alpha_{npp} < 1$  OFF  
ben minore

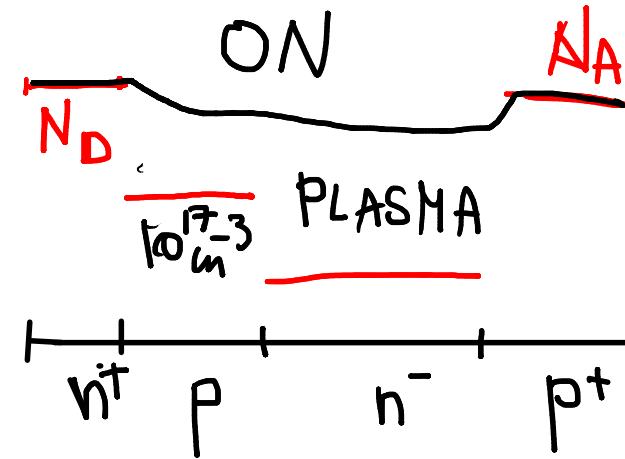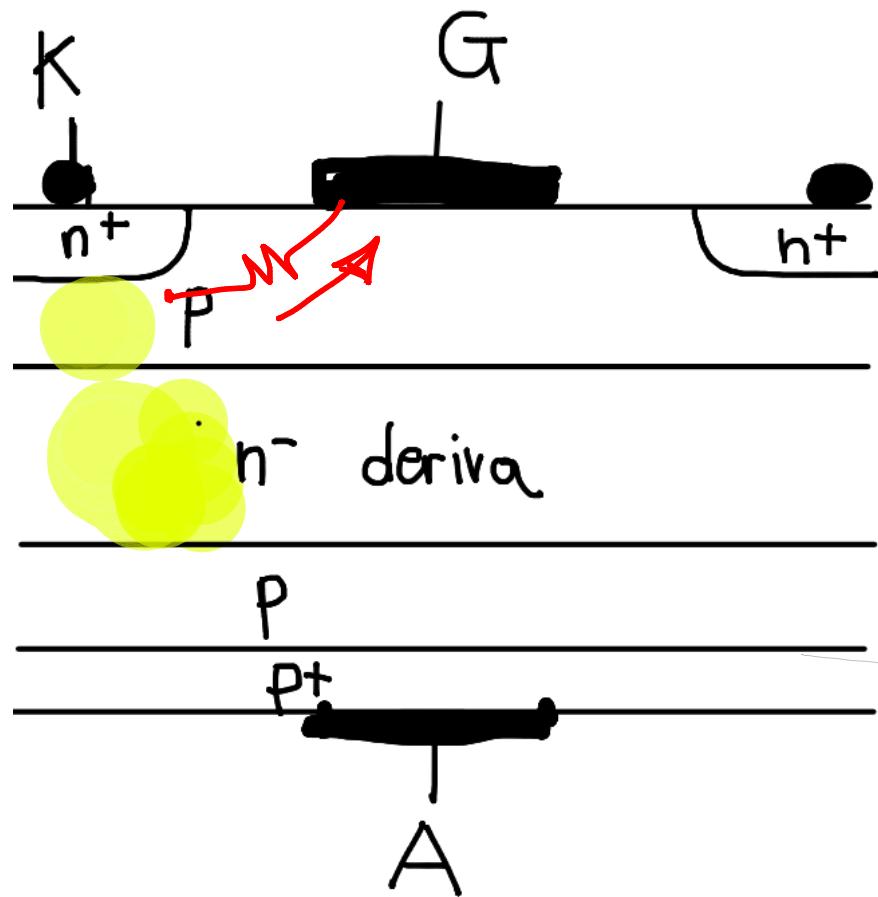$\alpha_{ppp} + \alpha_{npp} \approx 1$  ON



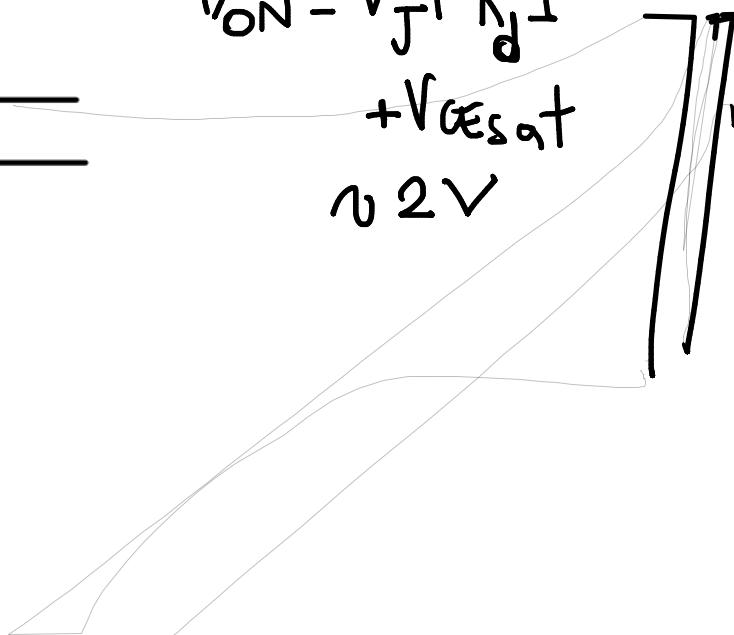
$$V_{ON} = V_J + R_d I + V_{CESAT} \approx 2V$$



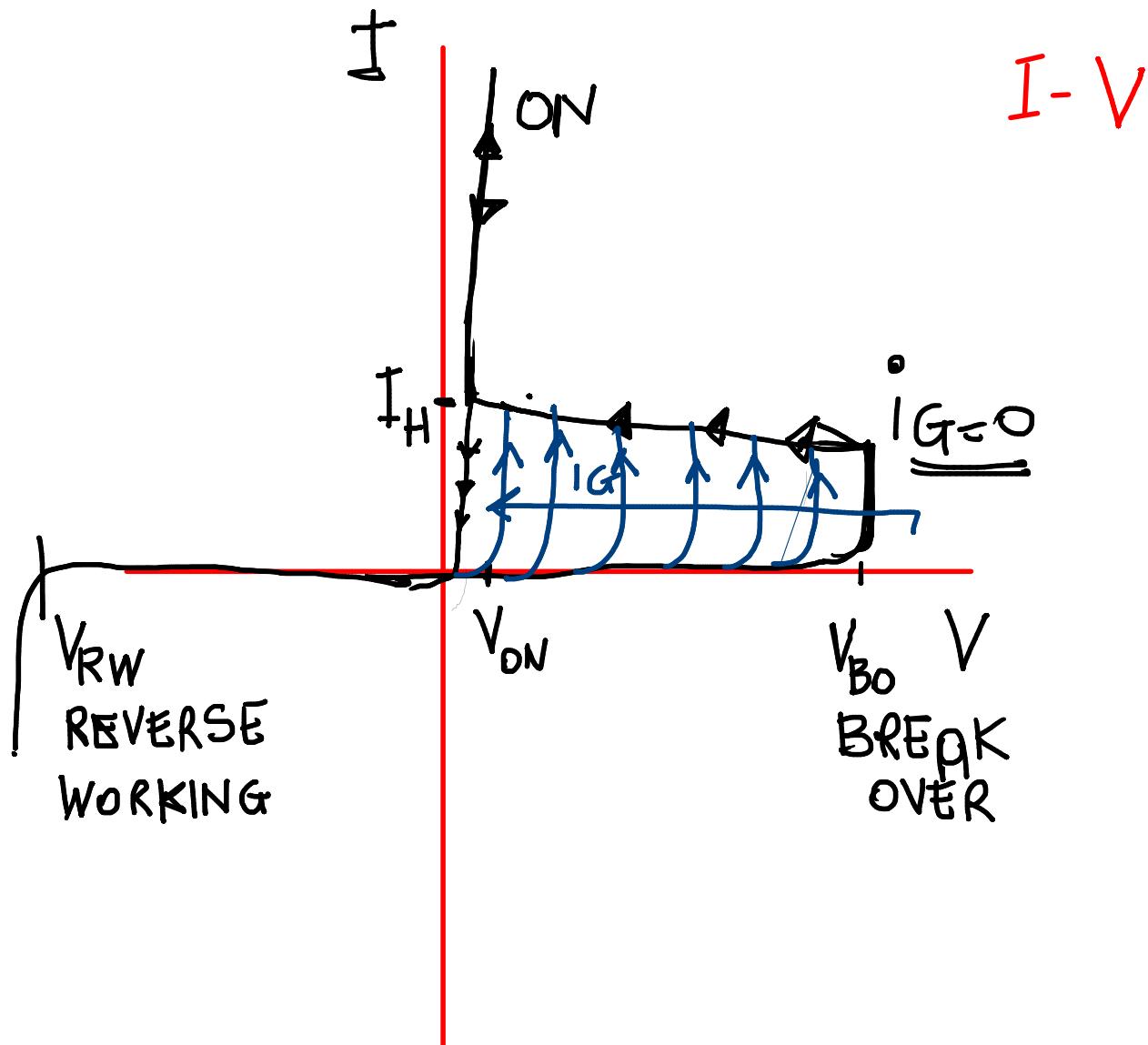

## Transitorio di accensione

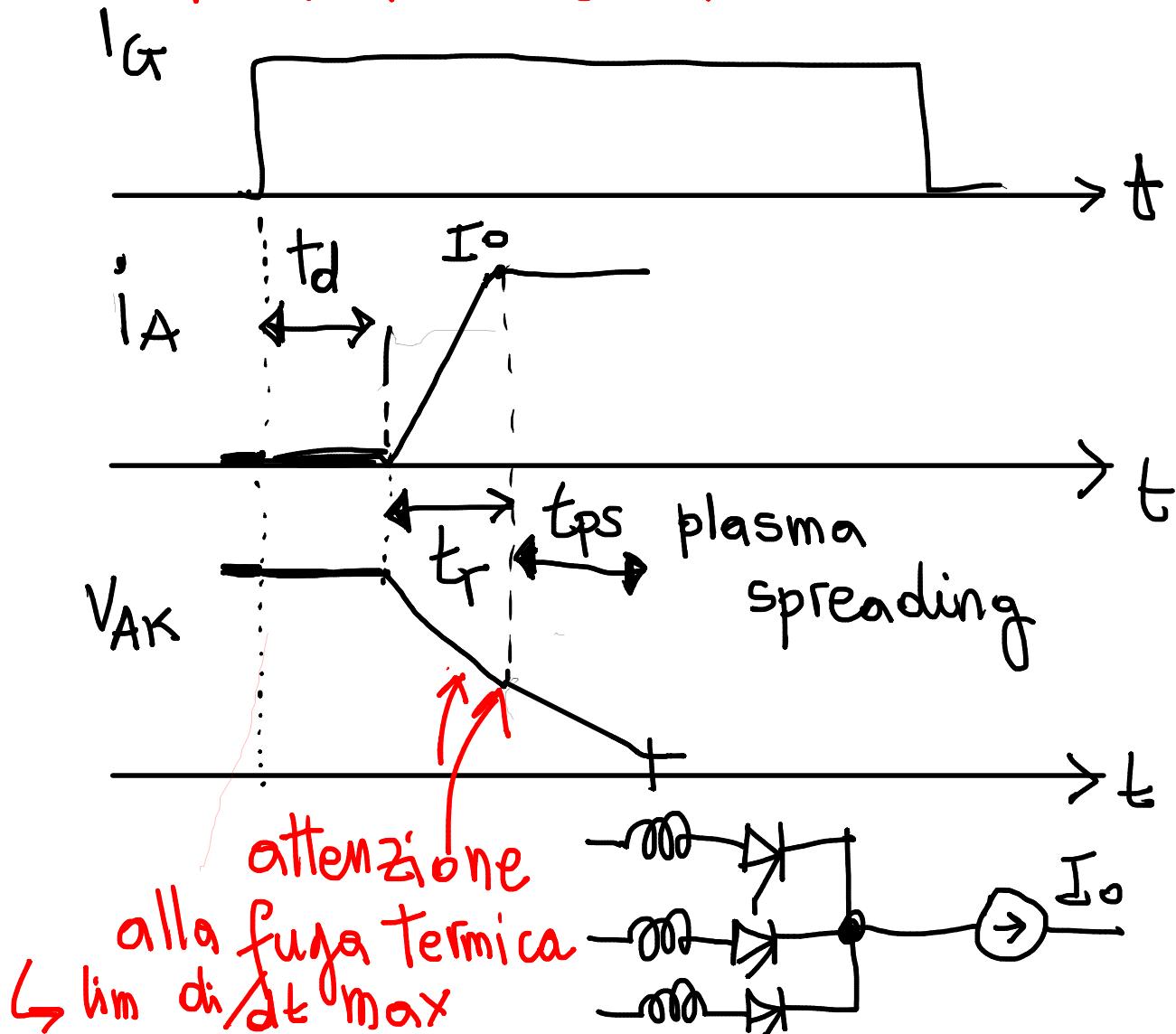

## Transitorio di spegnimento

