

DC-DC Converters

Typical uses:

- DC Power supplies
- DC Motor drives
- Portable Electronics

Types of converters

- **Step-down (buck)**
- **Step-up (boost)**
- Buck-boost
- Cuk
- Full-Bridge

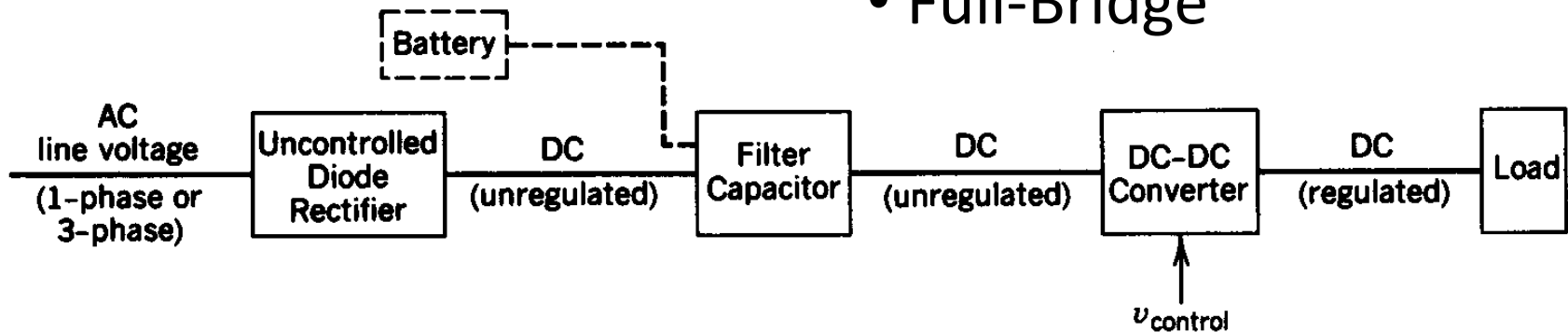


Figure 7-1 A dc–dc converter system.

Ideal concept of step-down converter with PWM* switching

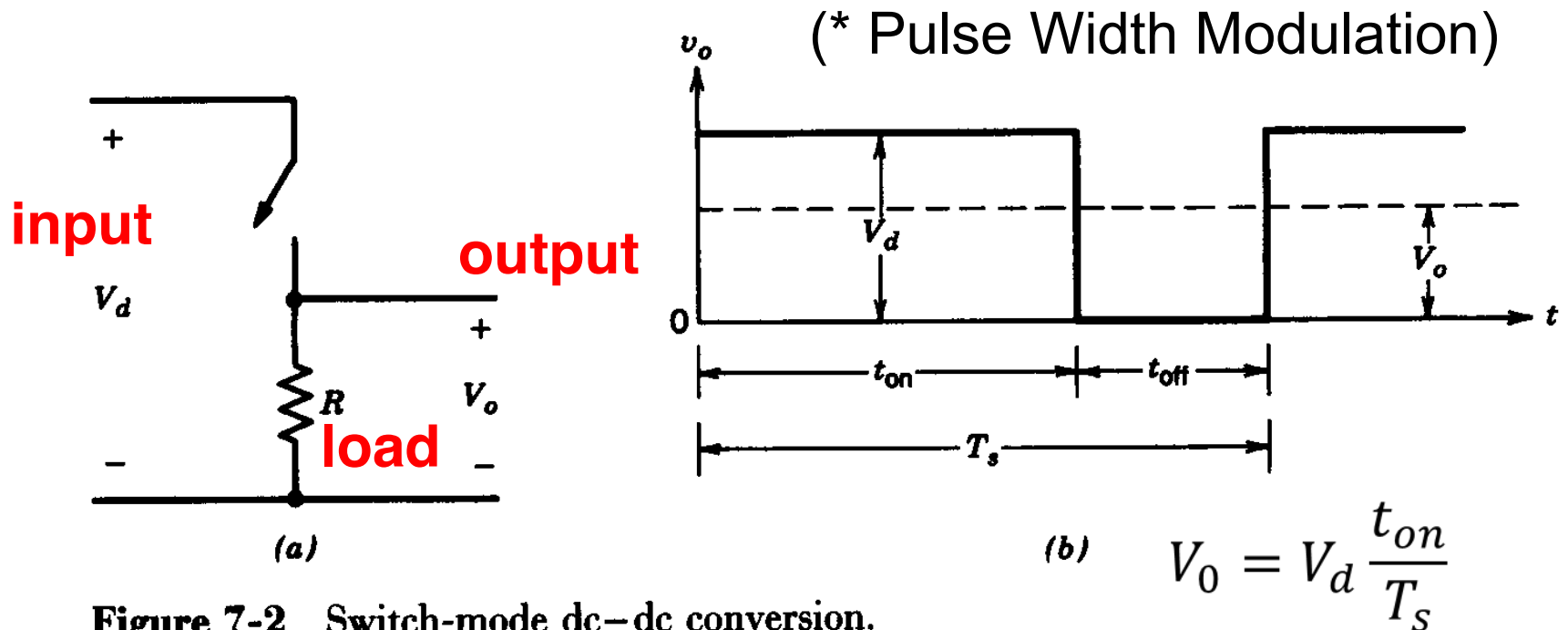


Figure 7-2 Switch-mode dc-dc conversion.

Assumptions: Switches, L, C are lossless, DC input has zero internal impedance, load is an equivalent R

This cannot work: 1. Load is inductive and can destroy switch by dissipating all stored energy, 2. output voltage must be continuous

Step-down (buck) converter



DC power supplies, DC motor drives -- $V_o < V_d$

Low-pass filter keeps output voltage constant

Note: 2nd order non dissipative filter

$$f_c = \frac{1}{2\pi} \frac{1}{\sqrt{LC}} \ll f_s$$

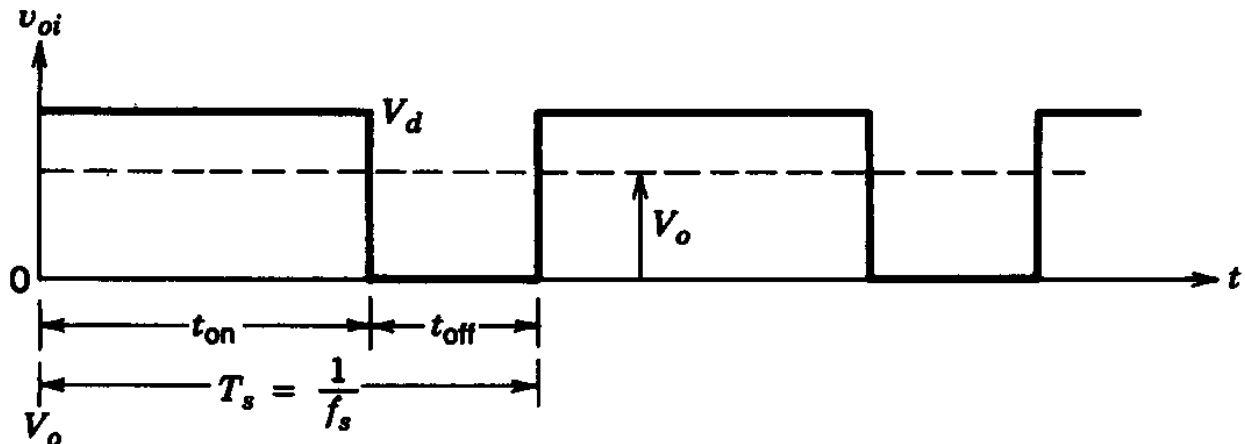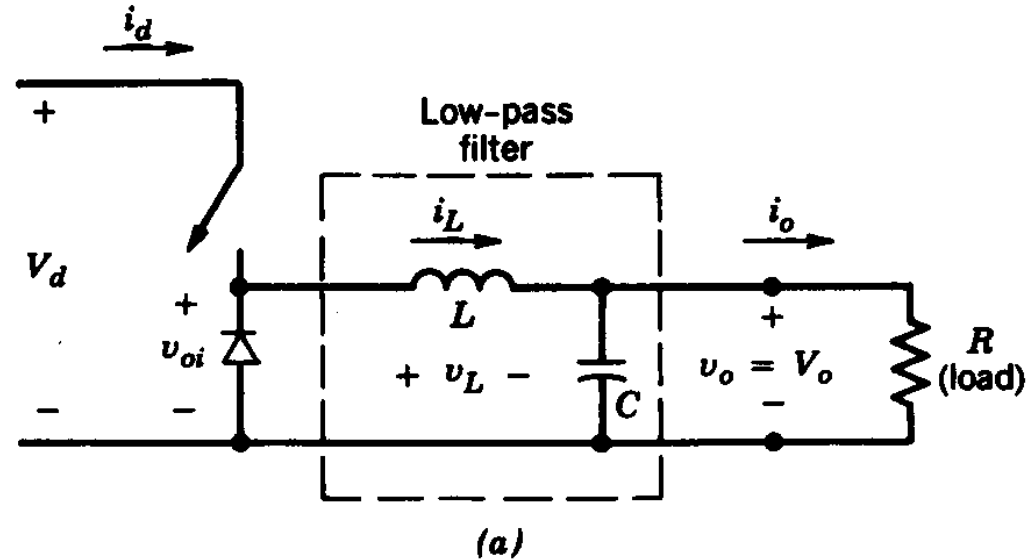Diode avoids voltage spike on switch (when switch is off, diode provides current to L)



Continuous-conduction mode

Current in L is always > 0



- $t_{\text{on}}: \frac{dI}{dt} = \frac{V_d - V_o}{L}$
- $t_{\text{off}}: \frac{dI}{dt} = -\frac{V_o}{L}$

At steady state: $I(t + T_s) = I(t)$.


Therefore

$$\frac{V_d - V_o}{L} t_{\text{on}} - \frac{V_o}{L} t_{\text{off}} = 0$$
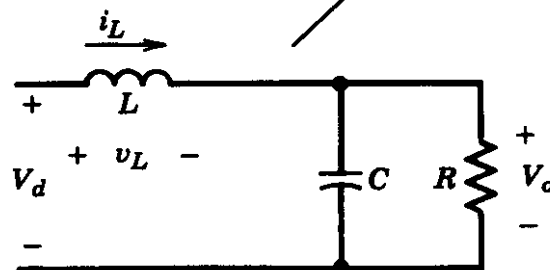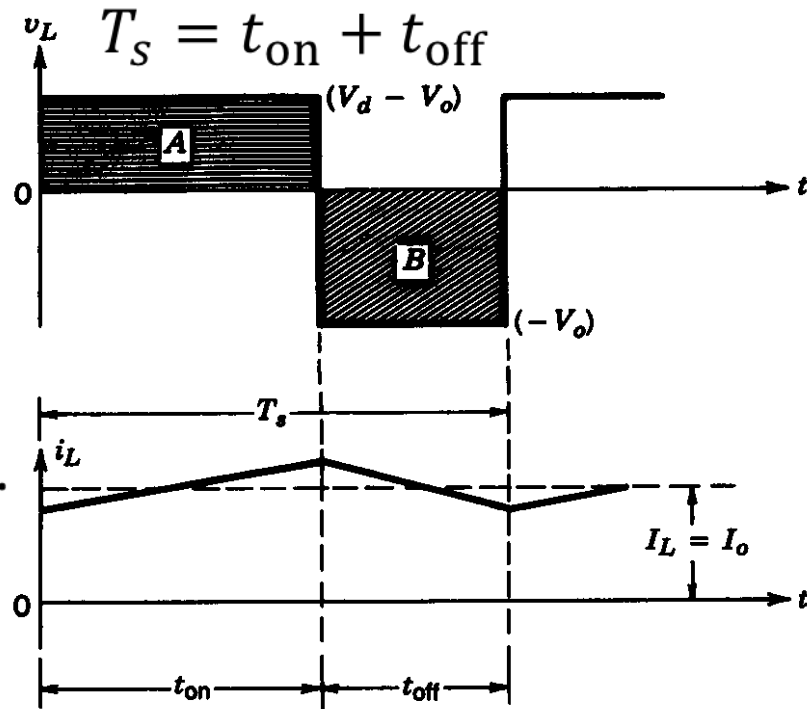
$$\frac{V_o}{V_d} = \frac{t_{\text{on}}}{T_s} = D$$



(a)

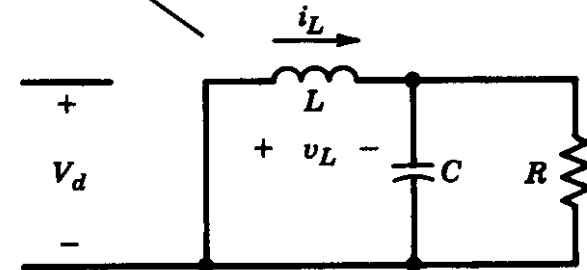

(b)

Limit of continuous conduction

If the ripple amplitude $I_{LB} \equiv \frac{I_{peak}}{2} = I_o$, the converter is at the limit of continuous conduction (i.e. $\min\{I_L\} = 0$)

$$I_{LB} \equiv \frac{I_{peak}}{2} = \frac{t_{on}(V_d - V_o)}{2L} = \frac{DT_s V_d (1 - D)}{2L} = I_{LBmax} 4D(1 - D)$$

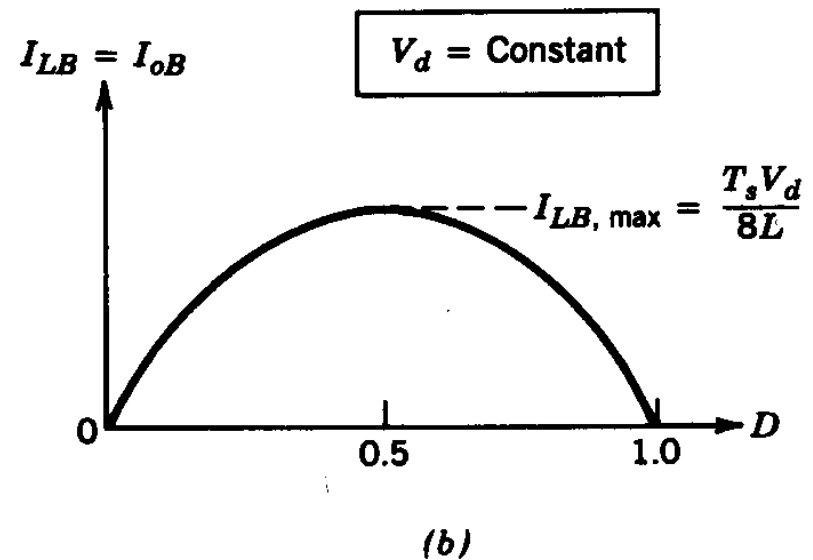
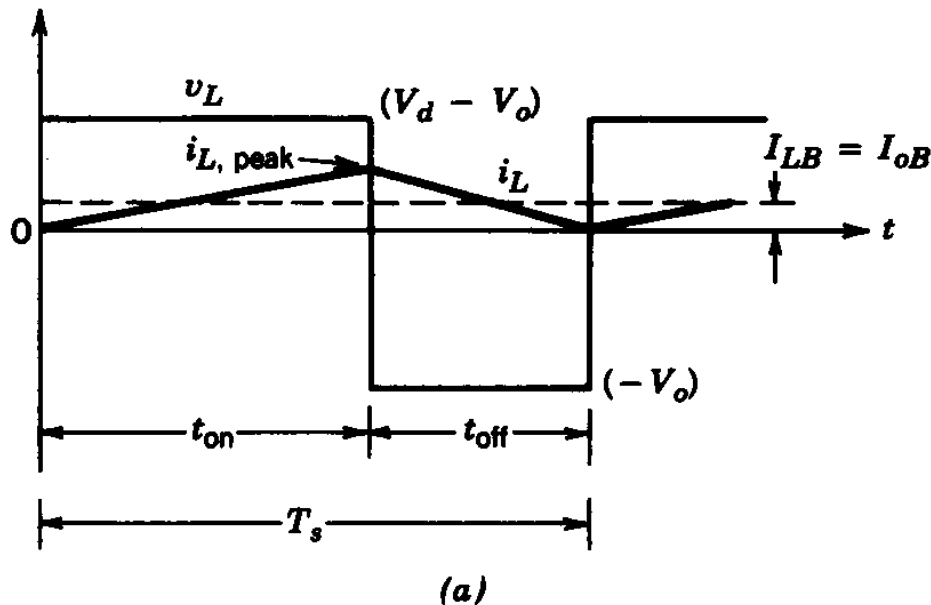


Figure 7-6 Current at the boundary of continuous–discontinuous conduction: (a) current waveform; (b) I_{LB} versus D keeping V_d constant.

Limits of continuous-discontinuous conduction (constant V_d)

Continuous

$$\frac{V_o}{V_d} = D$$

$$\frac{I_o}{I_{LB\max}} > 4D(1 - D)$$


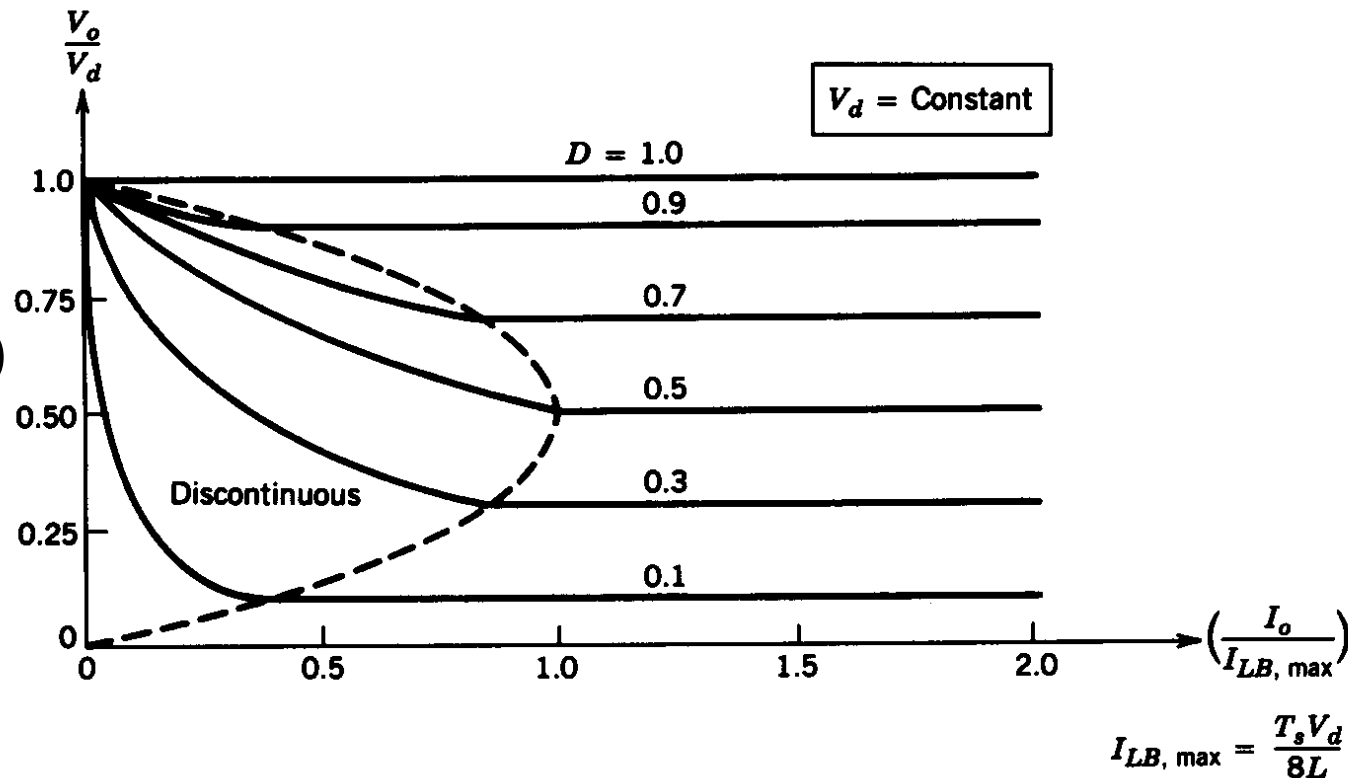


Figure 7-8 Step-down converter characteristics keeping V_d constant.

Discontinuous-conduction mode with constant V_d

Motor drives
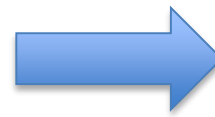
$$I_{\text{peak}} = \frac{(V_d - V_o)DT_s}{L} = \frac{V_o\Delta_1 T_s}{L}$$



$$\frac{V_o}{V_d} = \frac{D}{(D + \Delta_1)}$$

$$I_{\text{peak}} = \frac{V_d T_s}{L} \frac{D\Delta_1}{D + \Delta_1}$$

$$I_{\text{peak}} = 8I_{\text{LBmax}} \frac{D\Delta_1}{D + \Delta_1}$$

$$I_o T_s = \frac{I_{\text{peak}}(D + \Delta_1)T_s}{2}$$

$$I_o = 4I_{\text{LBmax}} D\Delta_1$$

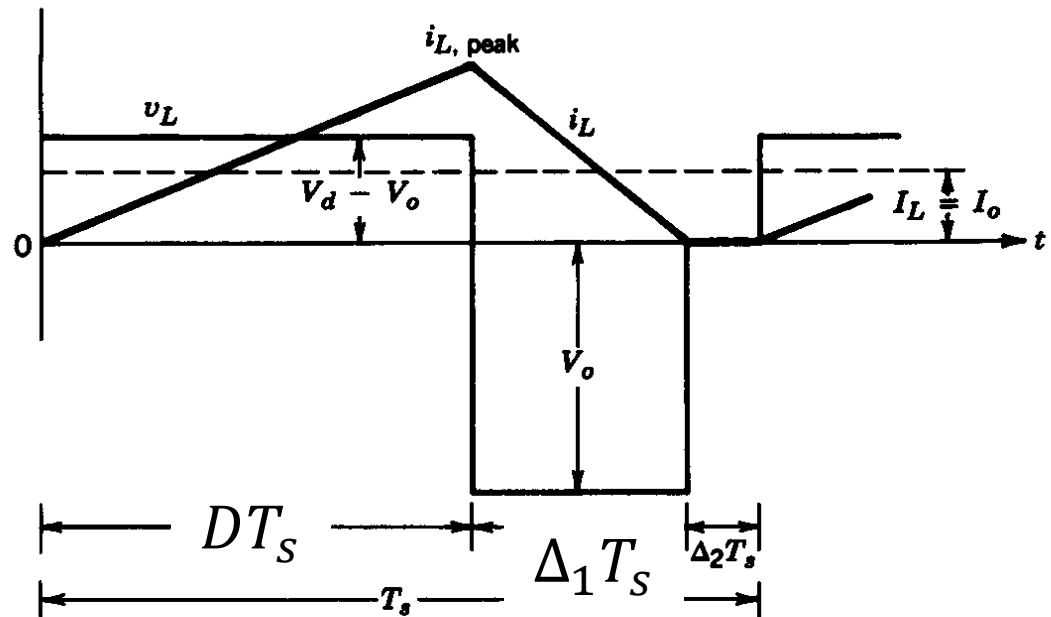


Figure 7-7 Discontinuous conduction in step-down converter.

$$\frac{V_o}{V_d} = \frac{D^2}{D^2 + I_o / (4I_{\text{LBmax}})}$$

Limits of continuous-discontinuous conduction (constant V_d)

Continuous

$$\frac{I_o}{I_{LB\max}} > 4D(1 - D)$$

$$\frac{V_o}{V_d} = D$$

Discontinuous

$$\frac{I_o}{I_{LB\max}} < 4D(1 - D)$$

$$\frac{V_o}{V_d} = \frac{D^2}{D^2 + \frac{I_o}{4I_{LB\max}}}$$

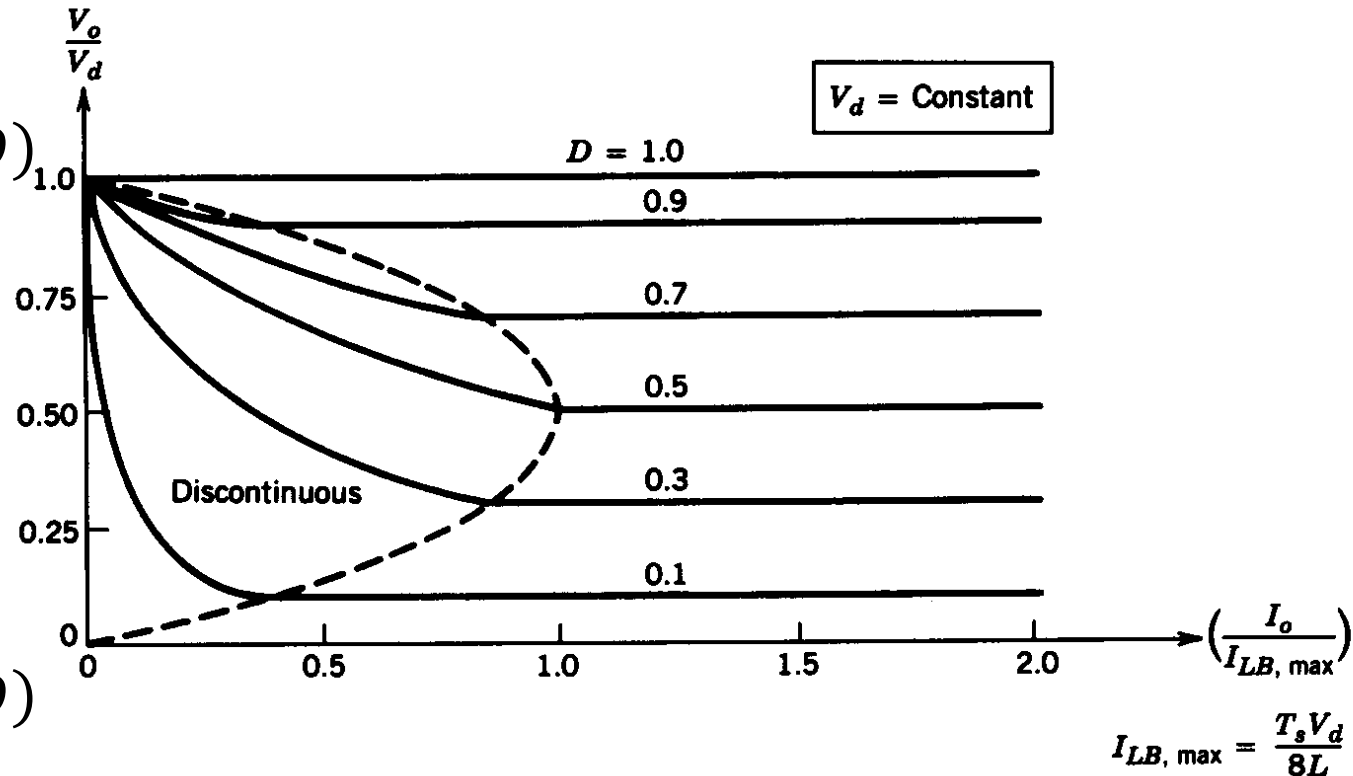


Figure 7-8 Step-down converter characteristics keeping V_d constant.

Discontinuous-conduction with constant V_o

DC voltage
supply

At the limit of continuous conduction

$$I_{LB} = \frac{V_o T_s (1 - D)}{2L} = I_{LB\max} (1 - D)$$

We can write D explicitly from:

$$I_{\text{peak}} = \frac{V_o \Delta_1 T_s}{L} = 2I_{LB\max} \Delta_1$$

$$I_o = \frac{I_{\text{peak}}(D + \Delta_1)}{2} = I_{LB\max} \Delta_1 (D + \Delta_1) \qquad \frac{V_d}{V_o} = \frac{D + \Delta_1}{D}$$

$$\frac{I_o}{I_{LB\max}} = D^2 \frac{V_d}{V_o} \left(1 - \frac{V_d}{V_o}\right) \Rightarrow D = \left[\frac{V_o}{V_d} \frac{I_o}{I_{LB\max}} \left(1 - \frac{V_d}{V_o}\right)^{-1} \right]^{\frac{1}{2}}$$

Discontinuous-conduction with constant V_o

DC voltage supply

Continuous: $I_o > I_{LB}$

$$D > 1 - \frac{I_o}{I_{LBmax}}$$

$$D = \frac{V_o}{V_d}$$

Discontinuous: $I_o < I_{LB}$

$$D < 1 - \frac{I_o}{I_{LBmax}}$$

$$D = \left[\frac{V_o}{V_d} \frac{I_o}{I_{LBmax}} \left(1 - \frac{V_d}{V_o} \right)^{-1} \right]^{\frac{1}{2}}$$

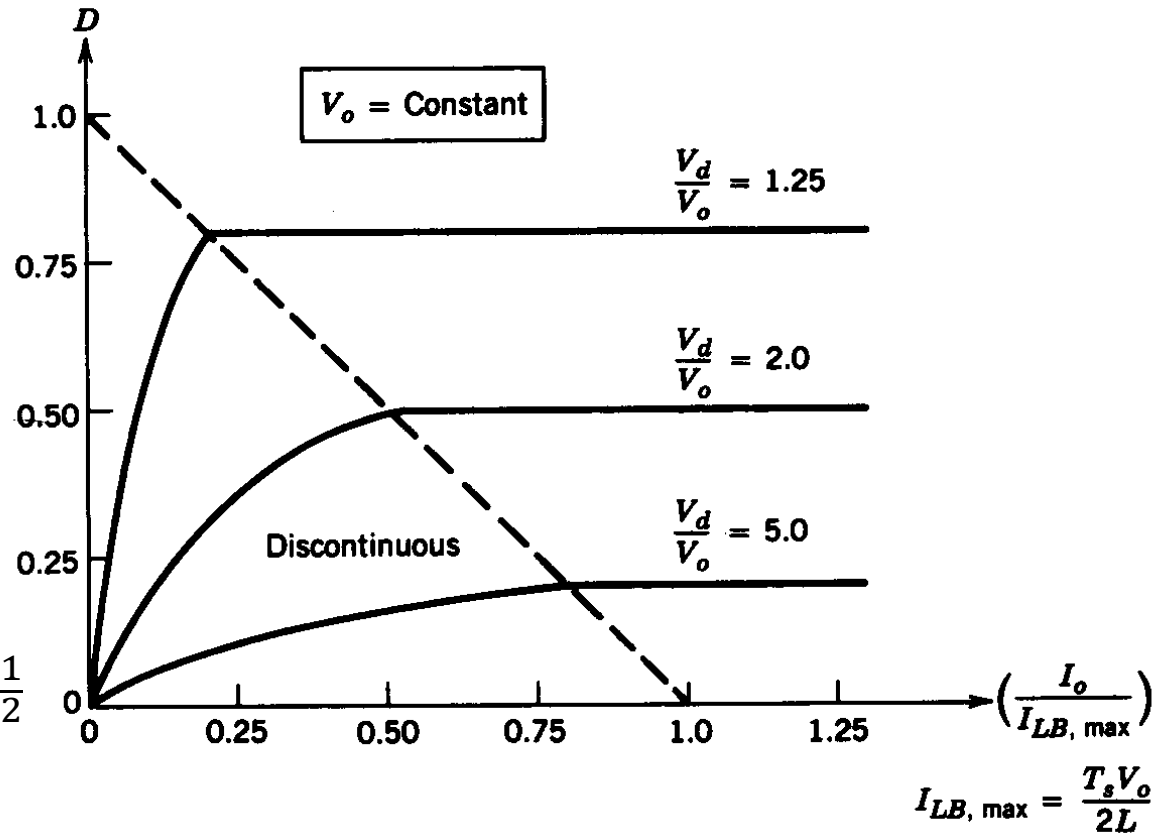


Figure 7-9 Step-down converter characteristics keeping V_o constant.

Output voltage ripple

First order calculation:

The average i_L flows in the load, and the ripple component in C.

Additional charge:

$$\Delta Q = \frac{1}{2} \frac{\Delta I_L}{2} \frac{T_s}{2}$$


Current ripple:

$$\Delta I_L = (V_o/L)(1-D)T_s$$

Voltage ripple:

$$\Delta V_o = \frac{\Delta Q}{C} = \frac{V_o}{8LC} T_s^2 (1-D)$$
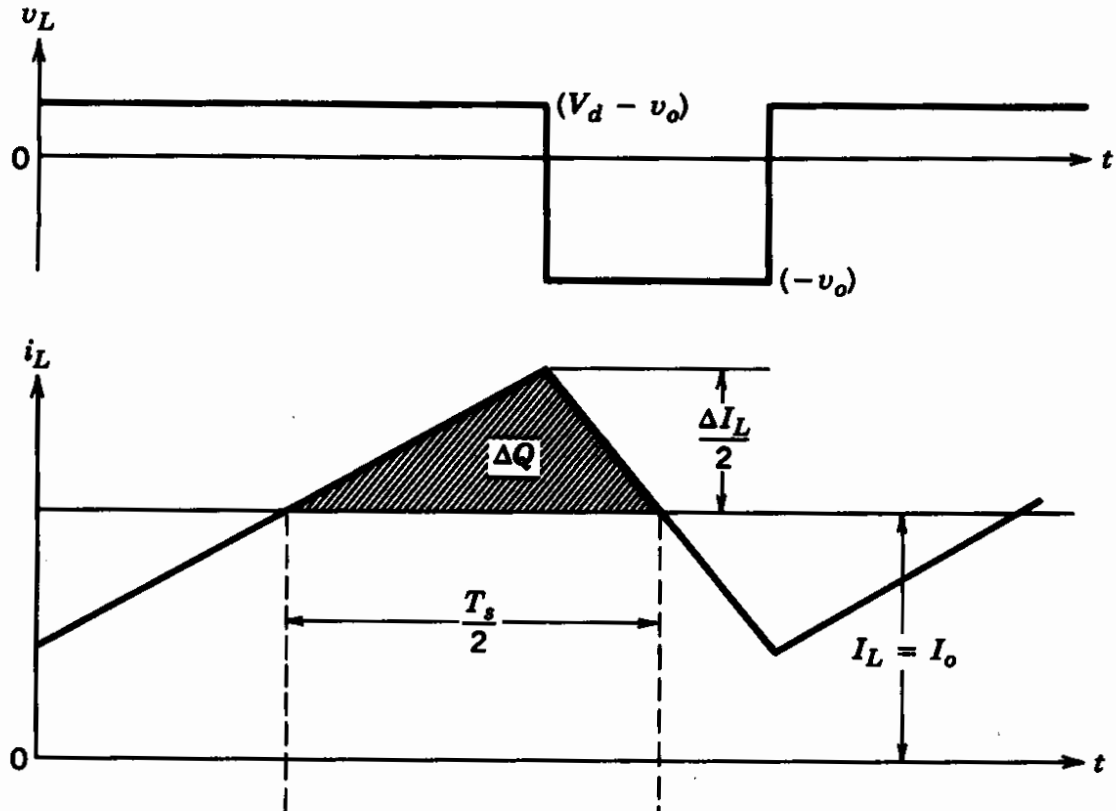
$$f_c = \frac{1}{2\pi} \frac{1}{\sqrt{LC}}$$



$$\frac{\Delta V_o}{V_o} = \frac{\pi^2}{2} (1-D) \frac{f_c^2}{f_s^2}$$


Step-up (boost) converter

- DC power supplies
- Regenerative braking of DC motors

Output voltage always larger than the input

Switch on → diode off, output isolated, L accumulates energy from input

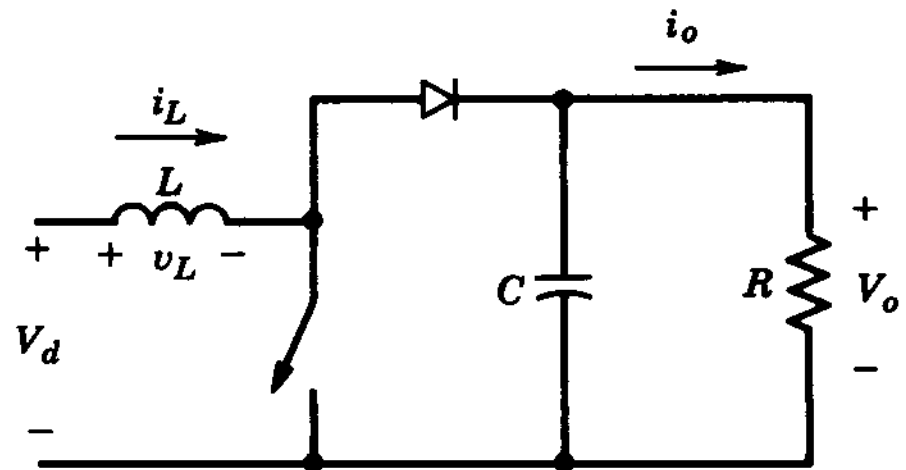Switch off → diode on, load receives energy from input and from L



Continuous-conduction mode

Periodic conditions:

$$\frac{t_{\text{on}} V_d}{L} + \frac{t_{\text{off}} (V_d - V_o)}{L} = 0$$

if $t_{\text{on}} = DT_s$ and



$$t_{\text{off}} = (1 - D)T_s$$

$$T_s V_d + T_s (1 - D) V_o = 0$$


$$\frac{V_o}{V_d} = \frac{1}{1 - D}$$

No losses:

$$V_o I_o = V_d I_d$$

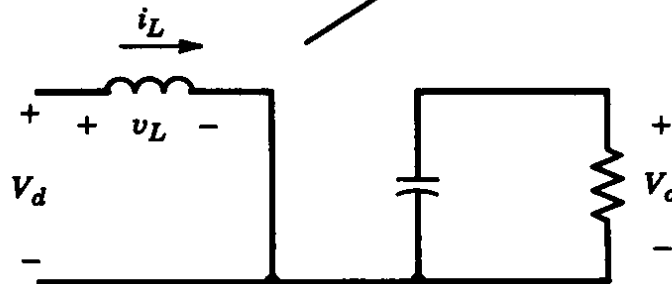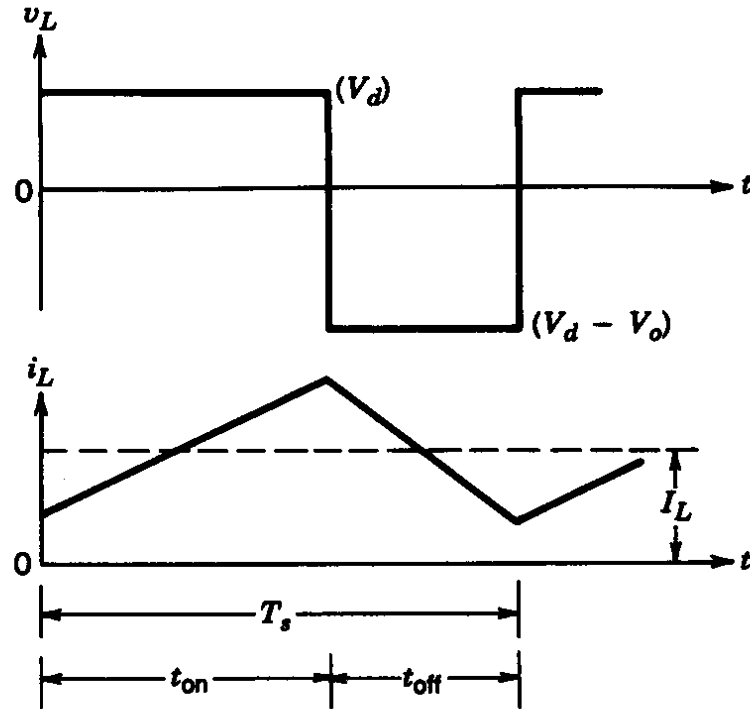

(a)

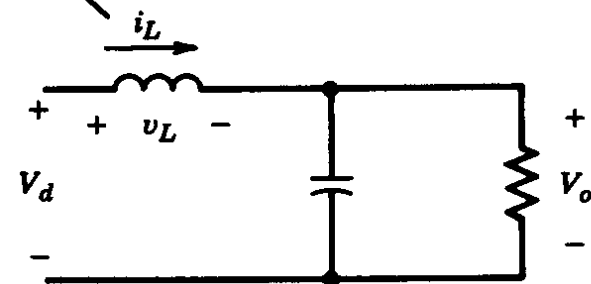

(b)

Continuous-discontinuous boundary

Average current in L
= ripple :


$$I_{LB} = \frac{V_d t_{on}}{2L}$$

$$= \frac{V_o(1-D)T_s D}{2L}$$

Average output
current at the limit:

$$I_{oB} = I_{LB}(1-D)$$

$$= \frac{V_o T_s (1-D)^2 D}{2L}$$

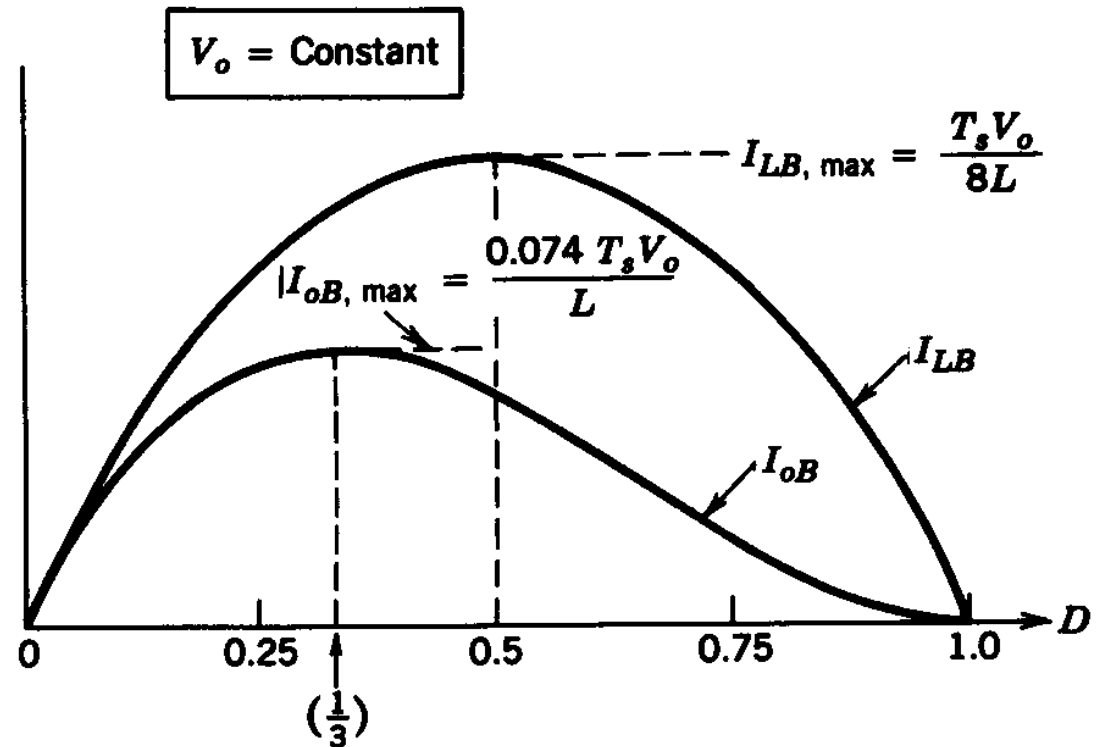

$$I_{LB} \text{ is max if } D=0.5 \rightarrow I_{LB\max} = \frac{V_o T_s}{8L},$$

$$I_{oB} \text{ is max if } D=1/3 \rightarrow I_{oB\max} = \frac{2V_o T_s}{27L} \rightarrow I_{oB} = \frac{27}{4} (1-D)^2 D I_{oB\max}$$

Discontinuous conduction mode (constant V_o)

Periodic conditions:

$$\frac{DT_s V_d}{L} + \frac{\Delta_1 T_s (V_d - V_o)}{L} = 0$$

$$\frac{V_o}{V_d} = 1 + \frac{D}{\Delta_1} = \frac{I_d}{I_o}$$


Average current in L

$$I_d T_s = \frac{DT_s V_d}{L} \frac{(D + \Delta_1) T_s}{2}$$

Average output current

$$I_o = I_d \frac{\Delta_1}{D + \Delta_1} = \frac{T_s V_d}{2L} D \Delta_1$$
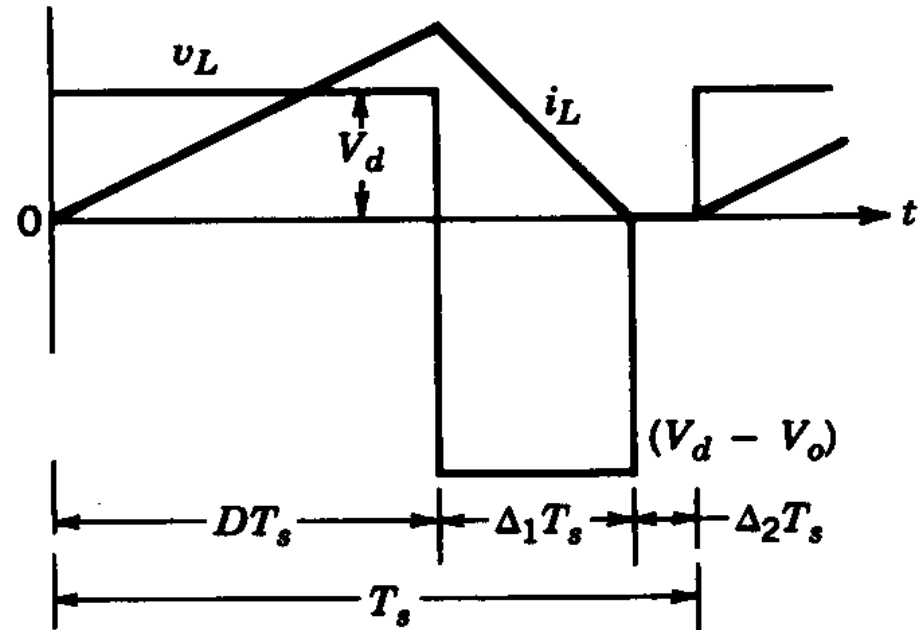
$$= \frac{27}{4} I_{oBmax} \frac{V_d}{V_o} D^2 \frac{V_d}{V_o - V_d}$$



$$\Rightarrow D = \left[\frac{4}{27} \frac{V_o}{V_d} \left(\frac{V_o}{V_d} - 1 \right) \frac{I_o}{I_{oBmax}} \right]^{\frac{1}{2}}$$

Continuous-discontinuous mode (constant V_o)

Continuous mode:

$$I_o > I_{oB}$$

$$= I_{oBmax} \frac{27(1-D)^2 D}{4}$$

$$D = 1 - \frac{V_d}{V_o}$$

Discontinuous mode:

$$I_o < I_{oB}$$

$$D = \left[\frac{4}{27} \frac{V_o}{V_d} \left(\frac{V_o}{V_d} - 1 \right) \frac{I_o}{I_{oBmax}} \right]^{\frac{1}{2}}$$

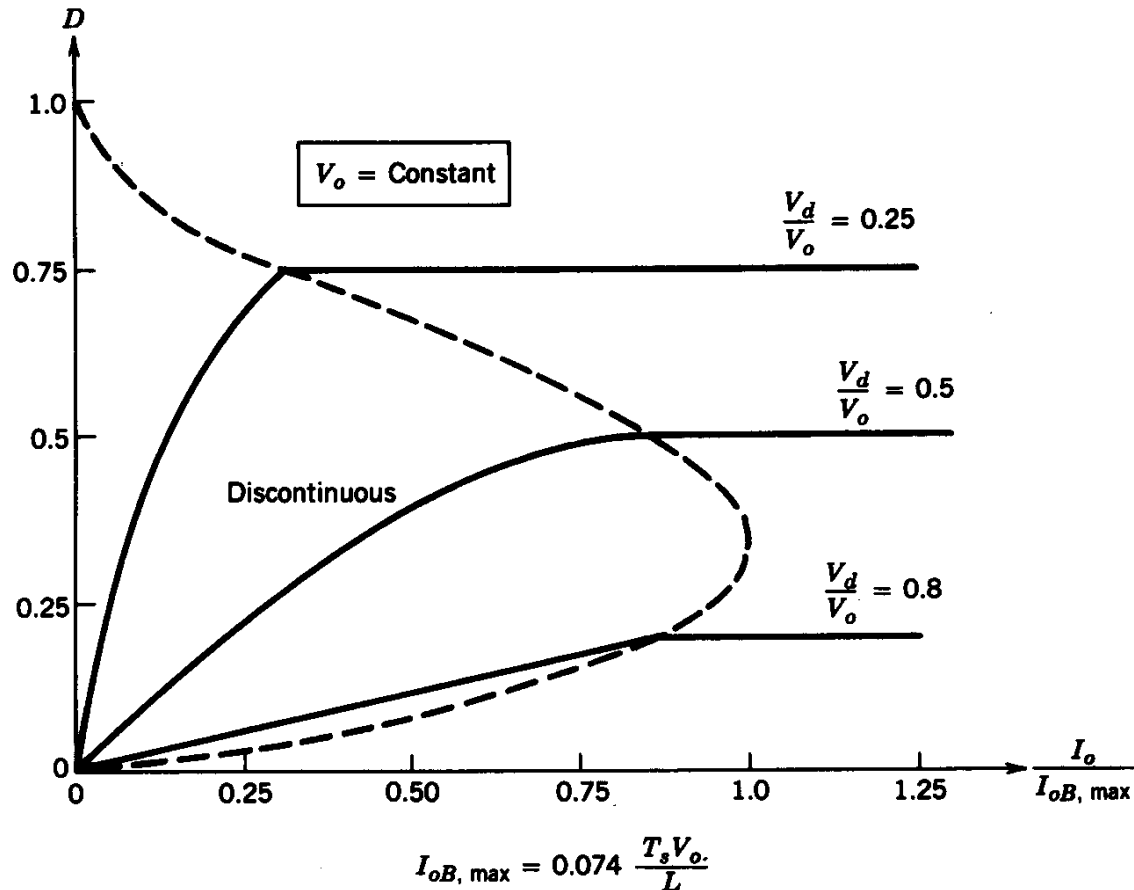


Figure 7-15 Step-up converter characteristics keeping V_o constant.

Losses and ripple

Losses: inductor, capacitor, switch, diode

Ripple: first order assumption: when the switch is on the C is discharged through the load

$$\Delta V_o = \frac{\Delta Q}{C} = \frac{I_o D T_s}{C} = \frac{V_o D T_s}{RC}$$


$$\frac{\Delta V_o}{V_o} = D \frac{T_s}{\tau}$$

Buck-boost converter

Negative DC power supply


Switch on: inductance accumulates energy, diode off, C supplies the load

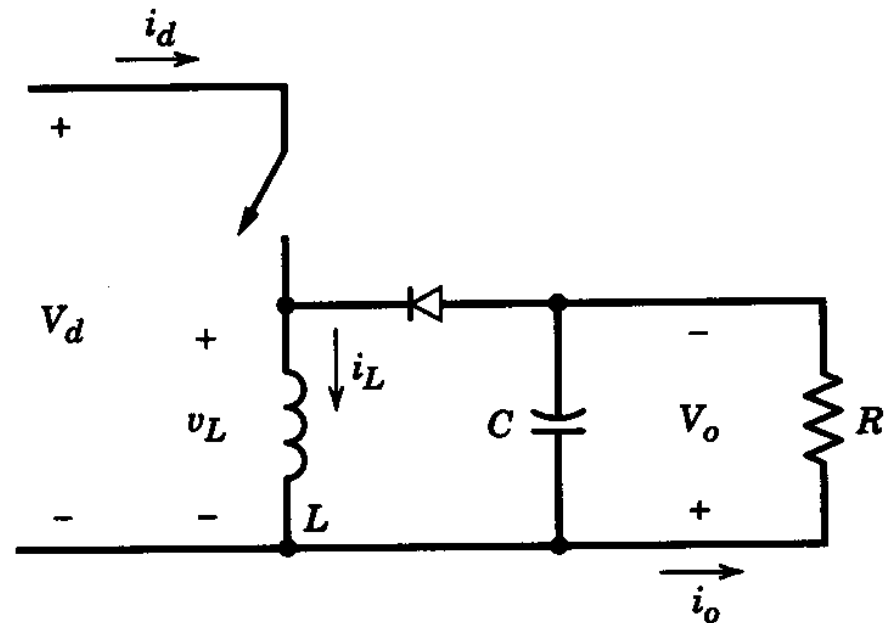Switch off: diode on, inductance transfers energy to the capacitance and to the load



Periodic conditions in continuous conduction mode:
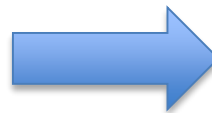
$$\frac{DT_s V_d}{L} - \frac{V_o(1-D)T_s}{L} = 0$$



$$\frac{V_o}{V_d} = \frac{D}{1-D} = \frac{I_d}{I_o}$$

$$I_L = I_o + I_d = \frac{I_o}{1-D}$$

Continuous-discontinuous boundary

Current in L at the boundary



$$I_{LB} = \frac{DT_s V_d}{2L}$$

Output current at the boundary:

$$I_{oB} = I_{LB}(1 - D) = \frac{T_s V_o}{2L} (1 - D)^2$$

$$I_{LB} = I_{LBmax}(1 - D)$$

$$I_{oB} = I_{oBmax}(1 - D)^2$$

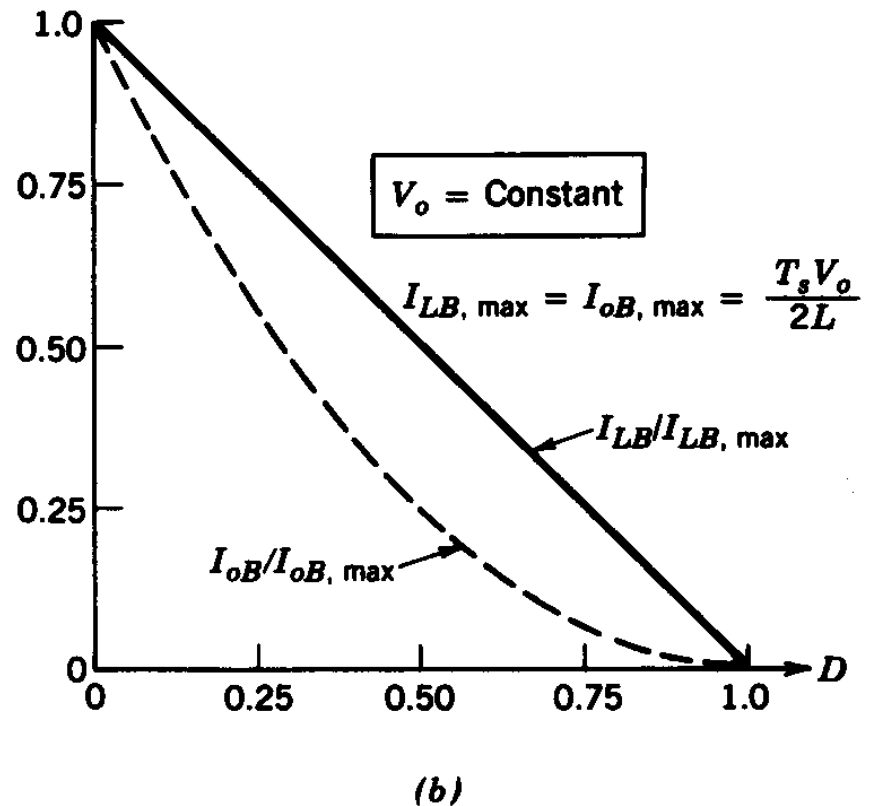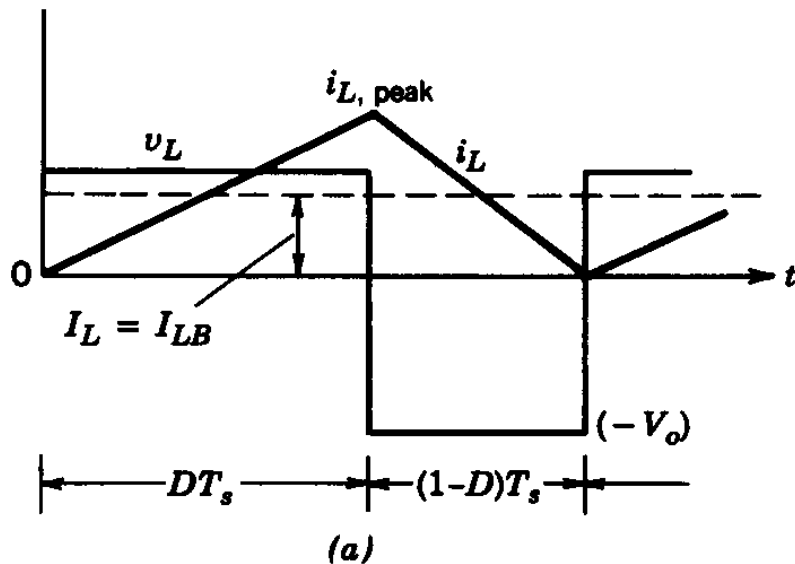

Discontinuous conduction

Periodic conditions:

$$\frac{DV_d T_s}{L} - \frac{V_o \Delta_1 T_s}{L} = 0$$

$$\frac{V_o}{V_d} = \frac{D}{\Delta_1} = \frac{I_d}{I_o}$$

Average current in L:

$$I_L T_s = \frac{V_d D T_s}{L} \frac{(D + \Delta_1) T_s}{2}$$

Therefore:

$$I_L = I_o \left(1 + \frac{D}{\Delta_1} \right) = \frac{V_d T_s}{2L} D (D + \Delta_1)$$

$$\frac{I_o}{I_{oBmax}} = D \Delta_1 \frac{V_d}{V_o} = D^2 \left(\frac{V_d}{V_o} \right)^2 \rightarrow D = \frac{V_o}{V_d} \sqrt{\frac{I_o}{I_{oBmax}}}$$

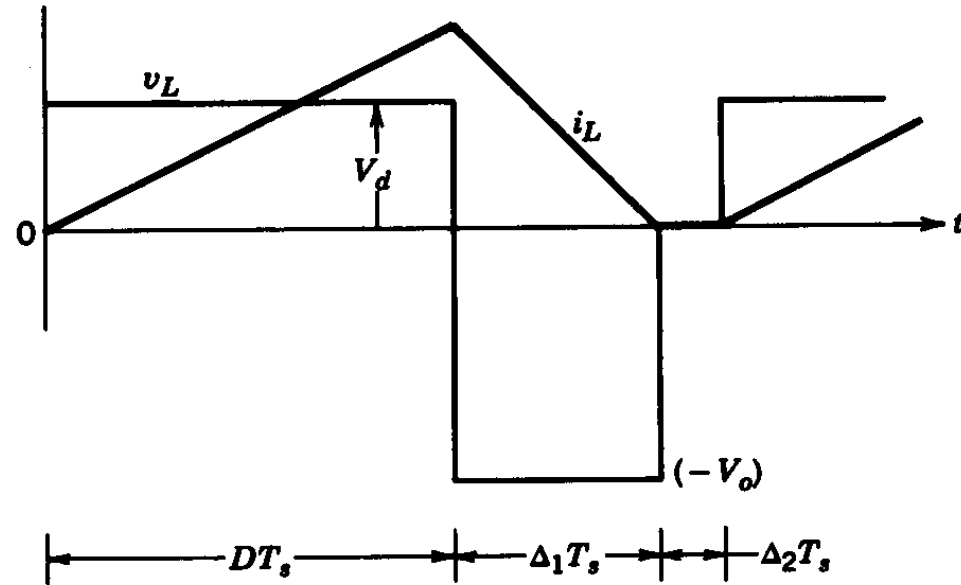


Figure 7-21 Buck–boost converter waveforms in a discontinuous-conduction mode.

Continuous-discontinuous mode

Continuous operation

$$I_o > I_{oB} = I_{oBmax}(1 - D)^2$$

$$D = \frac{V_o}{V_d - V_o}$$

Discontinuous operation

$$I_o < I_{oB}$$

$$D = \frac{V_o}{V_d} \sqrt{\frac{I_o}{I_{oBmax}}}$$

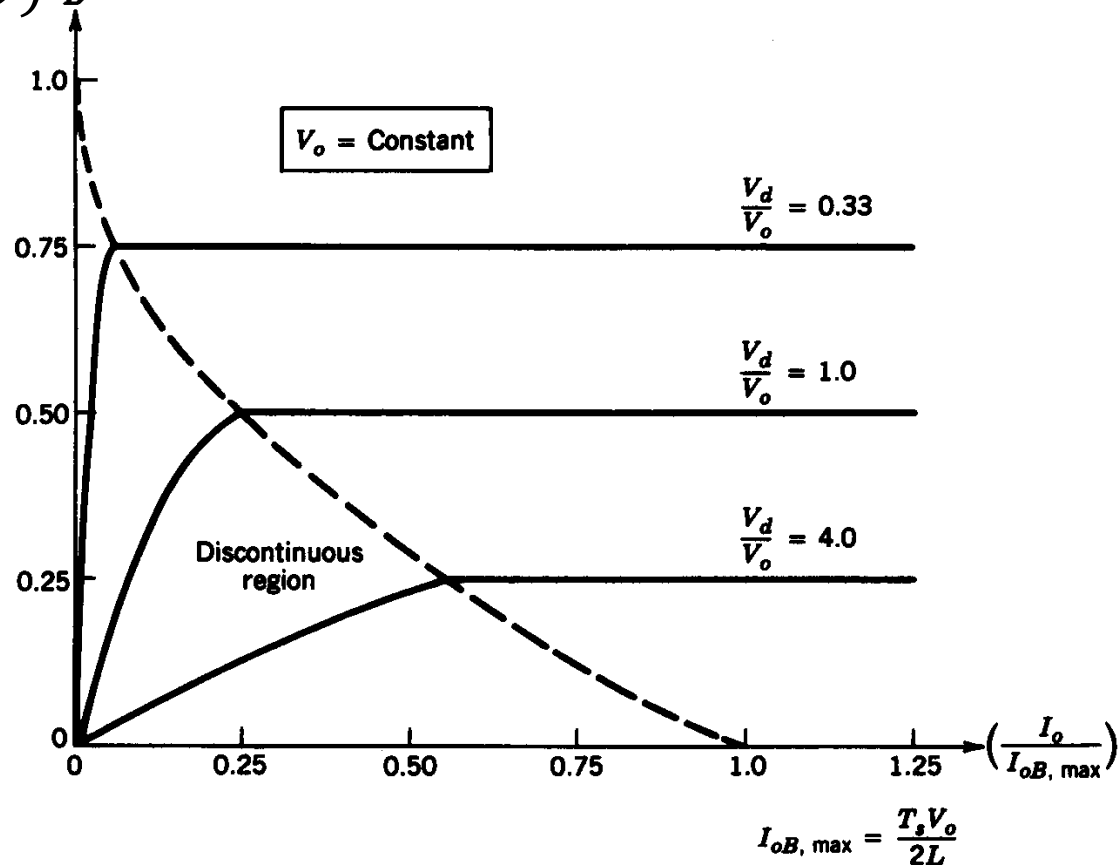


Figure 7-22 Buck-boost converter characteristics keeping V_o constant.

Output voltage ripple

When the switch is ON, C is discharged through the load

$$\Delta V_o = \frac{\Delta Q}{C} = \frac{DT_s V_o}{RC} \rightarrow \frac{\Delta V_o}{V_o} = D \frac{T_s}{\tau}$$

Cuk DC-DC converter

Negative DC power supply

DC analysis: $V_{C1} = V_d + V_o$ note: ($V_{C1} > V_d$)

Assumption: Large $C1$ (Voltage almost constant)

Switch OFF: $C1$ is charged through $L1$ and the input, Diode ON, $L2$ supplies energy to R (currents in $L1$ and $L2$ decrease)

Switch ON: $L1$ receives energy, Diode OFF, C supplies current to R , $C1$ gives energy to $L2$ (currents in $L1$ and $L2$ increase)

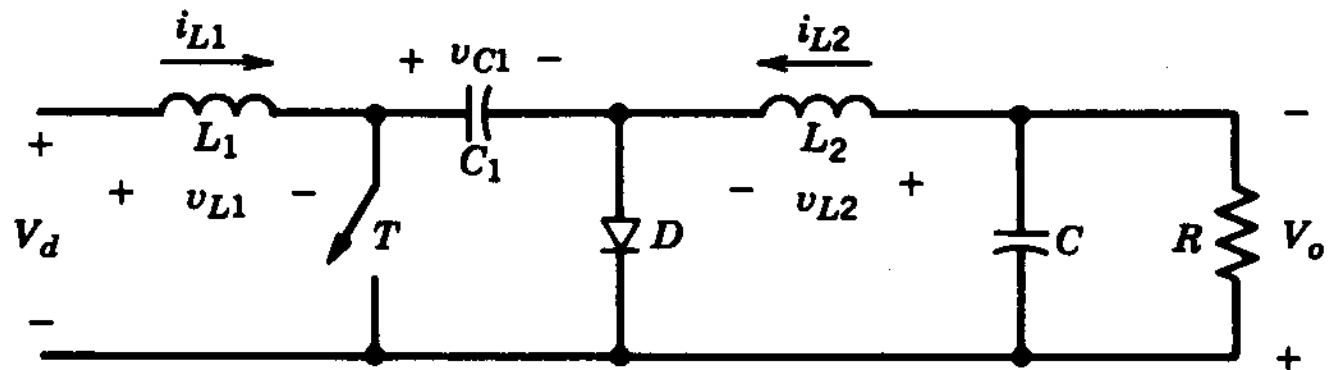


Figure 7-25 Cúk converter.

Cuk

Periodic conditions in L1

$$V_d D T_s + (1 - D) T_s (V_d - V_{C1}) = 0$$

$$V_{C1} = \frac{V_d}{1 - D}$$

Periodic conditions in L2

$$(V_{C1} - V_o) D T_s - V_o (1 - D) T_s = 0$$

$$V_{C1} = \frac{V_o}{D}$$

Therefore

$$\frac{V_o}{V_d} = \frac{D}{1 - D}$$

Pro: currents

in L1 and L2 ripple free

Con: C1 must be large

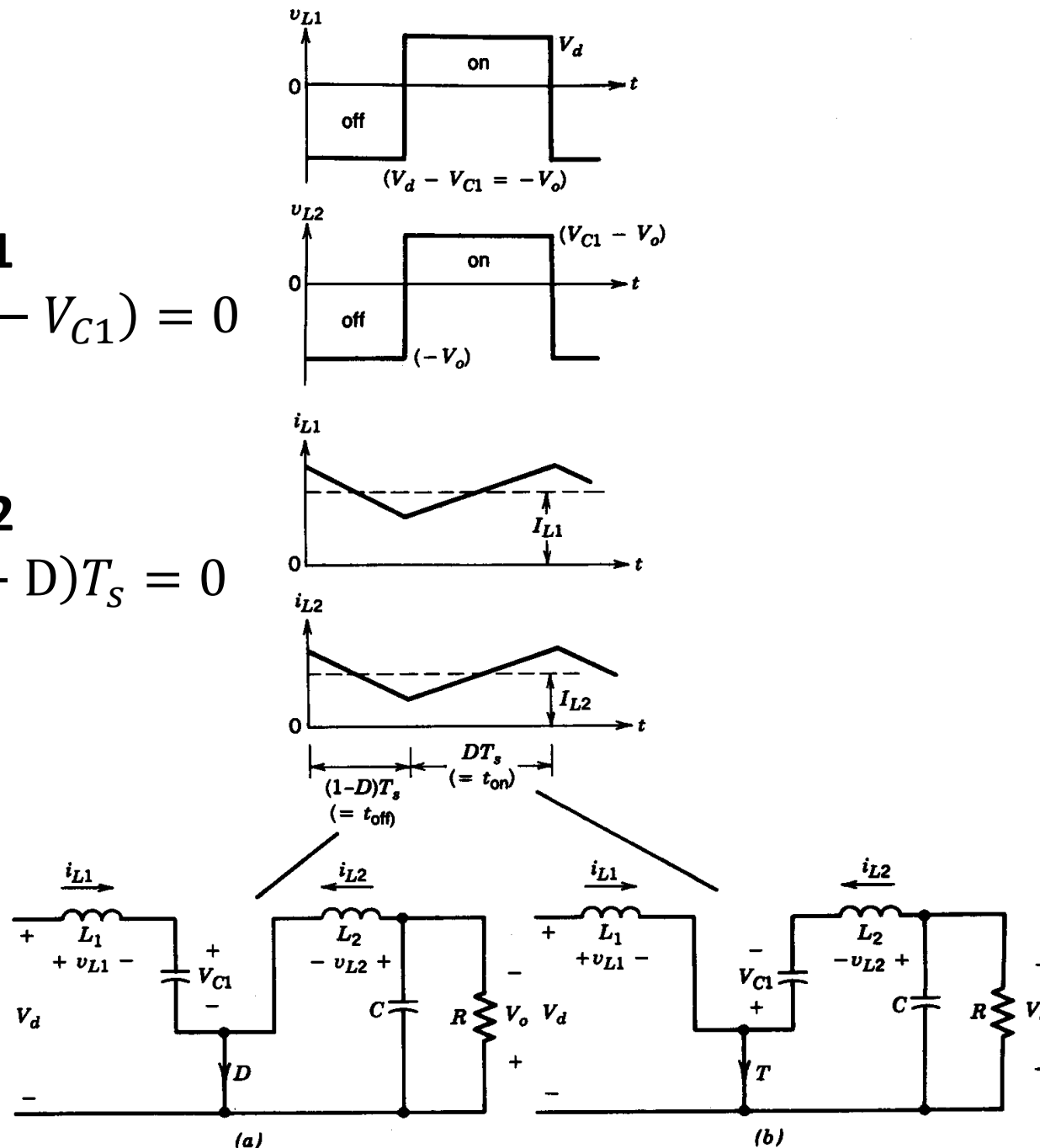


Figure 7-26 Cuk converter waveforms: (a) switch off; (b) switch on.

Full bridge DC-DC converter

Applications:

- DC motor drives
- DC to AC conversion in UPS
- DC to AC conversion in transformer isolated power supply

Fixed V_d .

Control polarity and amplitude of V_o

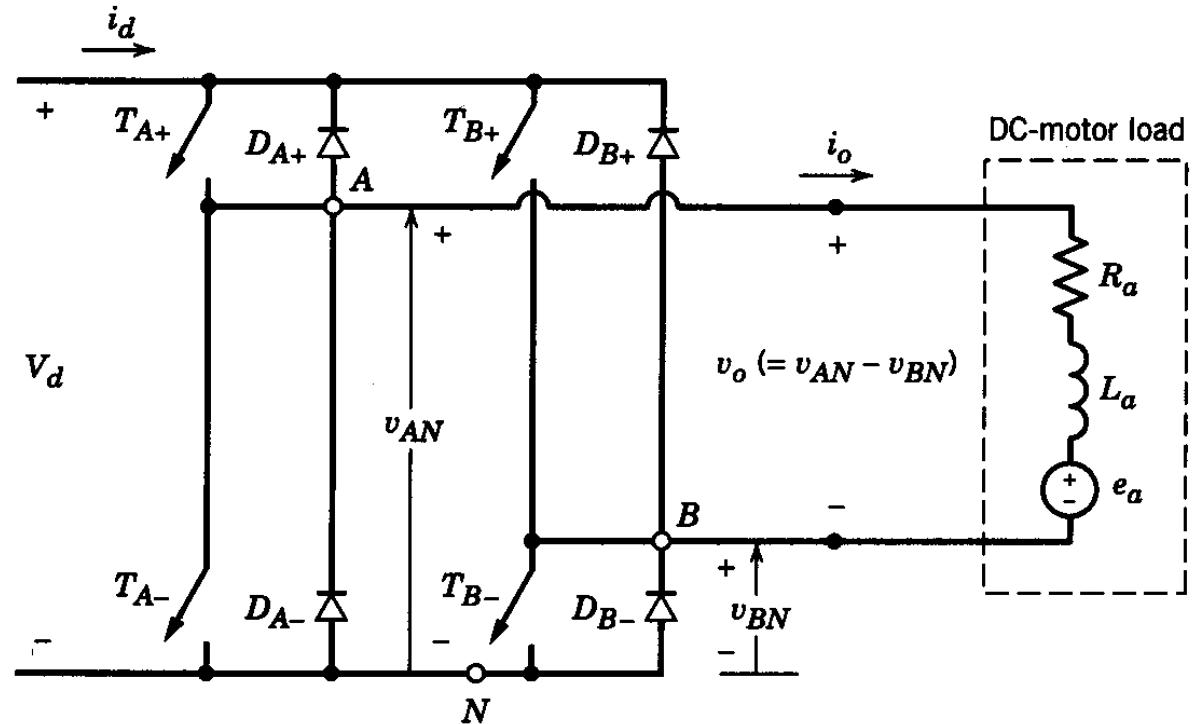


Figure 7-27 Full-bridge dc-dc converter.

Two legs: A and B. **Only one switch** in each leg is ON at any time

Full bridge DC-DC converter

When switch TA+ is on:

$i_o > 0$: i_o through TA+

$i_o < 0$: i_o through DA+

$V_{AN} = V_d \text{duty cycle}(TA^+)$

When switch TB+ is on:

$i_o < 0$: i_o through TB+

$i_o > 0$: i_o through DB+

$V_{BN} = V_d \text{duty cycle}(TB^+)$

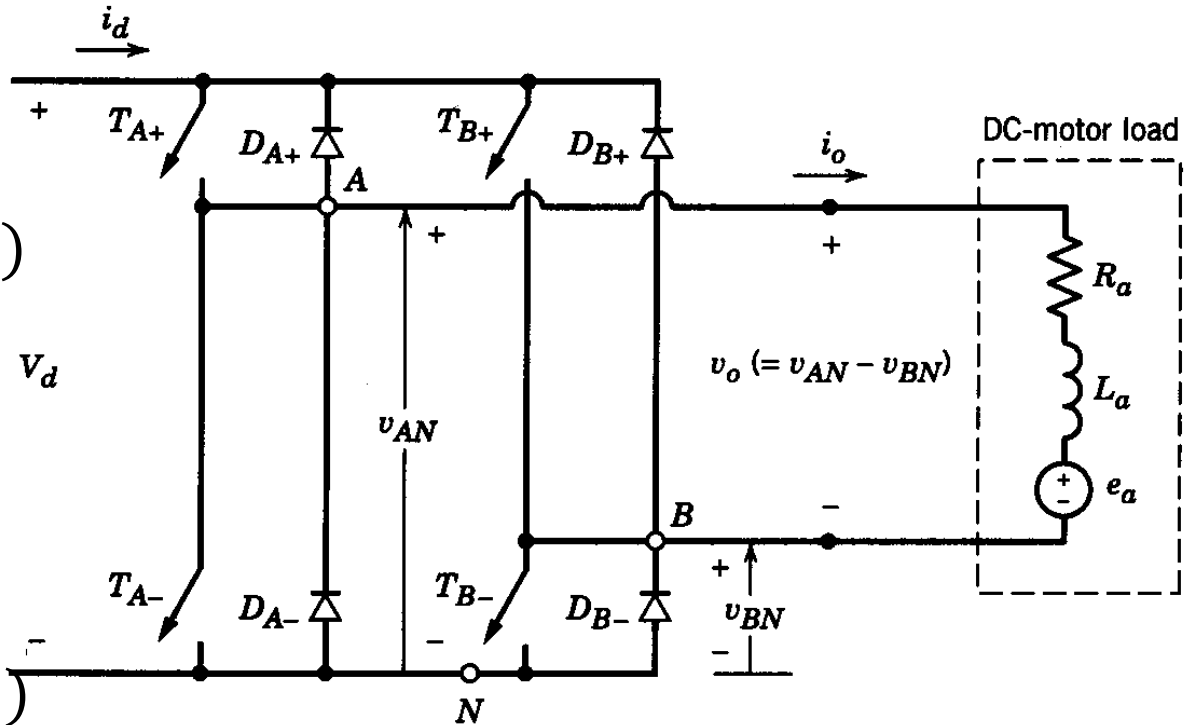


Figure 7-27 Full-bridge dc-dc converter.

$$V_o = V_{AN} - V_{BN}$$

Four quadrant operation
on V_o, I_o

PWM with bipolar voltage switching.

When $v_{control} > v_{tri}$,

TA+ and TB- are **ON**

Duty cycle

$$D_1 = \frac{1}{2} + \frac{v_{control}}{\widehat{V}_{tri}} \frac{1}{2}$$

When $v_{control} < v_{tri}$,


TA- and TB+ are **ON**

$$D_2 = 1 - D_1$$

$$V_o = V_{AN} - V_{BN} = D_1 V_d - D_2 V_d$$

$$= (2D_1 - 1)V_d$$
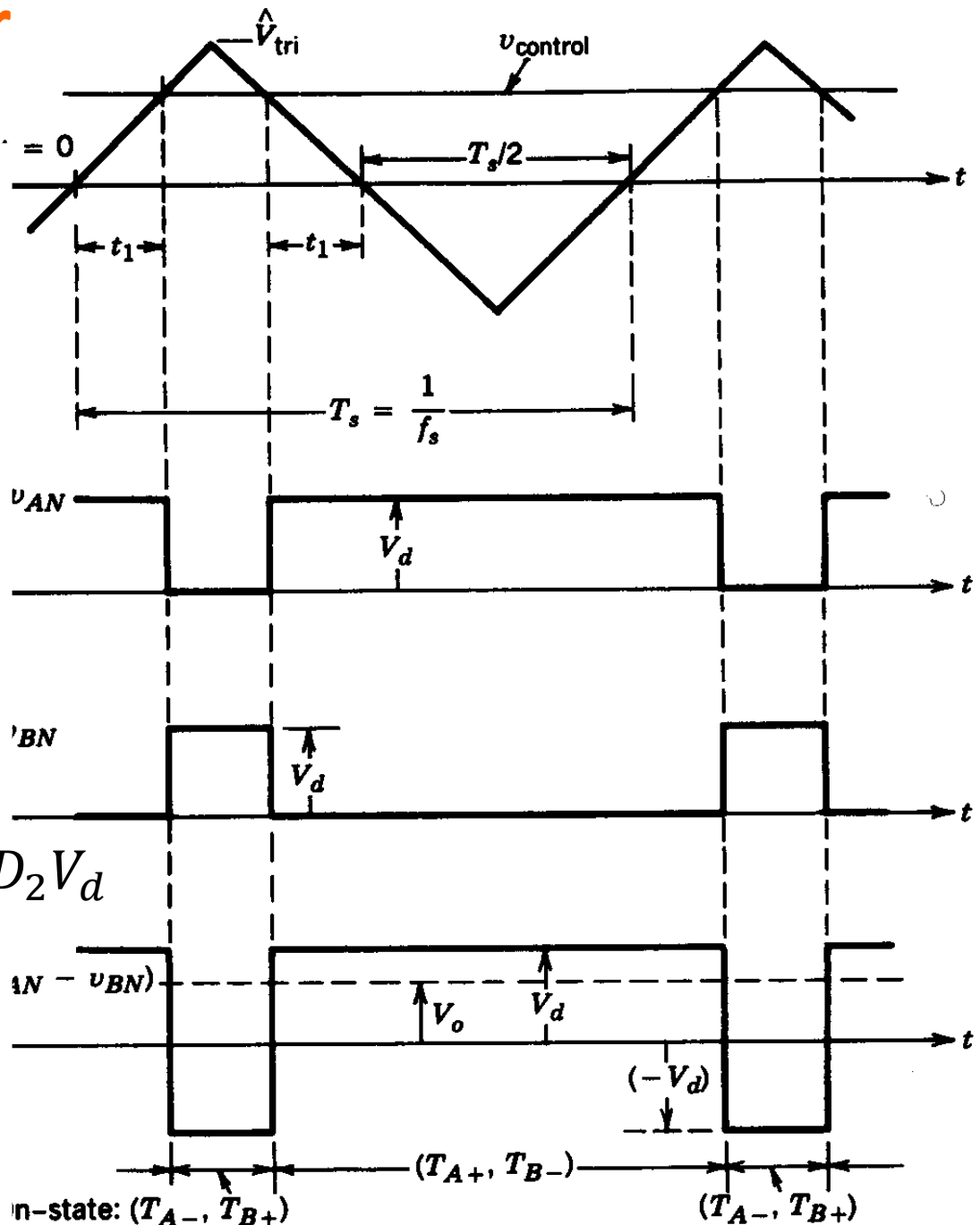
$$= \frac{V_d}{\widehat{V}_{tri}} v_{control}$$



PWM with unipolar voltage switching

When $v_{control} > v_{tri}^{(a)}$
TA+ and TB- are **ON**


Duty cycle

$$D_1 = \frac{1}{2} + \frac{v_{control}}{\widehat{V}_{tri}} \frac{1}{2}^{(b)}$$

When $-v_{control} < v_{tri}^{(c)}$
TA- and TB+ are **ON**



$$D_2 = 1 - D_1$$
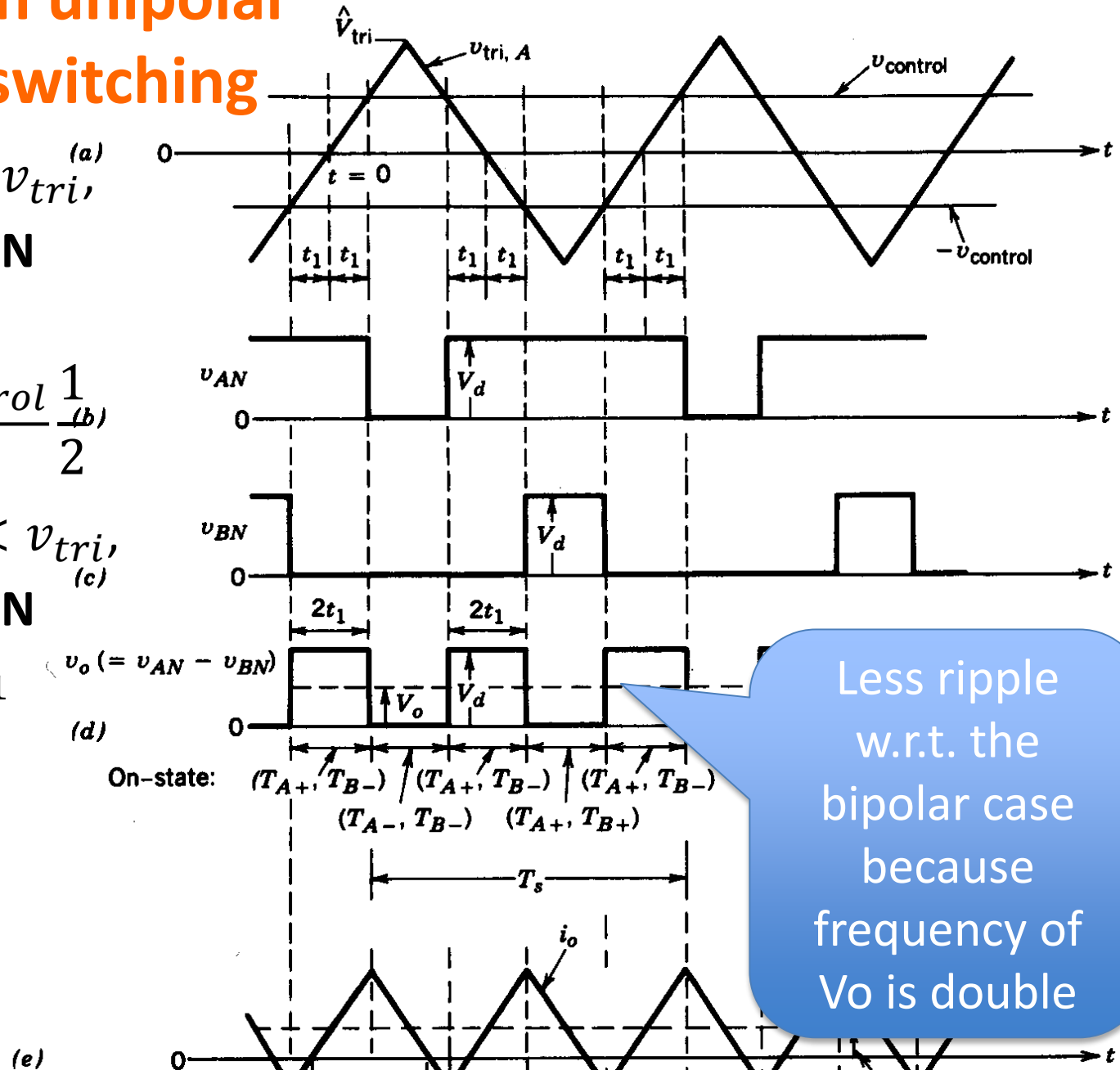
$$\begin{aligned} V_o &= V_{AN} - V_{BN} \\ &= D_1 V_d - D_2 V_d \\ &= (2D_1 - 1)V_d \\ &= \frac{V_d}{\widehat{V}_{tri}} v_{control} \end{aligned}$$




Less ripple
w.r.t. the
bipolar case
because
frequency of
 V_o is double

PWM signal generation

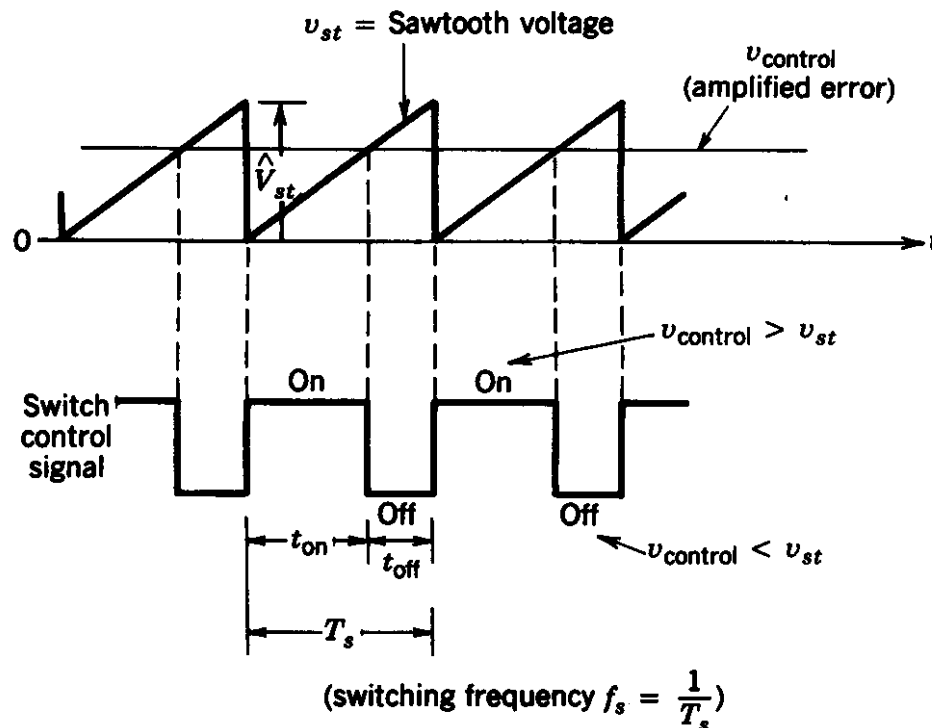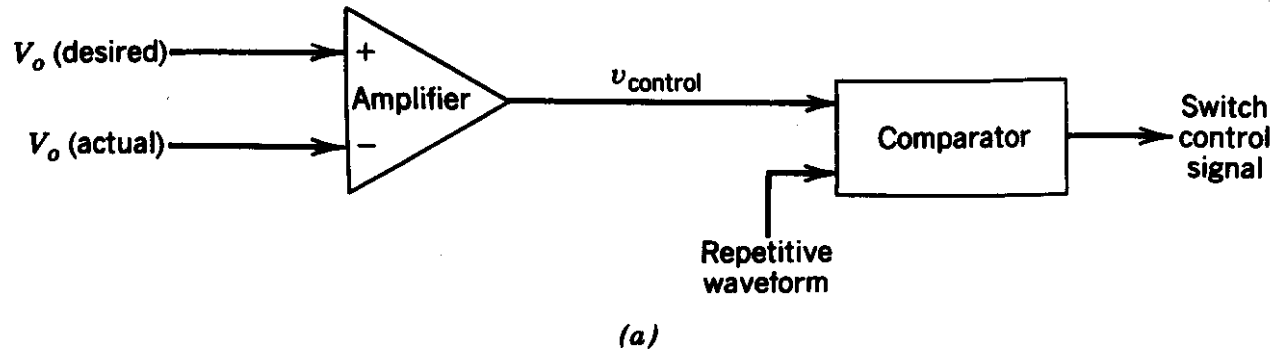

Back-boost


Wednesday, 10 May 2017 08:46

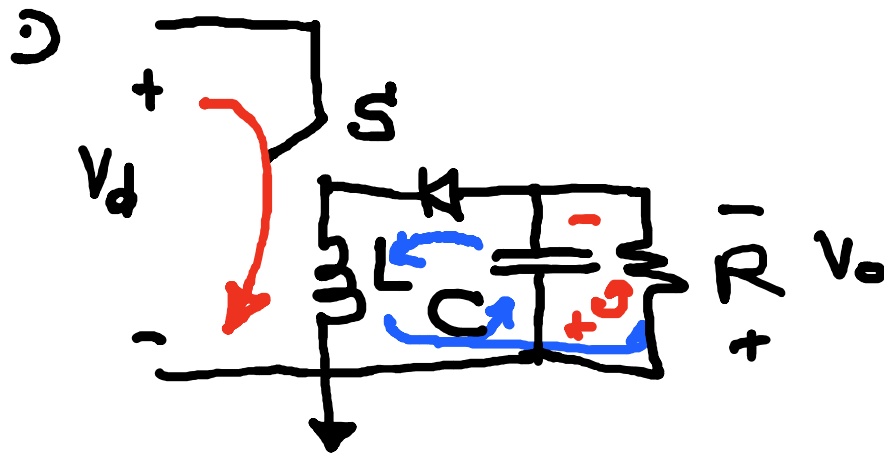

S ON Diodo OFF

$$\frac{di_L}{dt} = \frac{V_d}{L}$$

La C sostiene V_o

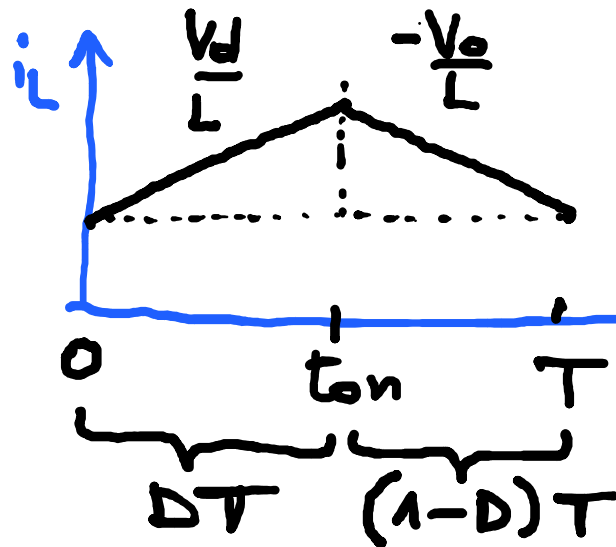

S OFF Diodo ON

$$\frac{V_d}{L} DT - \frac{V_o}{L} (1-D)T = 0$$


La L carica C e sostiene V_o

$$\frac{di_L}{dt} = -\frac{V_o}{L}$$

$$V_o = V_d \frac{D}{1-D}$$

Limite TRA conduzione continua e discontinua

Wednesday, 10 May 2017 09:01

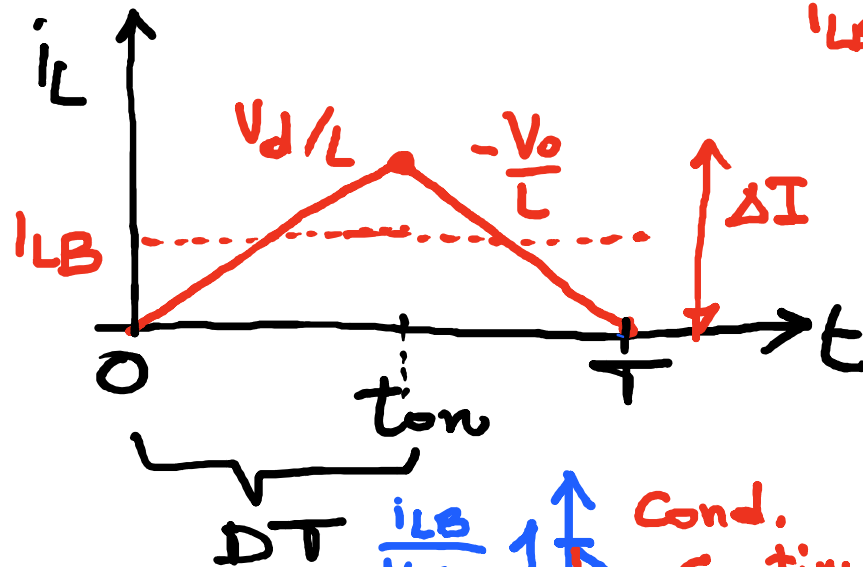


$$i_{LB} = \frac{\Delta I}{2} = \frac{V_d}{L} DT \frac{1}{2} = \frac{V_o(1-D)T}{L} \frac{1}{2}$$

$$i_{LB} = i_{LBmax}(1-D)$$

$$\left[i_{LBmax} \triangleq \frac{V_o T}{2L} \right]$$


$$\langle i_o \rangle = \langle i_L \rangle (1-D)$$
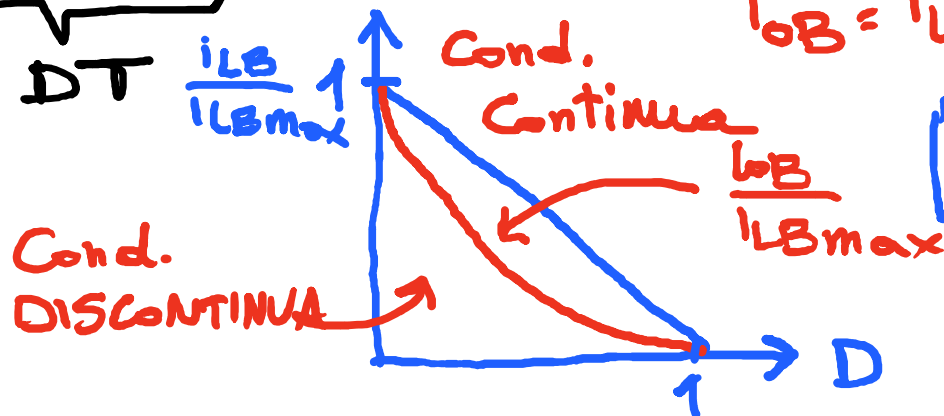
$$i_{oB} = i_{LB}(1-D) = i_{LBmax}(1-D)^2$$



Conduzione discontinua

Wednesday, 10 May 2017 09:09

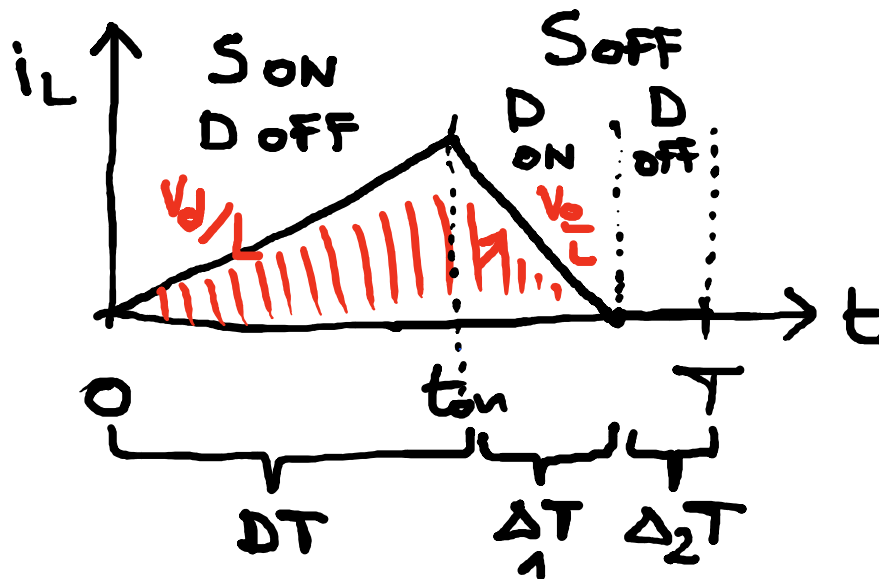

$$\langle i_L \rangle = \frac{V_d}{L} DT (D + \Delta_1) T \cdot \frac{1}{2} \cdot \frac{1}{T}$$


$$\langle i_o \rangle = \frac{\Delta_1}{\Delta_1 + D} \langle i_L \rangle =$$

$$= \frac{\Delta_1}{\Delta_1 + D} \frac{V_d}{L} \frac{DT}{2} (D + \Delta_1) = \frac{V_d}{L} \frac{DT}{2} \Delta_1$$

$$\frac{V_d}{L} DT = \frac{V_0}{L} \Delta_1 T \rightarrow V_d D = V_0 \Delta_1 \rightarrow \Delta_1 = \frac{V_d D}{V_0} \Rightarrow \langle i_o \rangle = \frac{V_d}{L} D^2 \left(\frac{V_d}{V_0} \right) \frac{T}{2} =$$

$$i_{LBmax} = i_{oBmax} = \frac{V_0 T}{2L}$$
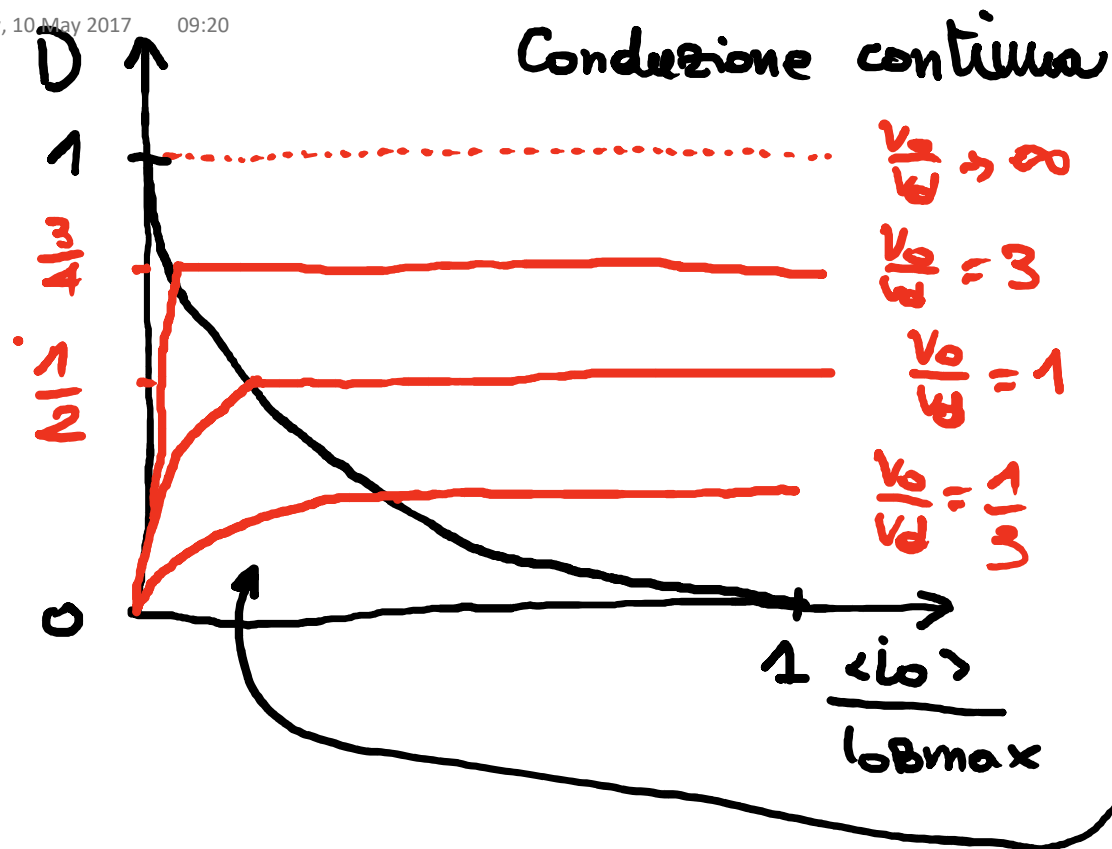
$$\langle i_o \rangle = i_{oBmax} \left(\frac{V_d}{V_0} \right)^2 D^2 \rightarrow D \propto \sqrt{\langle i_o \rangle}$$



$$\frac{V_0}{V_d} = \frac{D}{1-D}$$

Conduzione discontinua

$$D = \left(\frac{V_0}{V_d} \right) \sqrt{\frac{\langle I_o \rangle}{I_{oBmax}}}$$

Ripple :

Wednesday, 10 May 2017 09:33


Durante $t_{on} = DT$ la C si scarica su R

$$\Delta V = \frac{\Delta Q}{C} = \langle I_o \rangle \frac{DT}{C} = \frac{V_o}{R} \frac{DT}{C}$$

$$\Delta V \propto \frac{1}{C f_s}$$


Buck-Boost

Boost

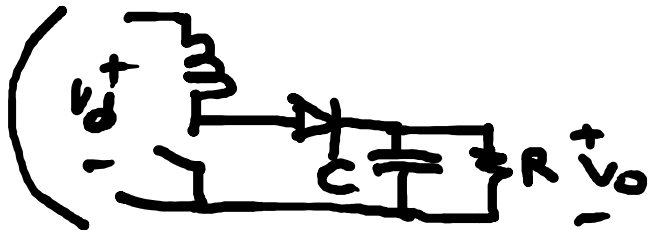


Cuk Converter

Wednesday, 10 May 2017 09:37

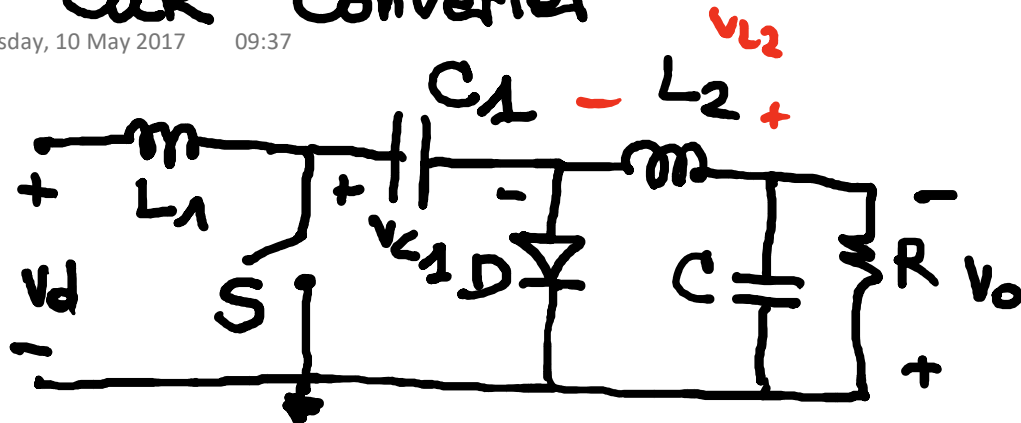


$$V_{c1} = V_d + V_o$$

Ton (D off)


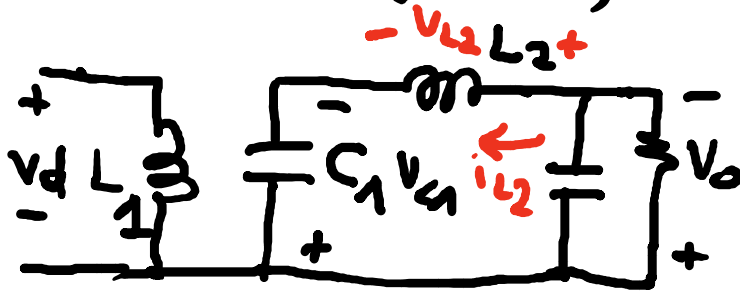


$$V_{L2} = V_d - V_o = V_d$$

Toff (D on)

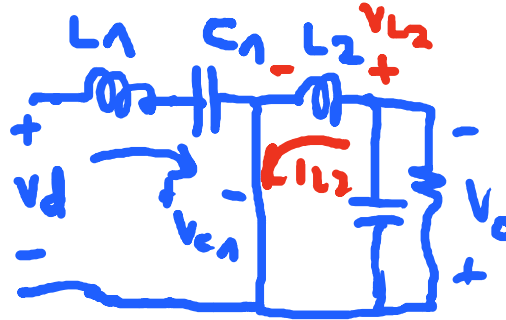


$$V_{L1} = V_d - V_{c1} = -V_o$$

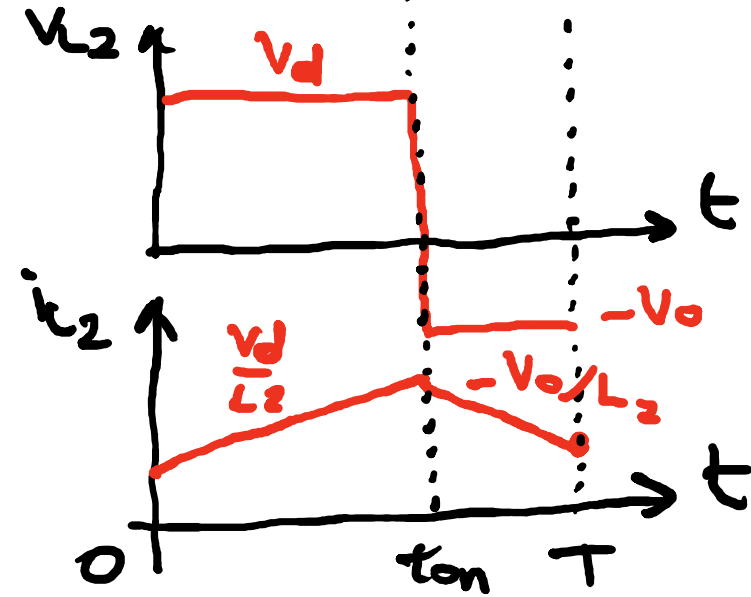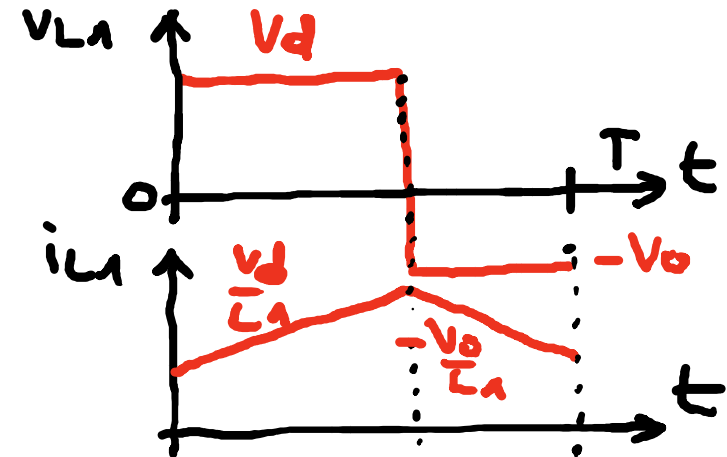


Full Bridge DCDC converter (a 4 quadrant)

Wednesday, 10 May 2017 09:53

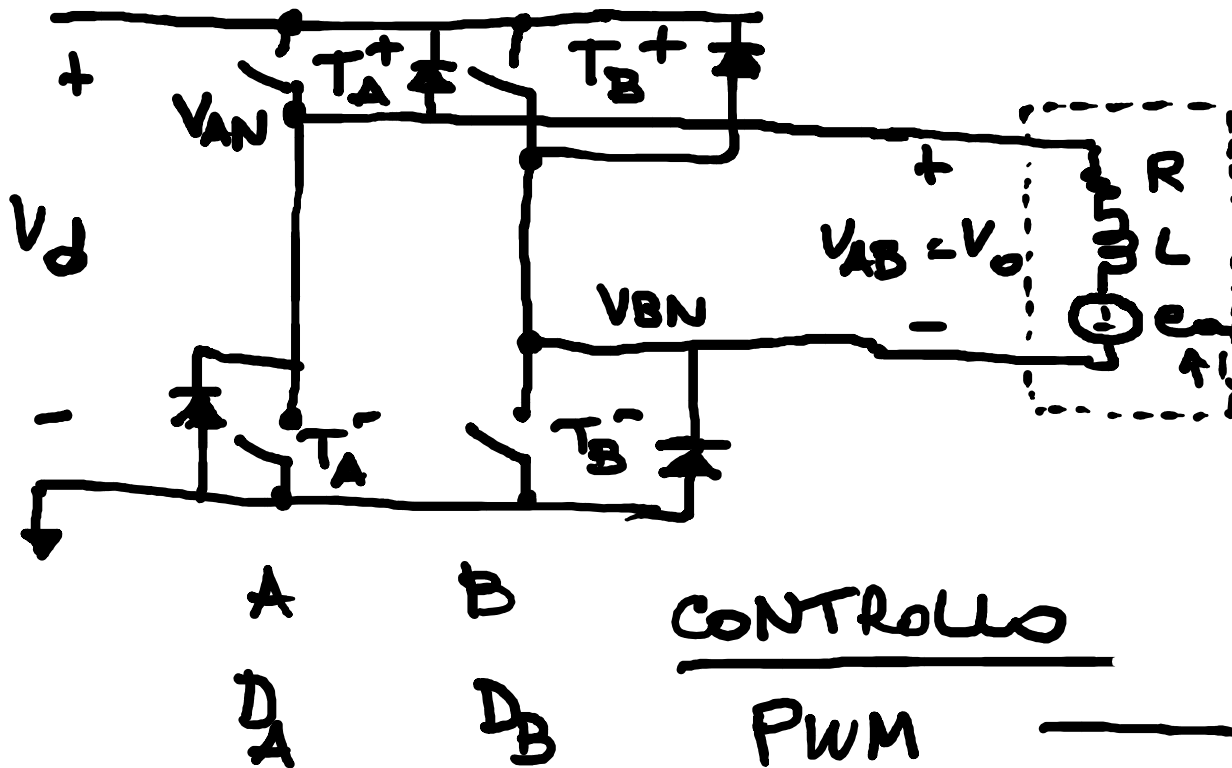

CONTROLS
PWM
Pulse Width Modulation

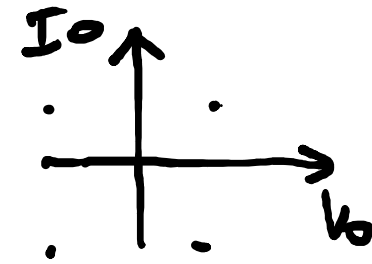

$$\langle V_{AN} \rangle = D_A V_d$$

$$\langle V_{BN} \rangle = D_B V_d$$

$$V_{AB} = V_{AN} - V_{BN}$$

$$\langle V_{AB} \rangle = \langle V_{AN} \rangle - \langle V_{BN} \rangle$$


$$\langle V_{AB} \rangle = V_d (D_A - D_B)$$

UNIPOLARE

BIPOLARE

PWM Bipolar

Wednesday, 10 May 2017 10:07

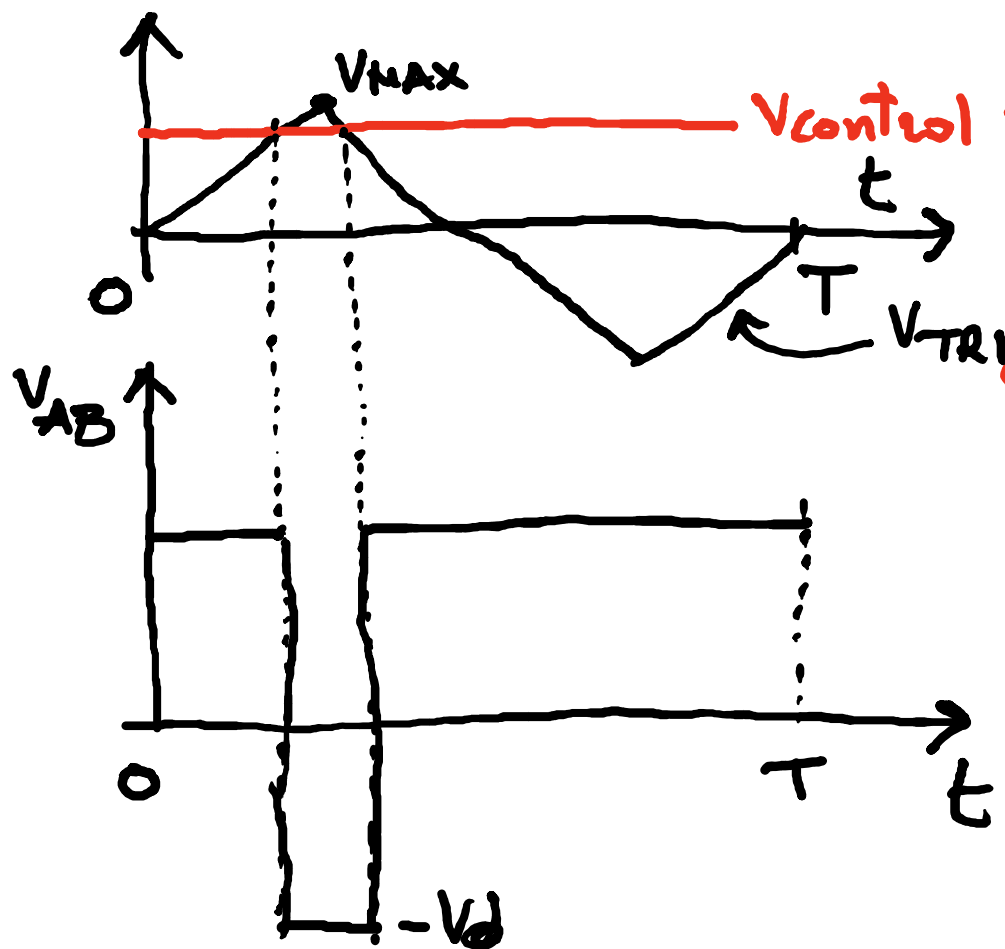

$$\left. \begin{array}{l} T_A^- \text{ ON} \\ T_B^+ \text{ ON} \end{array} \right\} \Rightarrow V_{AB} = -V_d$$

$$\left. \begin{array}{l} T_A^+ \text{ ON} \\ T_B^- \text{ ON} \end{array} \right\} \Rightarrow V_{AB} = +V_d$$


$$D_A = \frac{1}{2} + \frac{1}{2} \frac{V_{control}}{V_{max}}$$

$$D_B = \frac{1}{2} - \frac{1}{2} \frac{V_{control}}{V_{max}}$$

$$\langle V_{AB} \rangle = (D_A - D_B) V_d = \left(\frac{V_{control}}{V_{max}} \right) \cdot V_d$$

PWM Unipolare

Wednesday, 10 May 2017 10:16

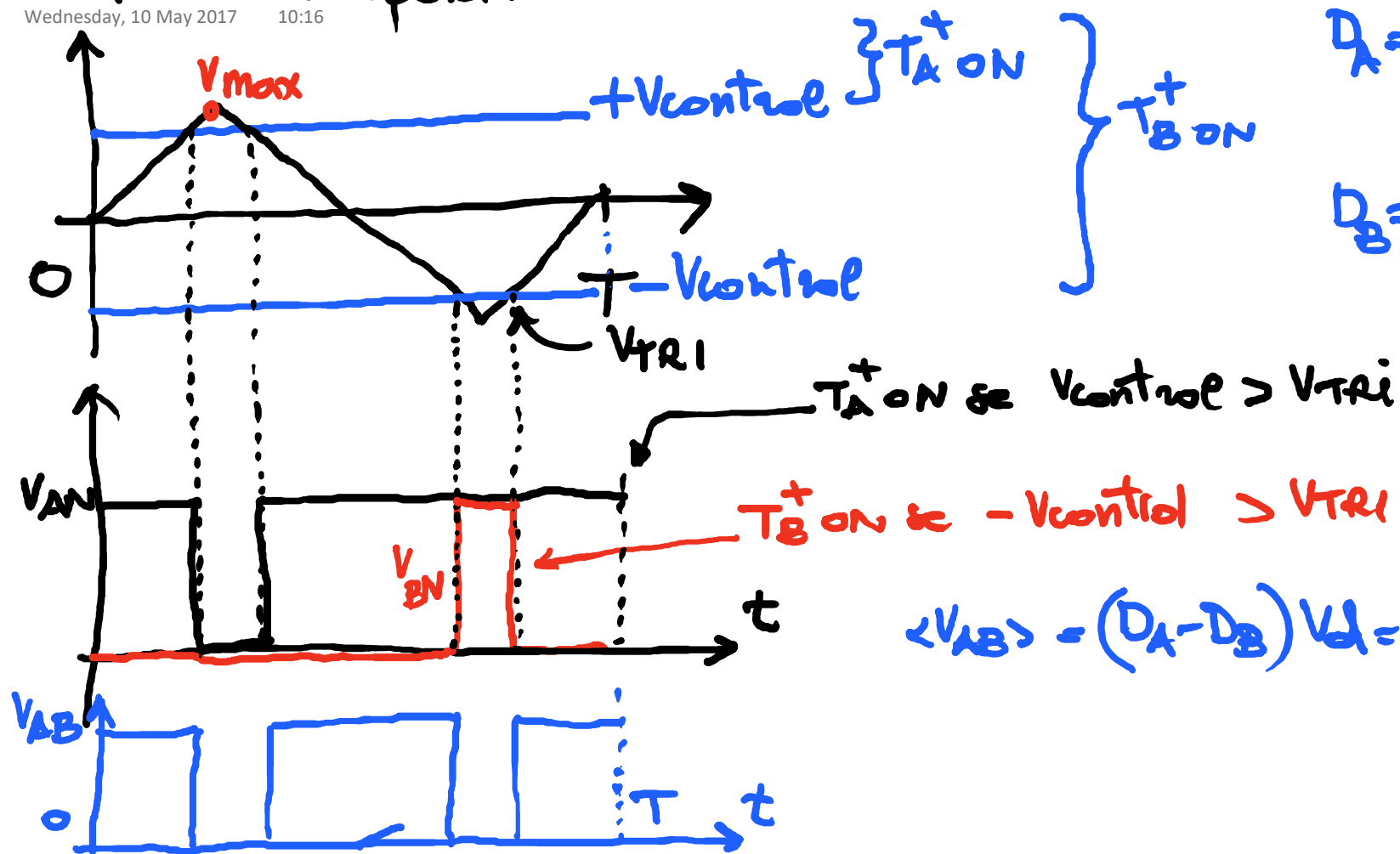

$$D_A = \frac{1}{2} + \frac{1}{2} \frac{V_{control}}{V_{max}}$$

$$D_B = \frac{1}{2} - \frac{1}{2} \frac{V_{control}}{V_{max}}$$

$$\langle V_{AB} \rangle = (D_A - D_B) V_d = \left(\frac{V_{control}}{V_{max}} \right) V_d$$

Convertitori DC DC inductorless


Tuesday, 16 May 2017 08:56

↳ Switched Cap vs inductor-based

↑ RIDOTTA AREA

↑ RIDOTTA ALTEZZA

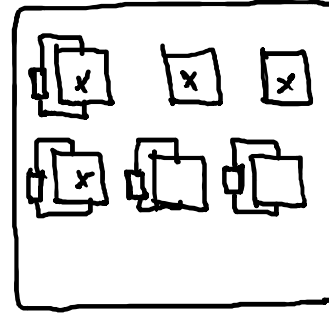↑ Possibilità di integrazione completa (per piccole potenze) e fornitura di power supply distribuita




↓ RAPPORTO DI CONVERSIONE IMPOSTO DALLA TOPOLOGIA

↓ EFFICIENZA DI CONVERSIONE RIDOTTA SE IL RAPPORTO DI CONVERSIONE NON È FRAZIONARIO


Esempio: LADDER 3:1

Tuesday, 16 May 2017 09:09

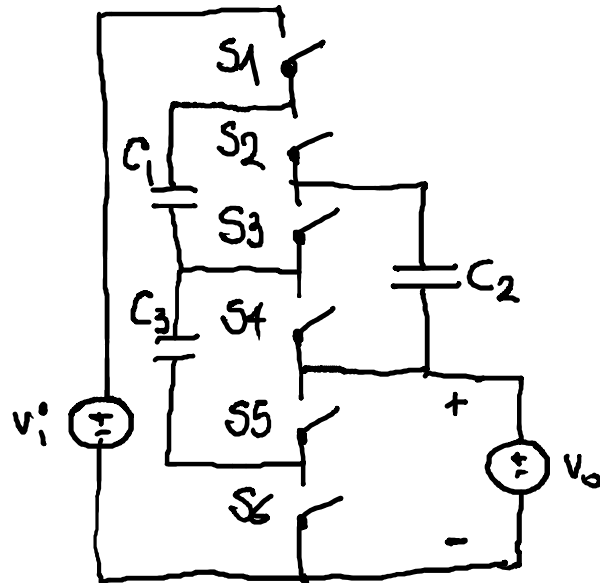


$$V_o = \frac{1}{3} V_i$$

$$I_i = q f_s$$

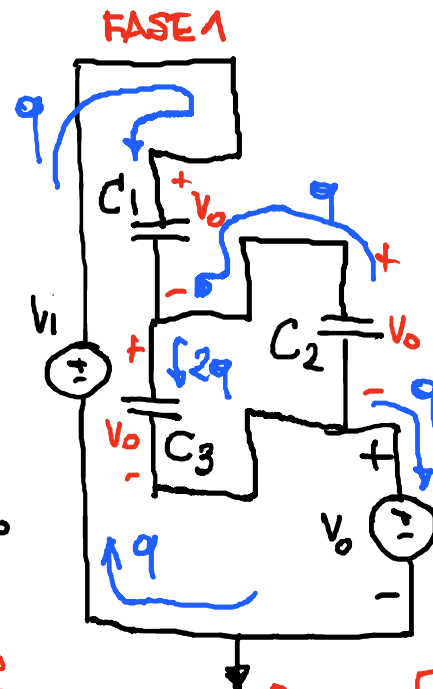

$$I_o = 3q f_s$$

$$I_o = 3I_i$$

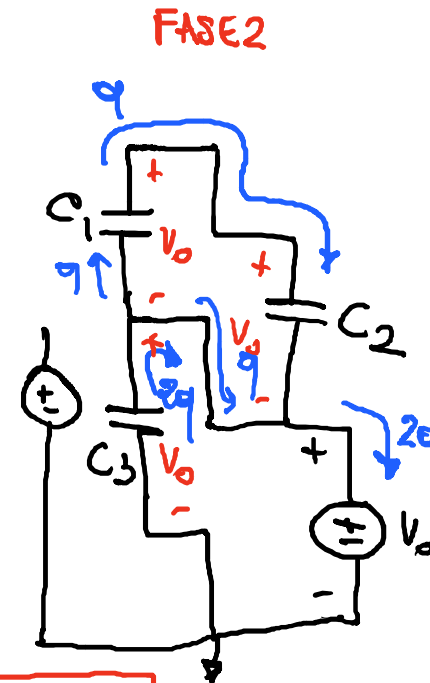

Limiti di funzionamento


Tuesday, 16 May 2017 09:26

1) SSL Slow Switching Limit [bassa f_s]

- durante ciascuna fase le capacità raggiungono lo stato finale di carica
- si può trascurare la potenza dissipata nella resistenza dei switch

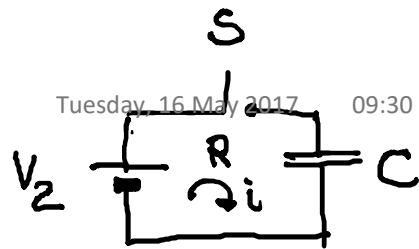2) FSL Fast Switching Limit [alta f_s]

- la tensione sulle capacità si può considerare costante durante ciascuna fase.



too divide S

$$V_C(0) = V_1$$

$$i(t) = \frac{V_2 - V_1}{R} e^{-\frac{t}{RC}}$$

ENERGIA EROGATA DA V_2

$$\int_0^{\infty} V_2 i(t) dt = V_2 \left(\frac{V_2 - V_1}{R} \right) RC = V_2 (V_2 - V_1) C$$

ENERGIA DISSIPATA NEL SWITCH

$$\int_0^{\infty} R i^2(t) dt = \int_0^{\infty} \frac{(V_2 - V_1)^2}{R} e^{-\frac{2t}{RC}} dt = \frac{(V_2 - V_1)^2}{R} \frac{RC}{2} = \frac{C}{2} (V_2 - V_1)^2$$

ENERGIA ACCUMULATA DALLA CAPACITANZA $= \frac{1}{2} C (V_2^2 - V_1^2)$

SSL

Tuesday, 16 May 2017 09:38

3 vettore moltiplicatore di carica

$$\vec{a}^{(1)} = \left\{ a_{out}^{(1)}, a_{c1}^{(1)}, a_{c2}^{(1)}, a_{c3}^{(1)}, a_{in}^{(1)} \right\}$$

FASE 1

carica che passa durante la fase
NORMAIZZATA rispetto alle cariche di uscita in un periodo

ES. LADDER


$$\vec{a}^{(1)} = \left\{ \frac{1}{3}, \frac{1}{3}, -\frac{1}{3}, \frac{1}{3}, \frac{1}{3} \right\}$$
$$\vec{a}^{(2)} = \left\{ \frac{2}{3}, -\frac{1}{3}, \frac{1}{3}, -\frac{2}{3}, 0 \right\}$$

Teorema di Tellegen

Tuesday, 16 May 2017 09:46

$$\sum_i v_i i_i = 0$$

$$v_{out} i_{out} + \sum_{i \in C_{op}} v_{c_i} i_{c_i} - v_{in} i_{in} = 0$$

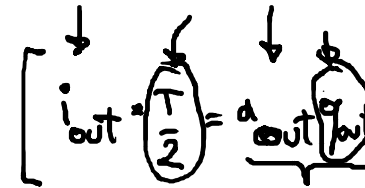

Fase 1

$$v_{out} a_{out}^{(1)} + \sum_{i \in C_{op}} v_{c_i}^{(1)} a_{c_i}^{(1)} - v_{in} d_{in}^{(1)} = 0$$

Fase 2

$$v_{out} a_{out}^{(2)} + \sum_{i \in C_{op}} v_{c_i}^{(2)} a_{c_i}^{(2)} - v_{in} a_{in}^{(2)} = 0$$

Somma

$$v_{out} + \sum_{i \in C_{op}} [v_{c_i}^{(1)} - v_{c_i}^{(2)}] a_{c_i} - v_{in} [d_{in}^{(1)} + a_{in}^{(2)}] = 0$$

N.B.


$$a_{out}^{(1)} + a_{out}^{(2)} = 1$$

$$a_{c_i}^{(1)} = -a_{c_i}^{(2)} = a_{c_i}$$

$$\Delta V_{out} = V_{out}^{\circ} - V_{out} = \sum_{i \in G_{op}} \underbrace{\left[V_{ci}^{(1)} - V_{ci}^{(2)} \right]}_{\frac{a_{ci} q_{out}}{C_i}} a_{ci} = \sum_{i \in G_{op}} \frac{a_{ci}^2}{C_i} q_{out}$$

↑
perdita di tensione
rispetto al caso
a vuoto

$$\Delta V_{out} = \underbrace{\left[\sum_{i \in G_{op}} \frac{a_{ci}^2}{C_i f_s} \right]}_{R_{out}^{SSL}} \cdot I_{out}$$

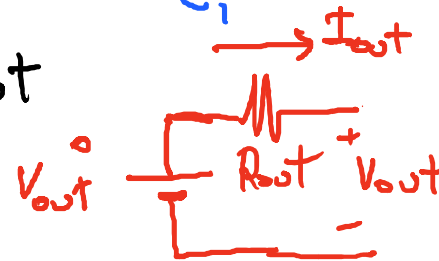

SSL 2
 $R_{out} I_{out}$ ← Potenza dissipata internamente

FSL

Tuesday, 16 May 2017 10:10

R_i : RESISTENZA SERIE DEL SWITCH i

\vec{a}_s vettore di moltiplicatore di carica per i switch

ES.

$$\vec{a}_s^{(1)} = \left\{ \overset{s_1}{\frac{1}{3}} \quad \overset{s_2}{0} \quad \overset{s_3}{\frac{1}{3}} \quad \overset{s_4}{0} \quad \overset{s_5}{-\frac{2}{3}} \quad \overset{s_6}{0} \right\}$$

$$\vec{a}_s^{(2)} = \left\{ 0 \quad \frac{1}{3} \quad 0 \quad \frac{1}{3} \quad 0 \quad -\frac{2}{3} \right\}$$

switch s_i $i_{s,i}^{(1)} = 2 a_{s,i}^{(1)} q_{out} f_s$; $i_{s,i}^{(2)} = 2 a_{s,i}^{(2)} q_{out} f_s$ $I_{out} q_{out} f_s$

$$P_{FSL} = \sum_{i \in \text{Switch}} R_i i_{s,i}^2 = \sum_{i \in \text{Switch}} 4 R_i q_{out}^2 f_s^2 a_{s,i}^2 = R_{out} I_{out}^2$$

LA FASE NON NULLA


$$R_{out}^{FSL} = \sum_{i \in \text{switch}} 4 R_i [a_{s,i}]^2$$

Nel caso intermedio tra i due limiti

Tuesday, 16 May 2017

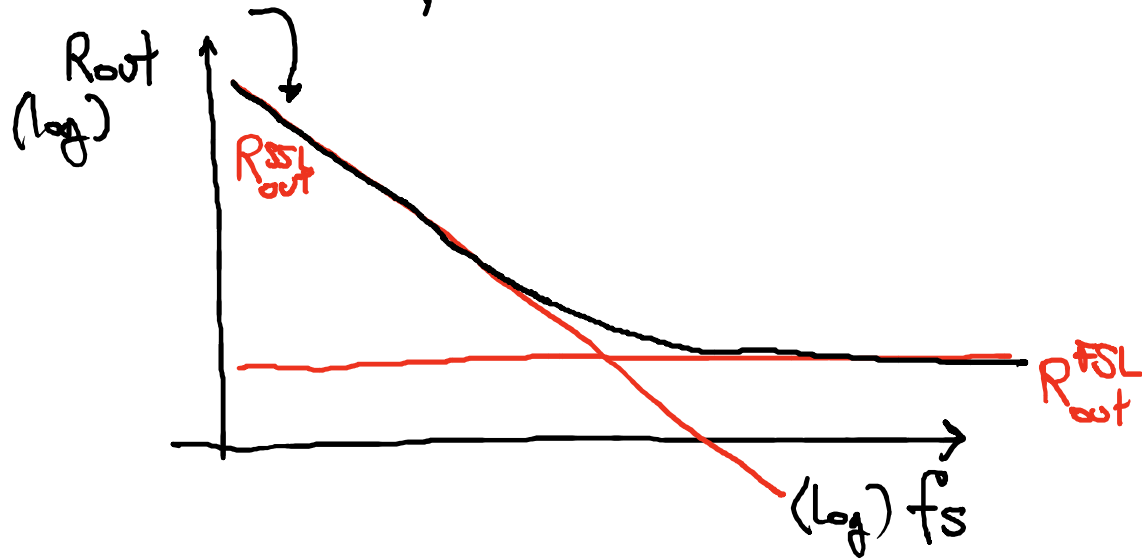10:23

$$R_{out} = \sqrt{R_{out}^{FSL^2} + R_{out}^{SSL^2}}$$




Altre perdite

Tuesday, 16 May 2017 10:28

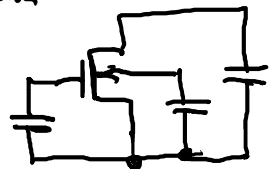3) Switching Loss

$$P_{sw} = f_s \sum_{i \in \text{Switch}} \left[C_{Gi} V_{Gi}^2 + C_{Di} V_{Di}^2 + C_{Bi} V_{Bi}^2 \right]$$



$$\propto f_s, A_s$$

↑ AREA COMPLESSIVA
OCCUPATA DAI SWITCH

3) Bottom-plate parasitic capacitance



$$P_{CAP} = f_s \sum_{i \in \text{Cap}} C_{Bi} V_{Bi}^2$$

AREA COMPLESSIVA
OCCUPATA DALLE
CAPACITÀ

$$\propto f_s, A_c$$

3) RESISTENZA SERIE EQUIVALENTE



$$P_{ESR} = R_{ESR} I_{out}^2$$

$$P_{\text{Loss}} = R_{\text{out}} I_{\text{out}}^2 + P_{\text{SW}} + P_{\text{CAP}} + P_{\text{ESR}}$$

$$P_{\text{out}} = V_{\text{out}} I_{\text{out}}$$

$$\eta = \frac{P_{\text{out}}}{P_{\text{out}} + P_{\text{Loss}}} \rightarrow \underline{\underline{50\% - 90\%}}$$



EFFICIENZA
DI CONVERSIONE

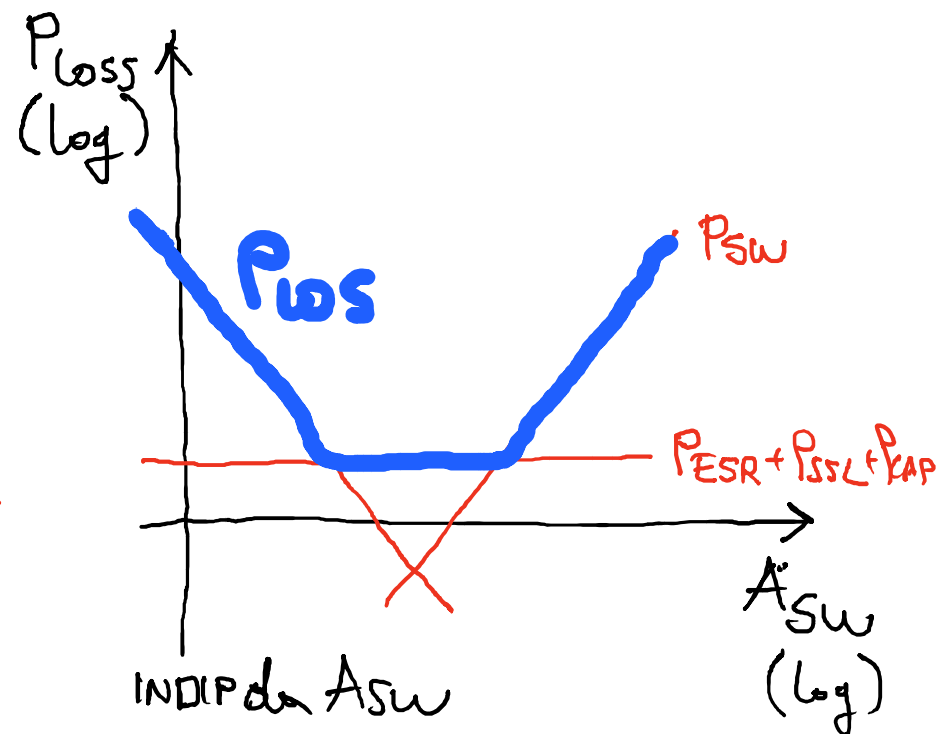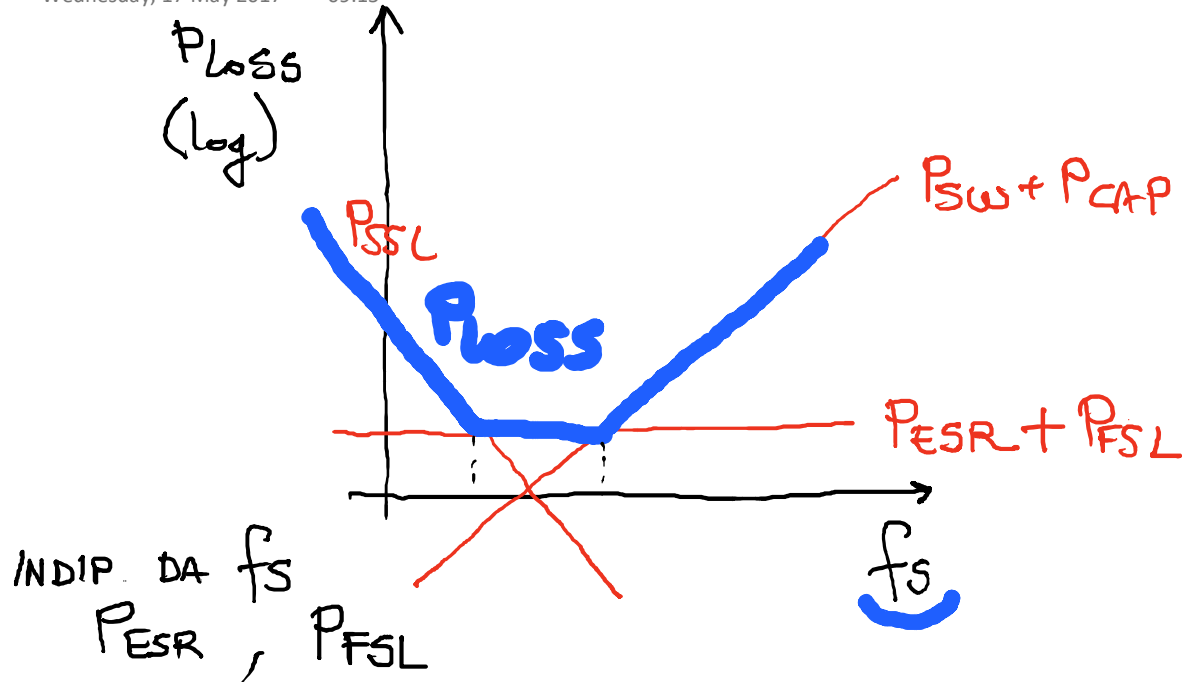

$$R_{out}^2 = \sqrt{P_{FSL}^2 + P_{SSL}^2} \cdot I_{out}^2 = \sqrt{\frac{P_{FSL}^2}{P_{FSL}} \cdot \frac{P_{SSL}^2}{P_{SSL}}}$$

$\propto f_s$ P_{SW} , P_{CAP}
 $\propto 1/f_s$ P_{SSL}

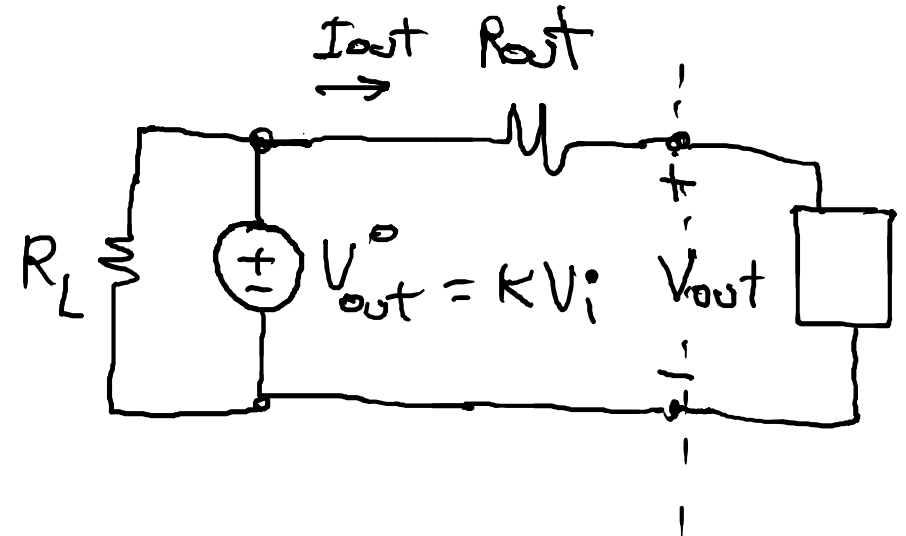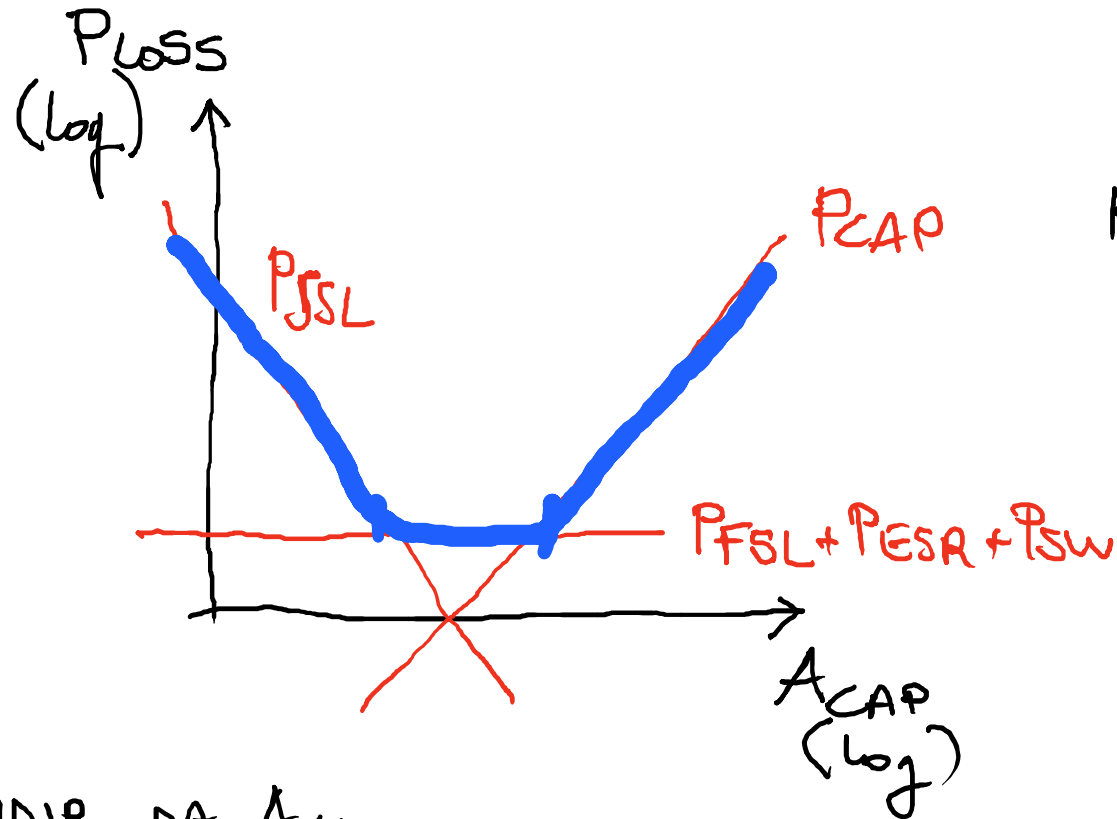$\propto A_{SW}$ P_{SW}
 $\propto \frac{1}{A_{SW}}$ P_{FSL}



INDIP DA A_{CAP}

P_{FSL}, P_{ESR}, P_{SW}

$\propto A_{CAP} \rightarrow P_{CAP}$

$\propto 1/A_{CAP} \rightarrow P_{FSL}$