


Power Converters

Wednesday, November 16, 2016 4:38 PM

- Power delivery network

1 PMIC

"Power Management IC"

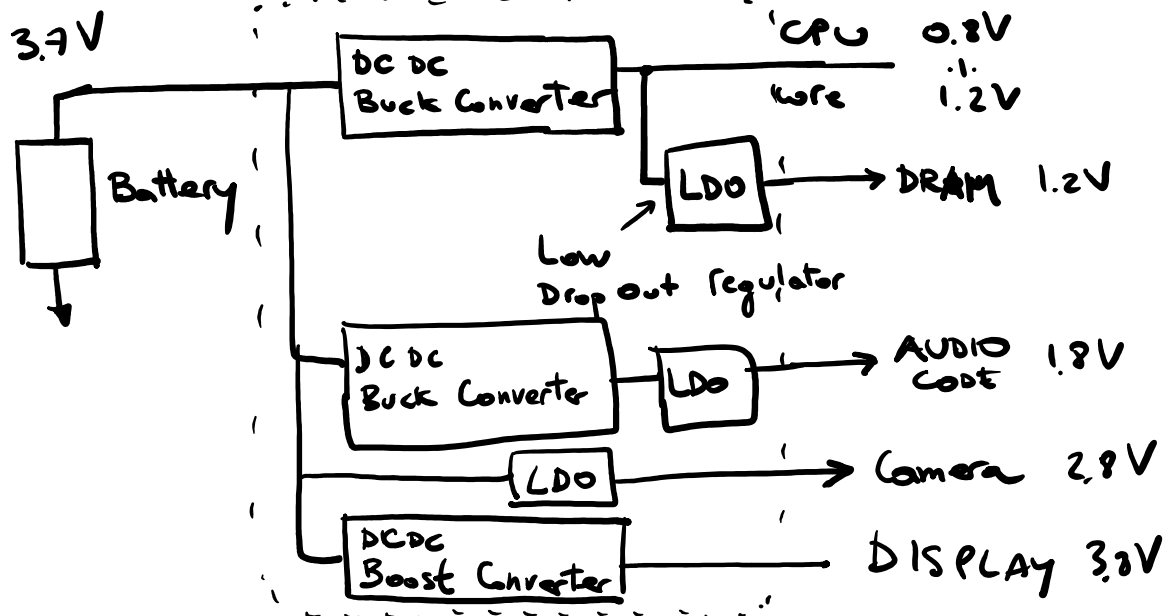



dcdc Page 1

Wednesday, November 16, 2016 4:52 PM

Buck Converter
(Step Down)

[Switching Regulator]


only reactive elements L, C
and switches

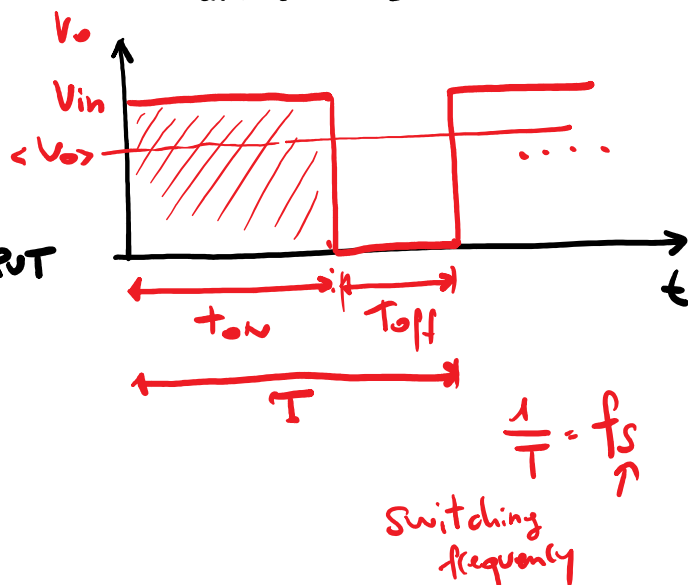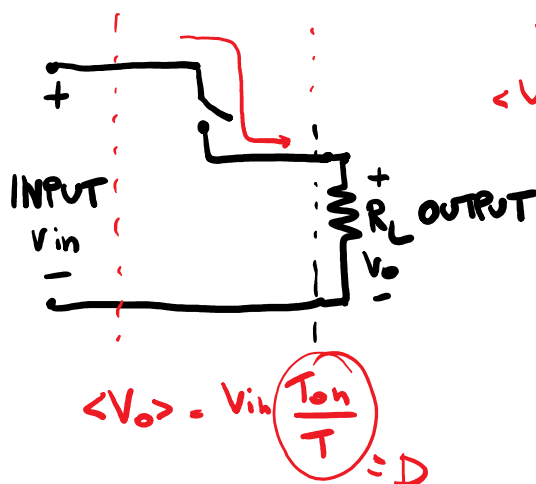

dcdc Page 2

BUCK CONVERTER

Wednesday, November 16, 2016 5:03 PM

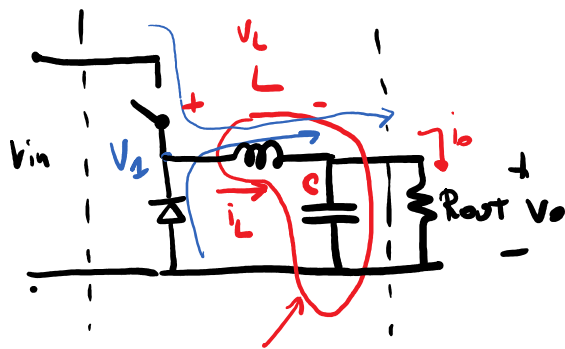


LOW PASS FILTER

$$f_s \gg f_c = \frac{1}{2\pi\sqrt{LC}}$$

cut off frequency
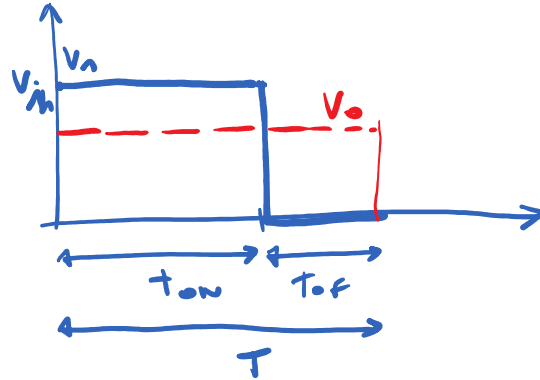
$$\langle V_o \rangle = \underbrace{\frac{T_{on}}{T}}_D V_{in} = V_o$$



inductor


$$V_L = L \frac{di_L}{dt}$$

dcdc Page 3

Wednesday, November 16, 2016 5:11 PM

$$T_{on}: V_L = V_{in} - V_o \Rightarrow \frac{di_L}{dt} = \frac{V_L}{L} = \frac{V_{in} - V_o}{L}$$
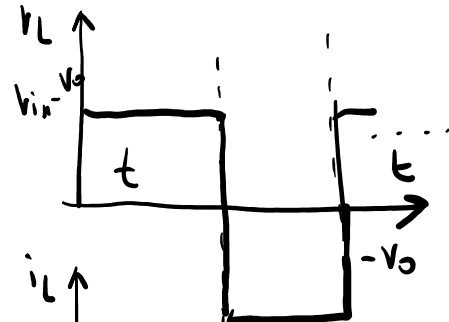
$$T_{off}: V_L = -V_o \rightarrow \frac{di_L}{dt} = \frac{V_L}{L} = -\frac{V_o}{L}$$



$$\underbrace{\frac{V_{in} - V_o}{L} \cdot t_{on}}_{\Delta I} = +\frac{V_o}{L} t_{off} = \frac{V_o}{L} (T - t_{on})$$


$$V_o = \frac{T_{on}}{T} V_{in}$$

$$i_o = \frac{V_o}{R_{out}}$$

dcdc Page 4

Limit of continuous conduction

Wednesday, November 16, 2016 5:21 PM

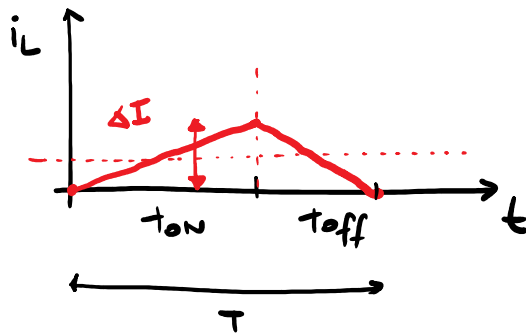

in the limit

$$\Delta I = 2 i_o$$

$$\frac{V_{in} - V_o}{L} t_{on} = 2 i_o$$

\uparrow
 DT

$$V_o = \frac{t_{on}}{T} V_{in}$$

\downarrow
 D


$$\frac{V_{in}(1-D)DT}{L} = 2 i_o$$

current at the
limit of continuous
conduction

$$\rightarrow i_o = \frac{V_{in} T}{2L} D(1-D)$$

$$i_o = i_{o_{max}} \quad 4D(1-D)$$

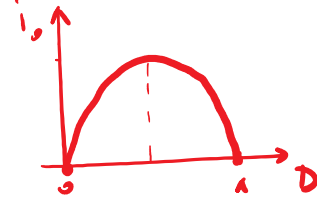
$$\uparrow i_{o_{max}} = \frac{V_{in} T}{8L}$$



dcdc Page 5

Discontinuous conduction

Wednesday, November 16, 2016 5:27 PM

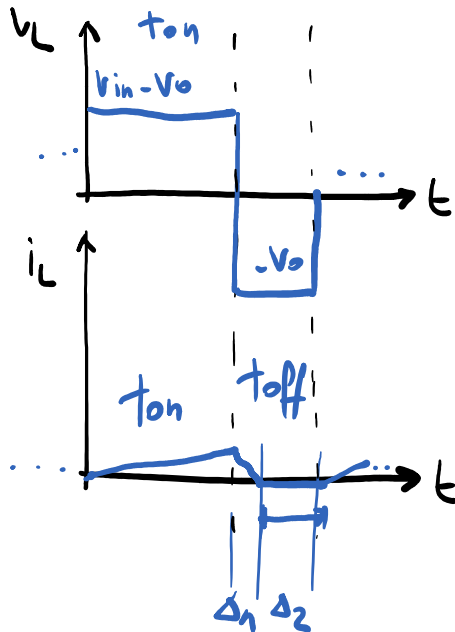

dcdc Page 6